

Finite State Machines in Verilog

Jay Brockman

Department of Computer Science and Engineering
Department of Electrical Engineering
University of Notre Dame

Key Points


- Not difficult to describe FSM *behavior* in an HDL
- But goal is to *synthesize good hardware*
 - Need to be very precise so synthesis tools can do this
 - Subtle mistakes can have major effect
- My goal: equip you with a simple yet flexible and reliable approach to writing FSMs in Verilog
 - enough detail to avoid getting bitten
 - but also avoid confusion




What we know so far

- Finite state machines
 - Binary encoded state names
 - Next state depends on
 - current state
 - input
 - Outputs depend on
 - Moore machine: state only
 - Mealy machine: state and inputs
- Verilog
 - Combinational logic
 - sensitive to changes in signal levels
 - Sequential logic (registers)
 - sensitive to changes in clock edges (and reset)

Describing FSM in Verilog

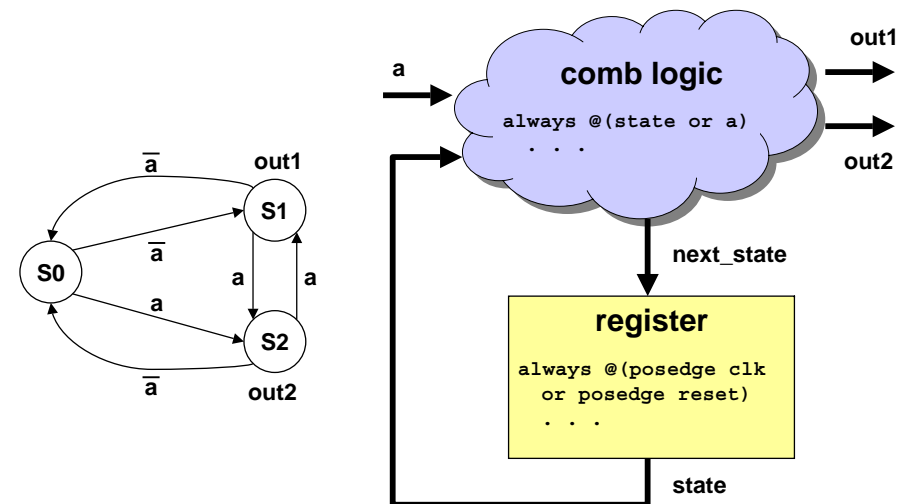

 

```

module fsm(clk, reset, a, out1, out2);
  input clk;
  input reset;
  input a;
  output reg out1;
  output reg out2;

```

```

  reg [1:0] state;
  reg [1:0] next_state;

  parameter s0 = 2'b00;
  parameter s1 = 2'b01;
  parameter s2 = 2'b10;

```

```

always @(posedge clk or posedge reset)
  if (reset)
    state <= s0;
  else
    state <= next_state;


```

```


always @(state or a)
  case (state)
    s0: begin
      if (a == 0)
        next_state <= s1;
      else
        next_state <= s2;
      out1 <= 0;
      out2 <= 0;
    end
    s1: begin
      if (a == 0)
        next_state <= s0;
      else
        next_state <= s2;
      out1 <= 1;
      out2 <= 0;
    end
    s2: begin
      if (a == 0)
        next_state <= s0;
      else
        next_state <= s1;
      out1 <= 0;
      out2 <= 1;
    end
  endcase
endmodule

```

Simulation Results

 

Looks good

 


Unassigned Output (Beware!)

Simplifying Notations

- FSMs
 - Assume unassigned output implicitly assigned 0

from Chapter 3

 


```

always @(state or a)
  case (state)
    s0: begin
      if (a == 0)
        next_state <= s1;
      else
        next_state <= s2;
      out1 <= 0;
      out2 <= 0;
    end
    s1: begin
      if (a == 0)
        next_state <= s0;
      else
        next_state <= s2;
      out1 <= 1;
    end
    s2: begin
      if (a == 0)
        next_state <= s0;
      else
        next_state <= s1;
      out2 <= 1;
    end
  endcase
endmodule

```




Unassigned Output: Simulation Results

 

Not what we intended!

 - Doesn't default to 0
- Keeps previous value




Synthesis of Unassigned Output

```



module unassigned_output(s, out1, out2);
    input [1:0] s;
    output reg out1;
    output reg out2;

    parameter s0 = 2'b00;
    parameter s1 = 2'b01;
    parameter s2 = 2'b10;

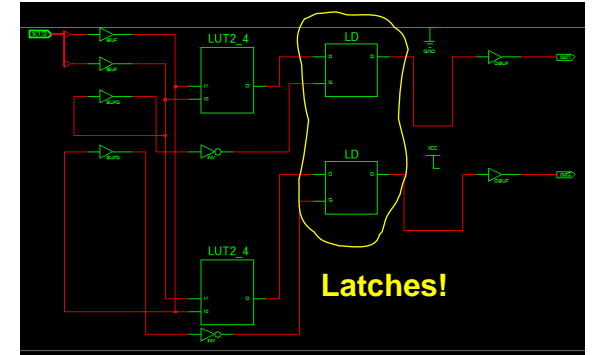    always @(s)
        case (s)
            s0: begin
                out1 <= 0;
                out2 <= 0;
            end
            s1: out1 <= 1;
            s2: out2 <= 1;
        endcase
endmodule
    
```



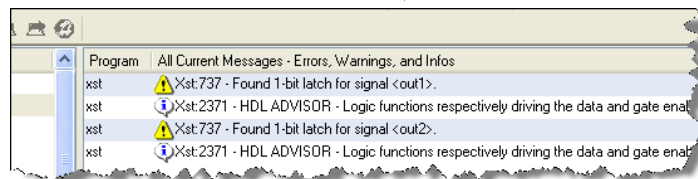 
Detecting Unassigned Output/Latch Problem



Always assign all outputs! Don't leave undefined input cases!

```

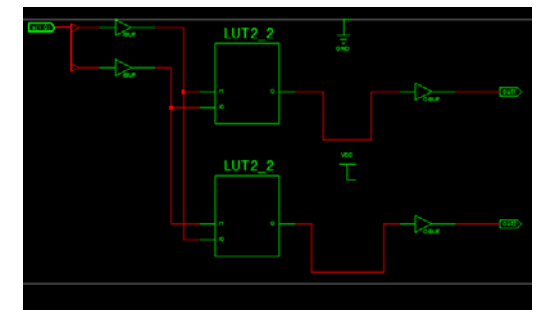always @(s)
    case (s)
        s0: begin
            out1 <= 0;
            out2 <= 0;
        end
        s1: begin
            out1 <= 1;
            out2 <= 0;
        end
        s2: begin
            out1 <= 0;
            out2 <= 1;
        end
        default: begin
            out1 <= 0;
            out2 <= 0;
        end
    endcase
    
```




Define default input case so
FSM can't get "stuck"
(Also a latch problem)

Mealy Machine

outputs on transitions

 Inputs: enough (bit)
Outputs: d, clear (bit)



```
always @(state or enough)
case (state)
s_init: begin
next_state <= s_wait;
d <= 0; clear <= 1;
end
s_wait: begin
if (!enough)
begin
next_state <= s_wait;
d <= 0; clear <= 0;
end
else
begin
next_state <= s_init;
d <= 1; clear <= 0;
end
end
endcase
```

Binary vs. One-Hot Encoding

binary

```
parameter s0 = 2'b00;
parameter s1 = 2'b01;
parameter s2 = 2'b10;
```

one-hot

```
parameter s0 = 3'b001;
parameter s1 = 3'b010;
parameter s2 = 3'b100;
```

- Synthesis tools will generally optimize, regardless of how you encode states
- FPGAs generally prefer one-hot
 - less fan in → simpler logic
 - less fan in → faster logic
 - plenty of flip-flops available (approximately 1 per LUT)