

Preface



- Any questions from last time?
 - Will review 1st 22 slides
- A bit more motivation, information about me
 - Research
 - ND
- A bit more about this class...
 - Microsoft
- Later:
 - HW 1
 - Review session
 - MD McNally about Lab 1



(1)
Any questions from
last time?



Digital Design

Chapter 8: Programmable Processors


Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>

Copyright © 2007 Frank Vahid


*Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites.. PowerPoint source (or pdf with animations) may **not** be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.*

Introduction


- Programmable (general-purpose) processor
 - Mass-produced, then programmed to implement different processing tasks
 - Well-known common programmable processors: Pentium, Sparc, PowerPC
 - Lesser-known but still common: ARM, MIPS, 8051, PIC
 - Low-cost embedded processors found in cell phones, blinking shoes, etc.
 - Instructive to design a very simple programmable processor
 - Real processors can be much more complex

 

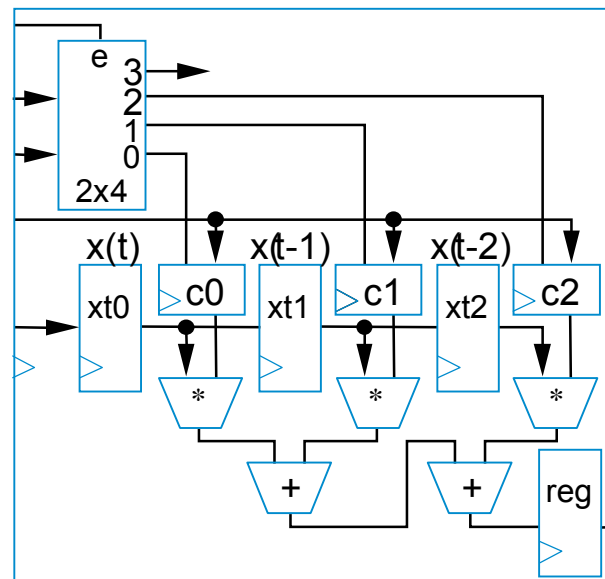Seatbelt warning
light single-purpose
processor



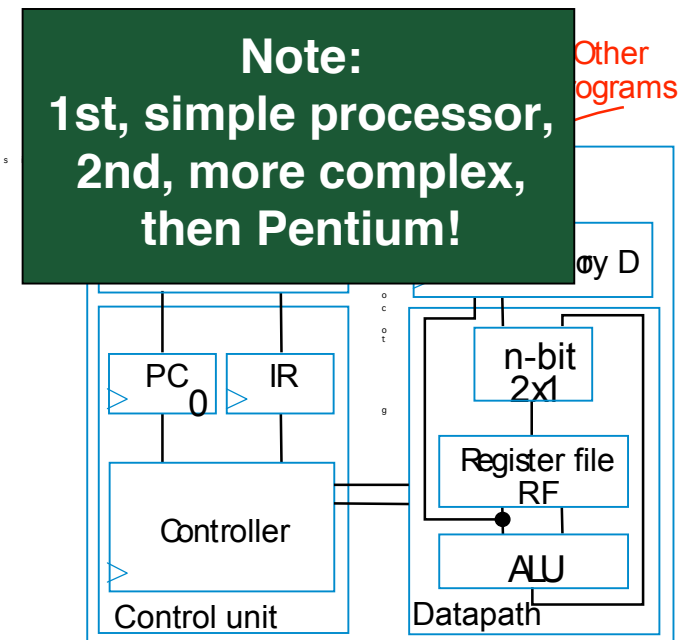3-tap FIR filter
single-purpose processor




General-purpose processor



Basic Architecture

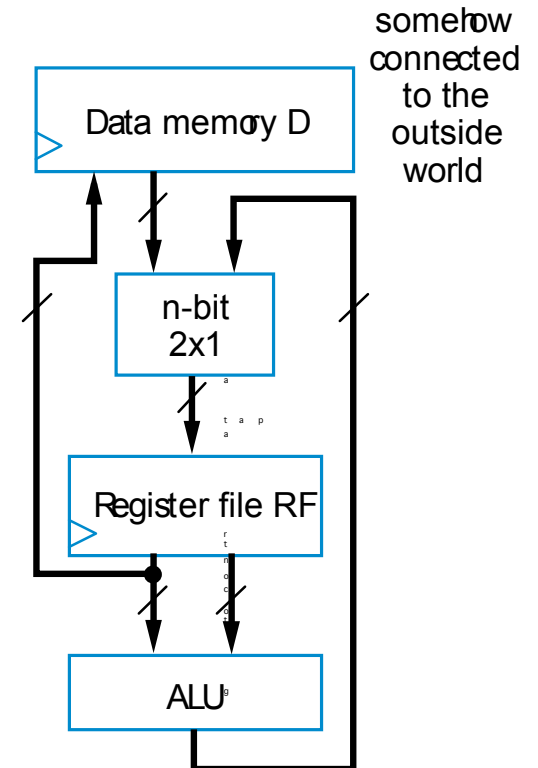- Processing generally consists of:
 - Loading some data
 - Transforming that data
 - Storing that data
- *Basic datapath*: Useful circuit in a programmable processor
 - Can read/write data memory, where main data exists
 - Has register file to hold data locally
 - Has ALU to transform local data



Datapath

Compare to Slide15,
Lecture 01.




Basic Datapath Operations


- Load operation: Load data from data memory to RF
- ALU operation: Transforms data by passing one or two RF register values through ALU, performing operation (ADD, SUB, AND, OR, etc.), and writing back into RF.
- Store operation: Stores RF register value back into data memory
- Each operation can be done in one clock cycle

Understand
idea of
register file?


Versus
RAM?

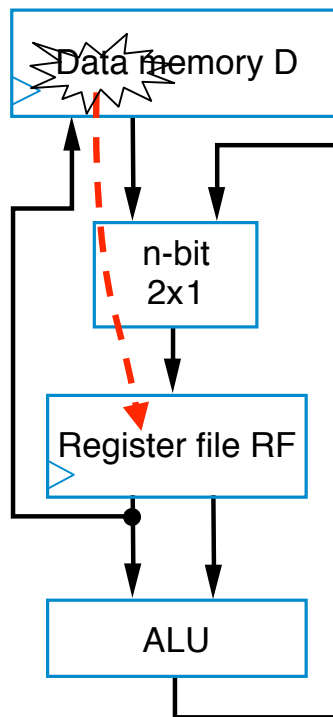

Load operation

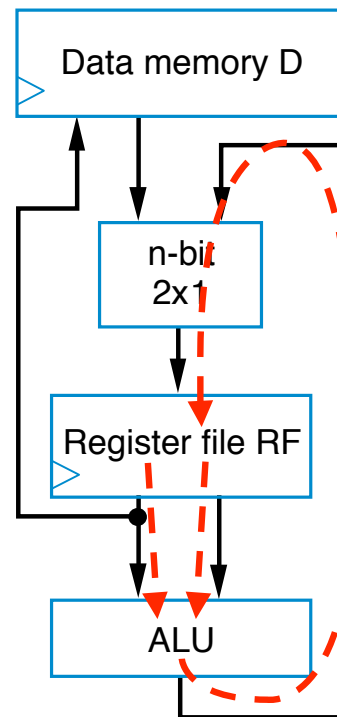

ALU operation

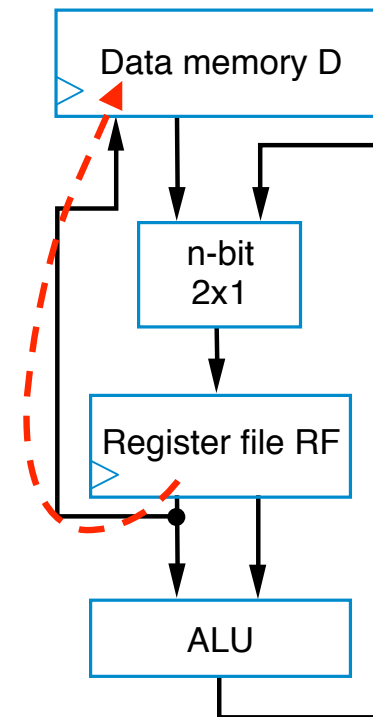


Store operation




Basic Datapath Operations

- **Q:** Which are valid *single-cycle operations* for given datapath?
 - Move D[1] to RF[1] (i.e., $RF[1] = D[1]$)
 - **A:** YES – That's a load operation
 - Store RF[1] to D[9] and store RF[2] to D[10]
 - **A:** NO – Requires two separate store operations
 - Add D[0] plus D[1], store result in D[9]
 - **A:** NO – ALU operation (ADD) only works with RF. Requires two load operations (e.g., $RF[0]=D[0]$; $RF[1]=D[1]$), an ALU operation (e.g., $RF[2]=RF[0]+RF[1]$), and a store operation (e.g., $D[9]=RF[2]$)


Let's do 1 more example...

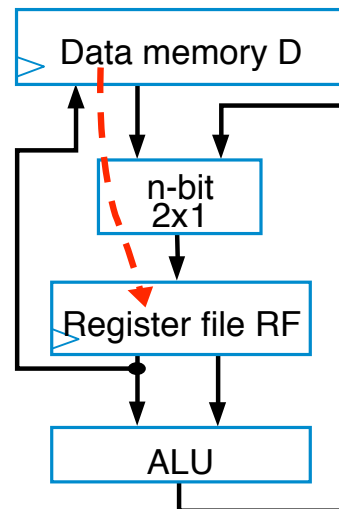

Load operation

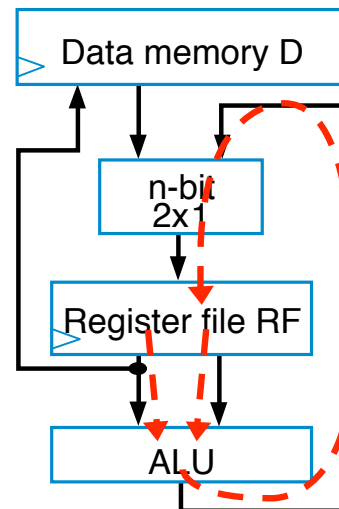

ALU operation

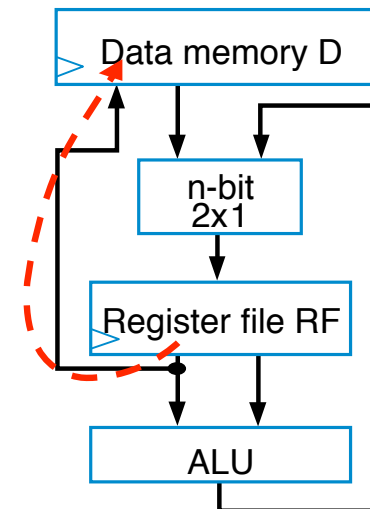


Store operation

One more example...

- Q: Which are valid *single-cycle operations* for given datapath?
 - Add $d(0) + R1$, store in R2?

Why?
No direct path from memory
to ALU

 

Exercise: Basic Datapath Operations

Q: How many cycles does each of the following take for given datapath?

- Move RF[1] to RF[2]
- Add D[8] with RF[2] and store the result in RF[4]
- Add D[8] with RF[1], then add the result with RF[4], and store the final result in D[8]


One more example...

- **Q:** How can we do: $d(0) + R1$, store in R2?

Need at least 2 instructions:


MOV R3, D(0) # LOAD D(0)

ADD R2, R1, R3 # Do the ADD

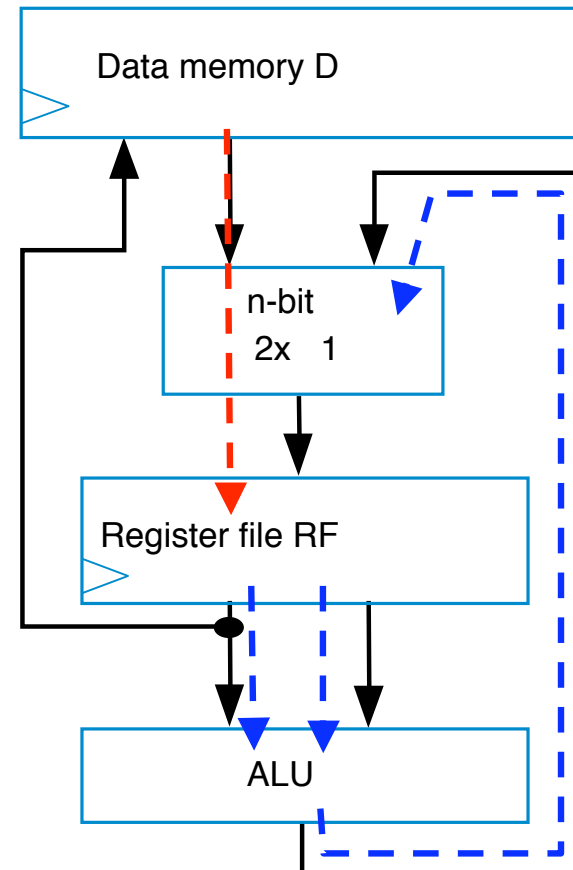


Basic Architecture – Control Unit

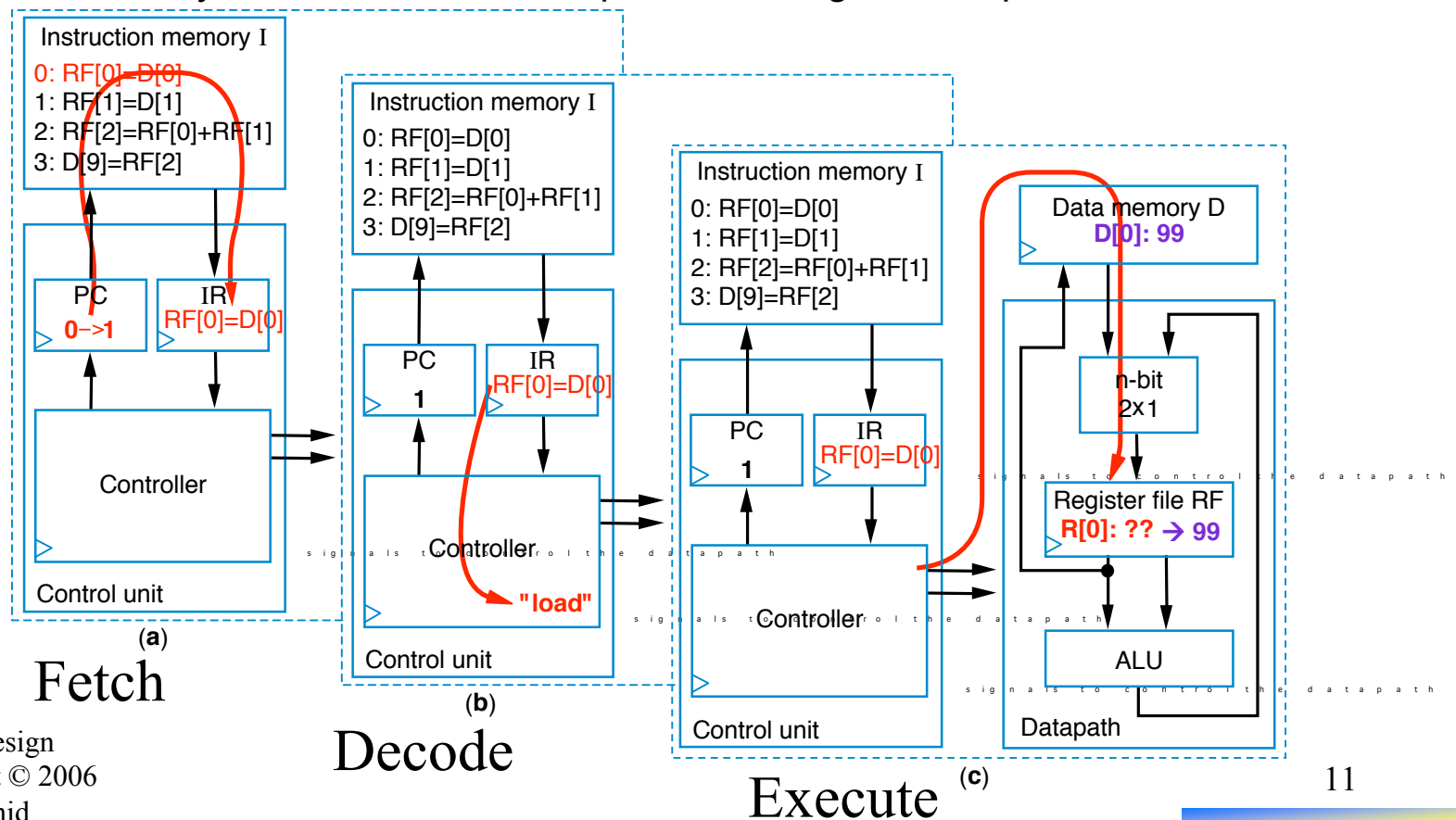- To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath




Basic Architecture – Control Unit

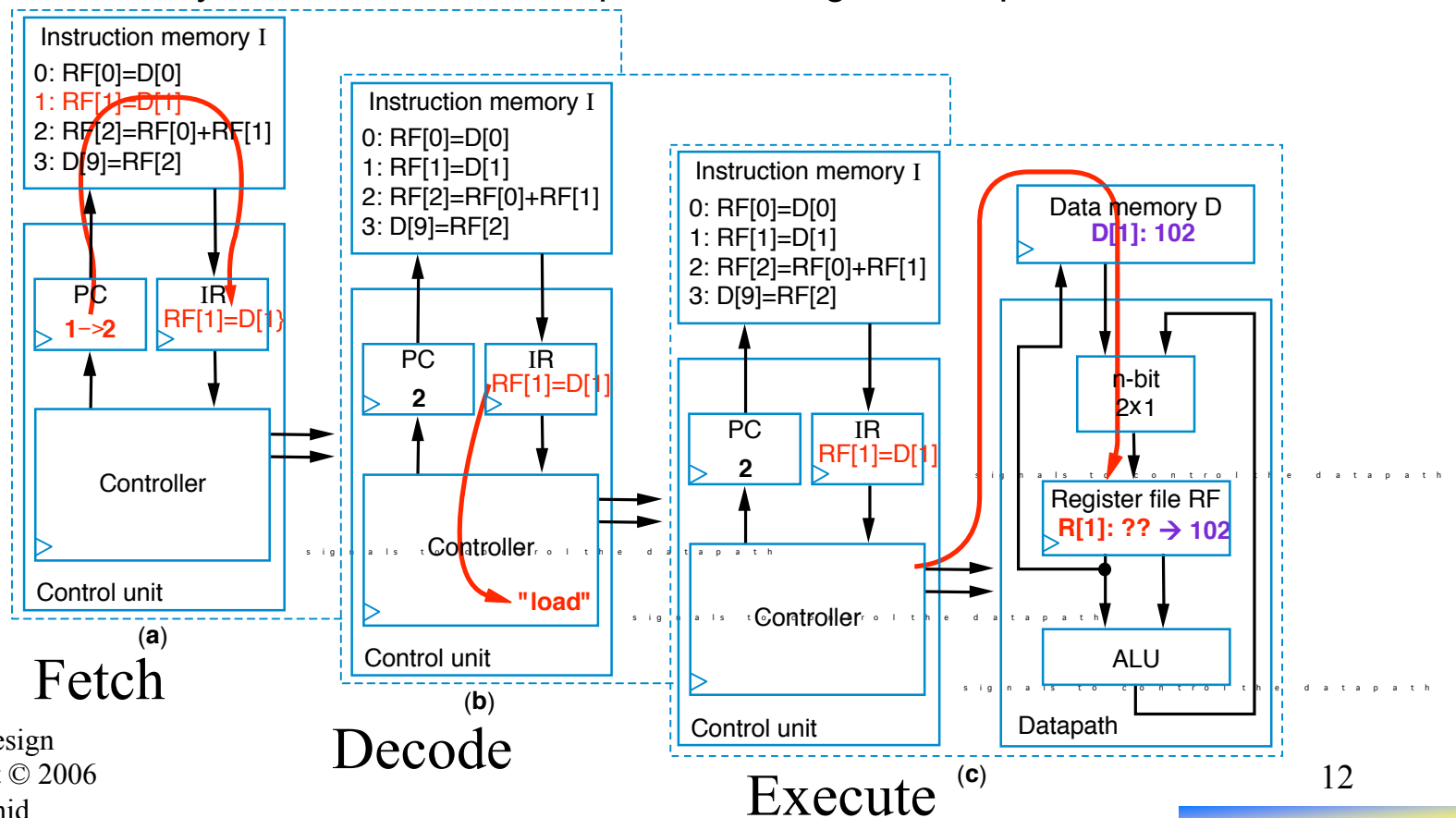- To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath




Basic Architecture – Control Unit

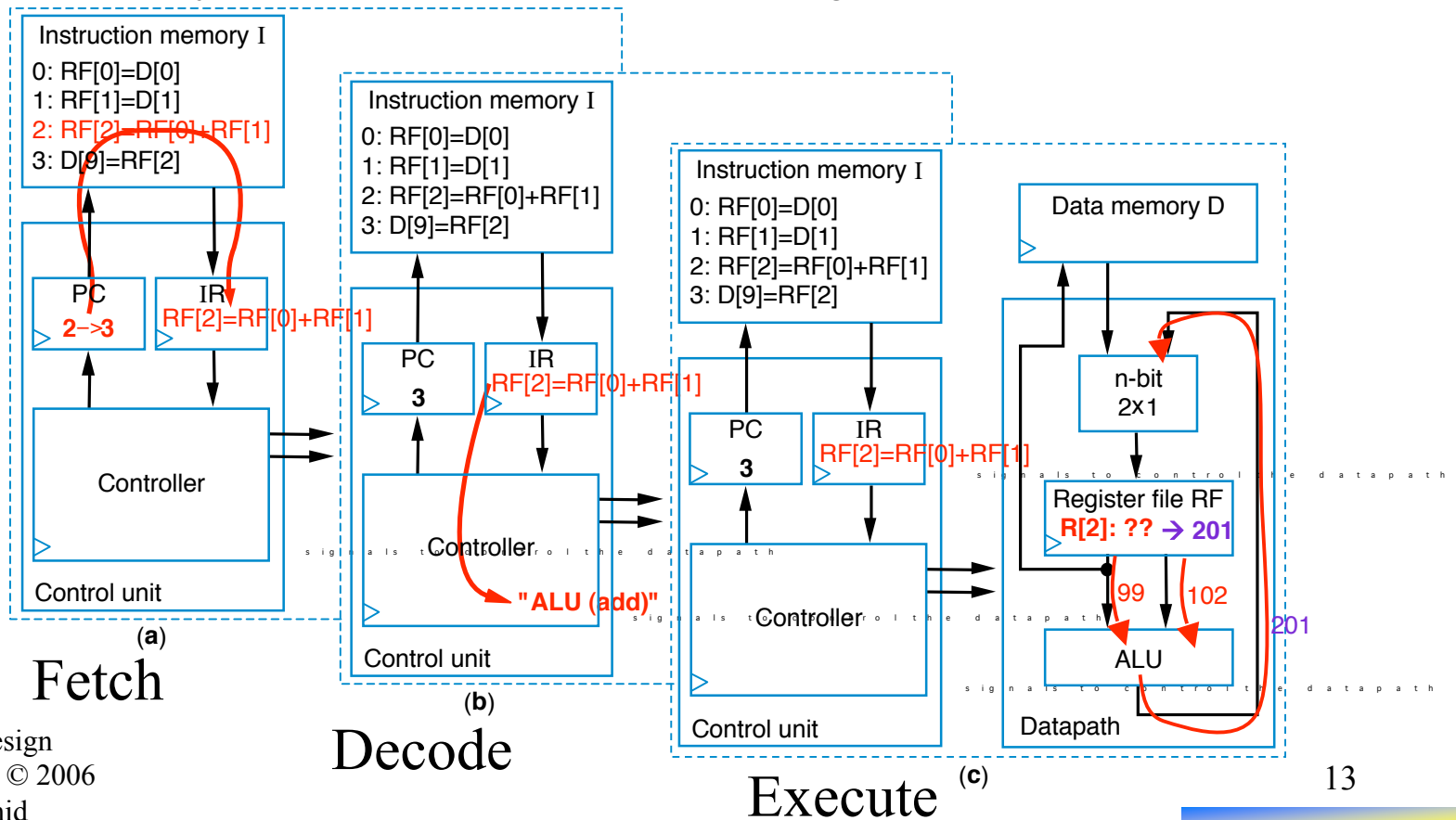- To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath



Basic Architecture – Control Unit


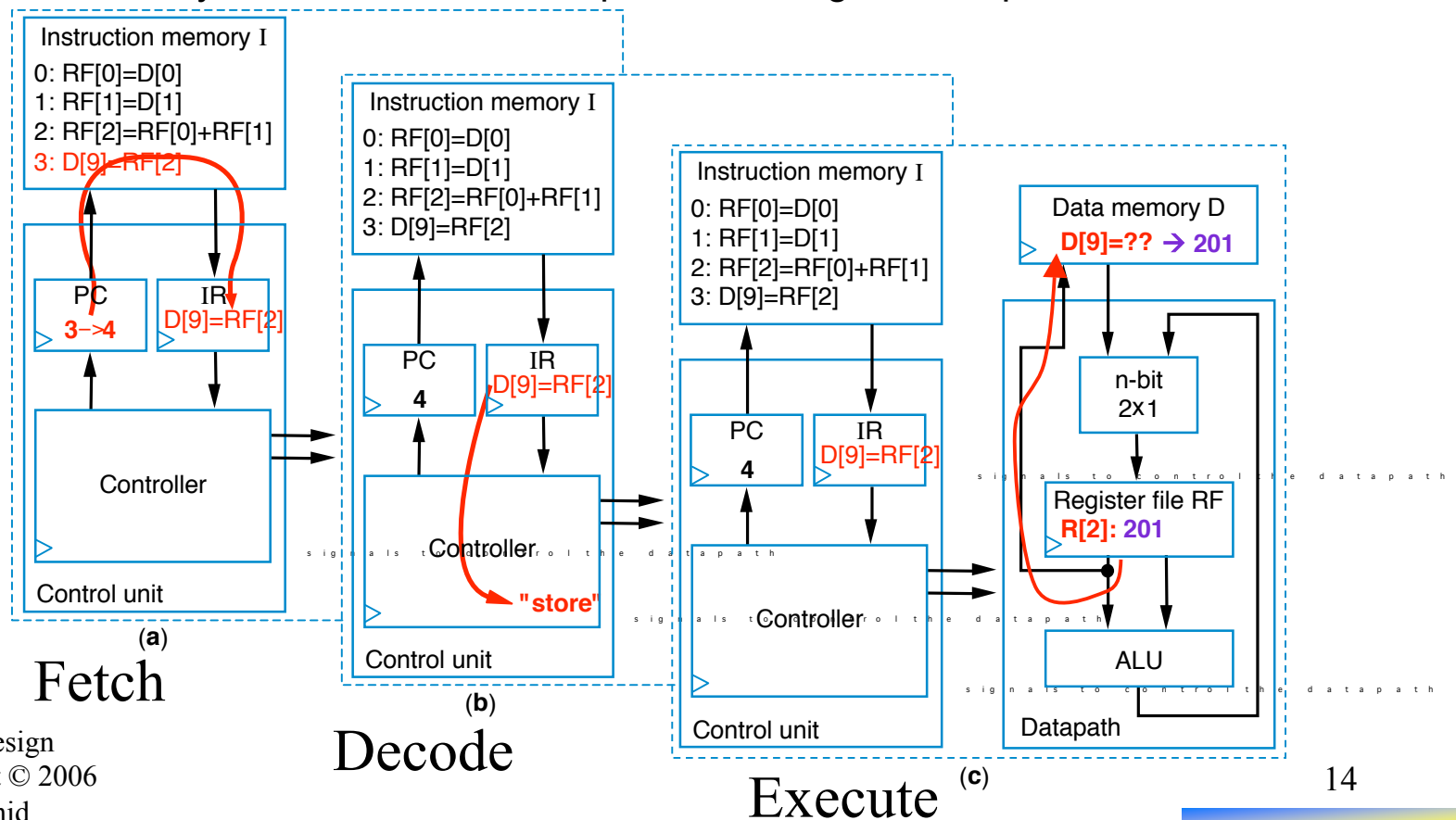
- To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath



Basic Architecture – Control Unit

To summarize, the control unit processes each instruction in three stages:

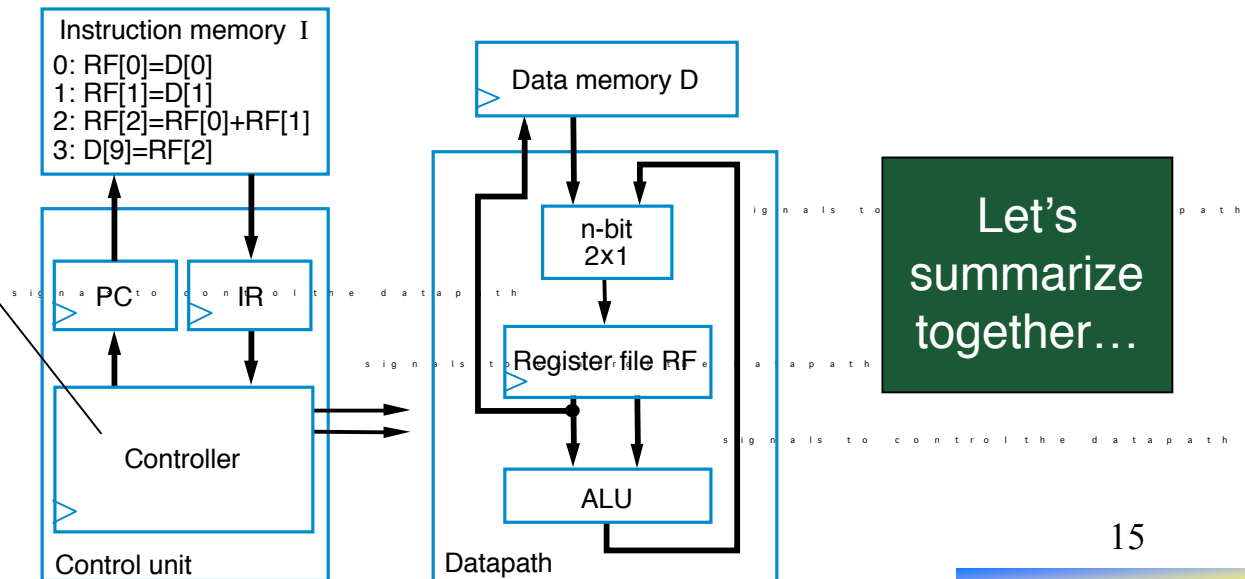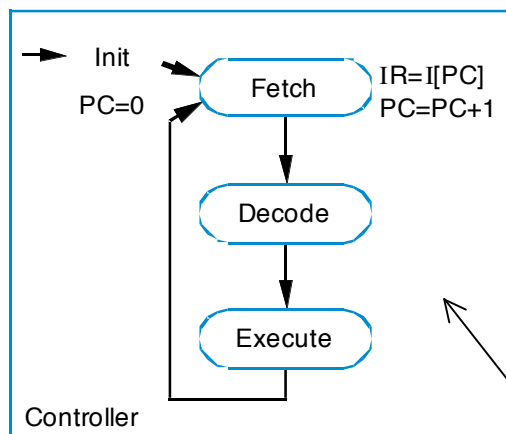1. first *fetching* the instruction by loading the current instruction into *IR* and incrementing the *PC* for the next fetch,
2. next *decoding* the instruction to determine its operation, and
3. finally *executing* the operation by setting the appropriate control lines for the datapath, if applicable. If the operation is a datapath operation, the operation may be one of three possible types:
 - (a) *loading* a data memory location into a register file location,
 - (b) transforming data using an *ALU* operation on register file locations and writing results back to a register file location, or
 - (c) *storing* a register file location into a data memory location.



Creating a Sequence of Instructions

- **Q:** Create sequence of instructions to compute $D[3] = D[0] + D[1] + D[2]$ on earlier-introduced processor
- **A1:** One possible sequence
 - First load data memory locations into register file
 - $R[3] = D[0]$
 - $R[4] = D[1]$
 - $R[2] = D[2]$

(Note arbitrary register locations)
 - Next, perform the additions
 - $R[1] = R[3] + R[4]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$
- **A2:** Alternative sequence
 - First load $D[0]$ and $D[1]$ and add them
 - $R[1] = D[0]$
 - $R[2] = D[1]$
 - $R[1] = R[1] + R[2]$
 - Next, load $D[2]$ and add
 - $R[2] = D[2]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$



Exercise: Creating Instruction Sequences



Q1: $D[8] = D[8] + RF[1] + RF[4]$


Let's do 1 more example...

Q2: $RF[2] = RF[1]$

One more example...

- $R2 = R3 \parallel R3 = R2$ (swap) -- Thoughts?
 - MOV d(x), R2
 - MOV d(y), R3
 - MOV R2, d(y)
 - MOV R2, d(x)

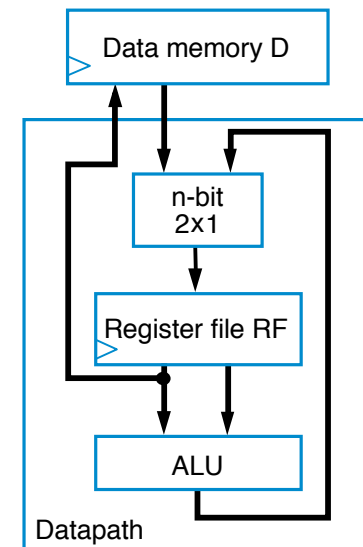- Could do in 3 ... but only with added functionality:
 - How?



Three-Instruction Programmable Processor

- Instruction Set – List of allowable instructions and their representation in memory, e.g.,

– Load instruction	0000	$r_3 r_2 r_1 r_0$	$d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
– Store instruction	0001	$r_3 r_2 r_1 r_0$	$d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
– Add instruction	0010	$ra_3 ra_2 ra_1 ra_0$	$rb_3 rb_2 rb_1 rb_0$ $rc_3 rc_2 rc_1 rc_0$

Desired program

0: RF[0]=D[0]
 1: RF[1]=D[1]
 2: RF[2]=RF[0]+RF[1]
 3: D[9]=RF[2]

Instruction memory		I
0:	0000 0000	00000000
1:	0000 0001	00000001
2:	0010 0010	0000 0001
3:	0001 0010	00001001

opcode operands

“Instruction” is an idea that helps abstract 1s, 0s, but still provides info. about HW

Instructions in 0s and 1s
 – *machine code*



Program for Three-Instruction Processor

Desired program



- 0: RF[0]=D[0]
- 1: RF[1]=D[1]
- 2: RF[2]=RF[0]+RF[1]
- 3: D[9]=RF[2]

Instruction memory I

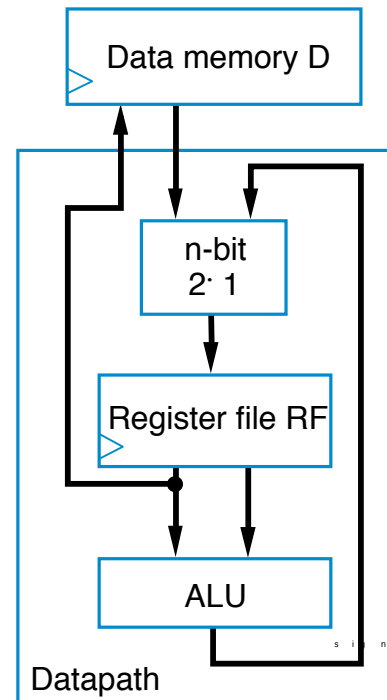 - 0: 0000 0000 00000000
- 1: 0000 0001 00000001
- 2: 0010 0010 0000 0001
- 3: 0001 0010 00001001

Computes
 $D[9]=D[0]+D[1]$

OPCODE =
sequence of 1s, 0s
that's fed to
controller to tell
datapath what to
do



Program for Three-Instruction Processor

- Another example program in machine code
 - Compute $D[5] = D[5] + D[6] + D[7]$

```
0: 0000 0000 00000101 // RF[0] = D[5]
1: 0000 0001 00000110 // RF[1] = D[6]
2: 0000 0010 00000111 // RF[2] = D[7]
3: 0010 0000 0000 0001 // RF[0] = RF[0] + RF[1]
                        // which is D[5]+D[6]
4: 0010 0000 0000 0010 // RF[0] = RF[0] + RF[2]
                        // now D[5]+D[6]+D[7]
5: 0001 0000 00000101 // D[5] = RF[0]
```

–**Load** instruction—**0000** $r_3 r_2 r_1 r_0$ $d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$ signals to control the datapath

–**Store** instruction—**0001** $r_3 r_2 r_1 r_0$ $d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$

–**Add** instruction—**0010** $ra_3 ra_2 ra_1 ra_0$ $rb_3 rb_2 rb_1 rb_0$
 $rc_3 rc_2 rc_1 rc_0$



Assembly Code

- Machine code (0s and 1s) hard to work with
- Assembly code – Uses mnemonics
 - **Load** instruction—**MOV Ra, d**
 - specifies the operation $RF[a]=D[d]$. a must be 0,1, ..., or 15—so $R0$ means $RF[0]$, $R1$ means $RF[1]$, etc. d must be 0, 1, ..., 255
 - • **Store** instruction—**MOV d, Ra**
 - specifies the operation $D[d]=RF[a]$
 - • **Add** instruction—**ADD Ra, Rb, Rc**
 - specifies the operation $RF[a]=RF[b]+RF[c]$

“Instruction” is an idea that helps abstract 1s, 0s, but still provides info. about HW

Desired program

0: $RF[0]=D[0]$	0: 0000 0000 00000000	0: MOV R0, 0
1: $RF[1]=D[1]$	1: 0000 0001 00000001	1: MOV R1, 1
2: $RF[2]=RF[0]+RF[1]$	2: 0010 0010 0000 0001	2: ADD R2, R0, R1
3: $D[9]=RF[2]$	3: 0001 0010 00001001	3: MOV 9, R2

machine code

assembly code



Exercise: Creating Assembly Code

Q1: $D[8] = D[8] + RF[1] + RF[4]$

$RF[2] = RF[1] + RF[4]$

$RF[3] = D[8]$

$RF[2] = RF[2] + RF[3]$

$D[8] = RF[2]$


Q2: $RF[2] = RF[1]$

$RF[2] = RF[1] + 0$

MOV R1, 0??

Control-Unit and Datapath for Three-Instruction Processor

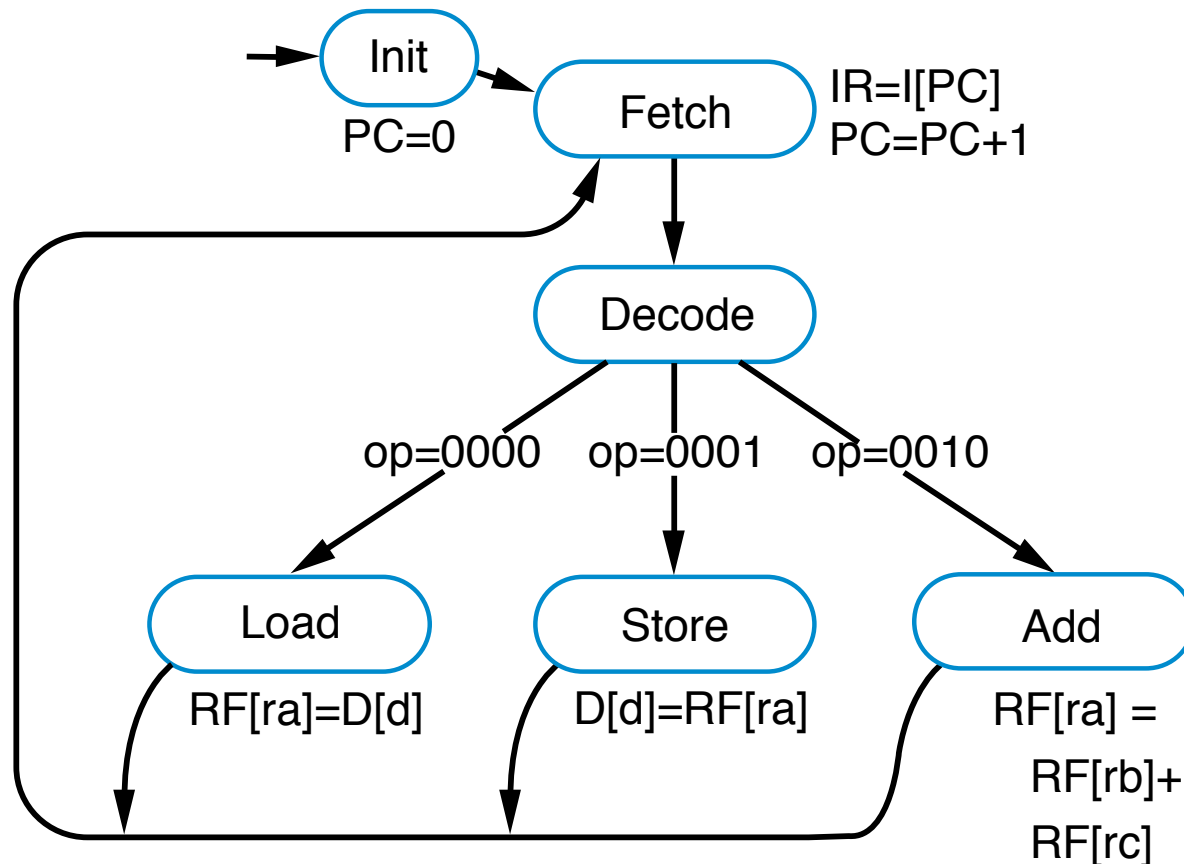
- To design the processor, we can begin with a high-level state machine description of the processor's behavior



Your 1st lab is about state machines.
They're important b/c they help to automate instruction processing.



Control-Unit and Datapath for Three-Instruction Processor

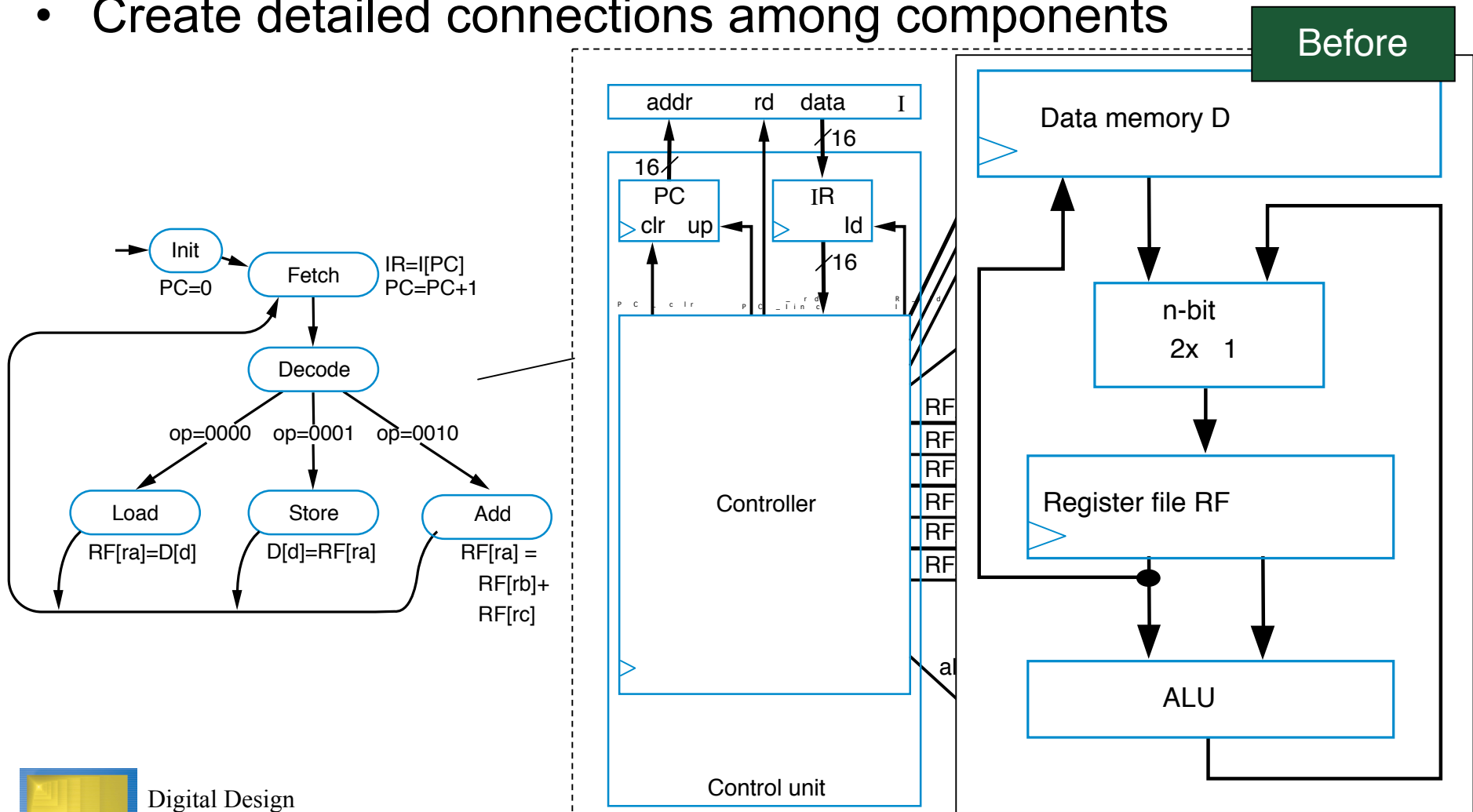- Create detailed connections among components



Control-Unit and Datapath for Three-Instruction Processor

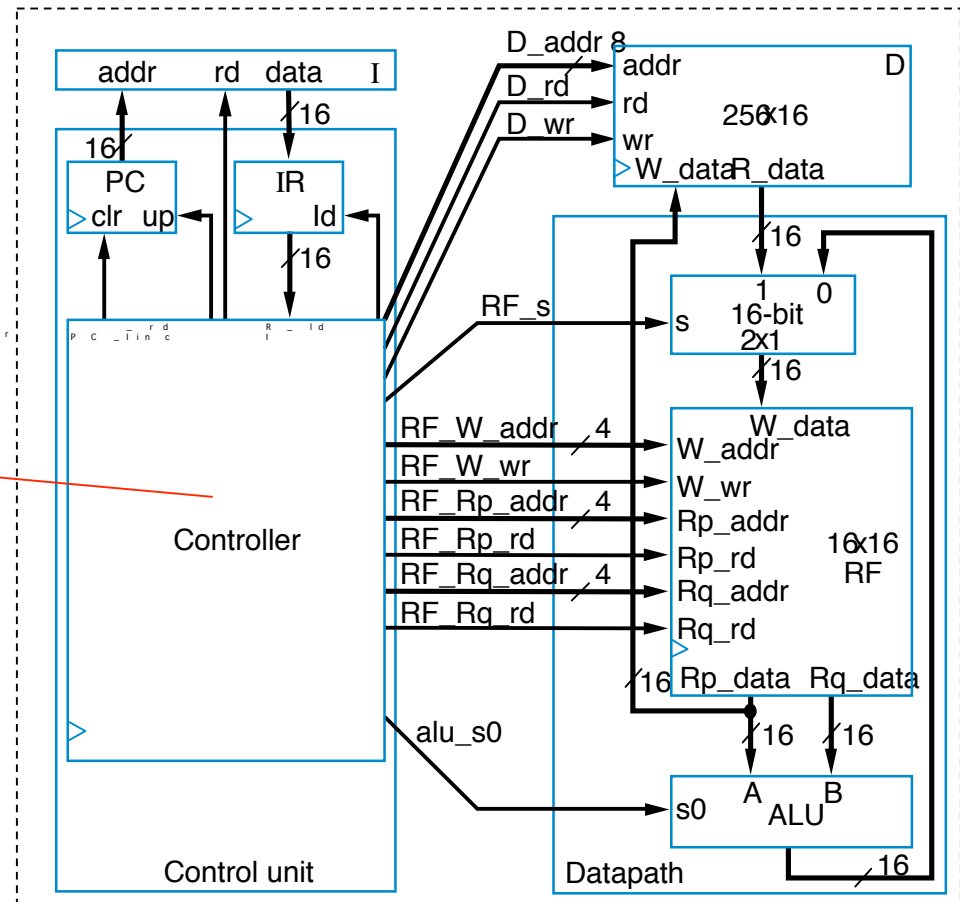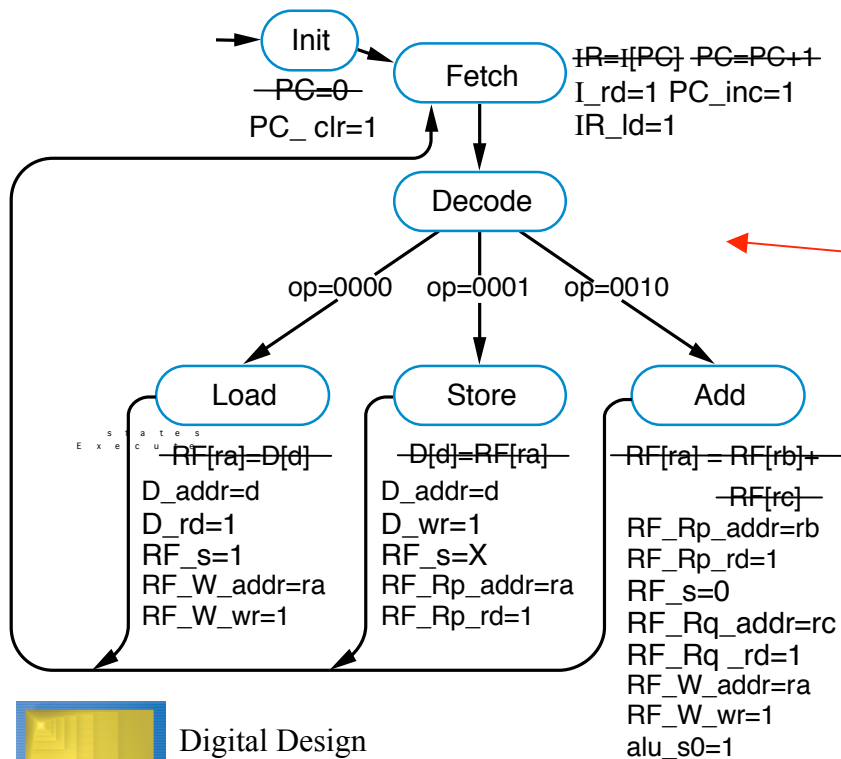- Convert high-level state machine description of entire processor to FSM description of controller that uses datapath and other components to achieve same behavior



Exercise: Understanding the Processor Design (1)

- Will the correct instruction be fetched if PC is incremented during the fetch cycle?
 - No, since PC will not be updated until the beginning of the next cycle
- While executing “**MOV R1, 3**”, what is the content of PC and IR at the end of the 1st cycle, 2nd cycle, 3rd cycle, etc.?
 - 1st cycle: PC = 0, IR = xxxx
 - 2nd cycle: PC = 1, IR = I[0]
 - 3rd cycle: PC = 1, IR = I[0]
- What if it takes more than 1 cycle for memory read?
 - Cannot decode until IR is loaded

Exercise: Understanding the Processor Design (2)

Q1: $D[8] = D[8] + RF[1] + RF[4]$

...

I[15]: Add R2, R1, R4

RF[1] = 4


I[16]: MOV R3, 8

RF[4] = 5

I[17]: Add R2, R2, R3

D[8] = 7

...

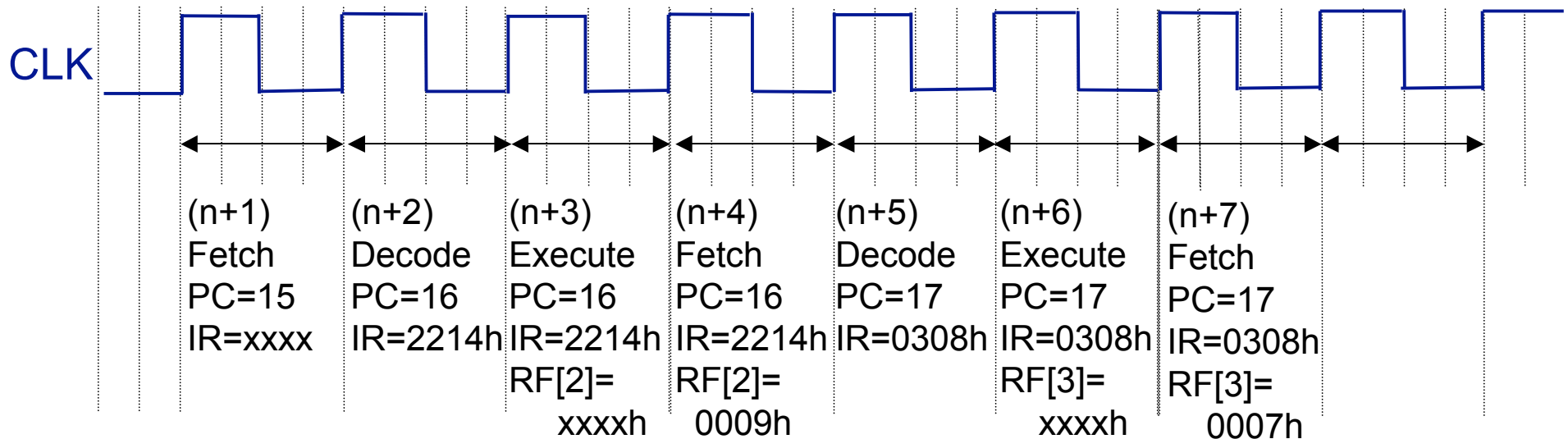

Exercise: Extending the Three-Instruction Processor

Add a instruction:



JMP: jump to a location specified by the 12-bit offset

RTL: $PC = PC + I[15:4]$

AS: JMP 3

MC: 1000000000000011

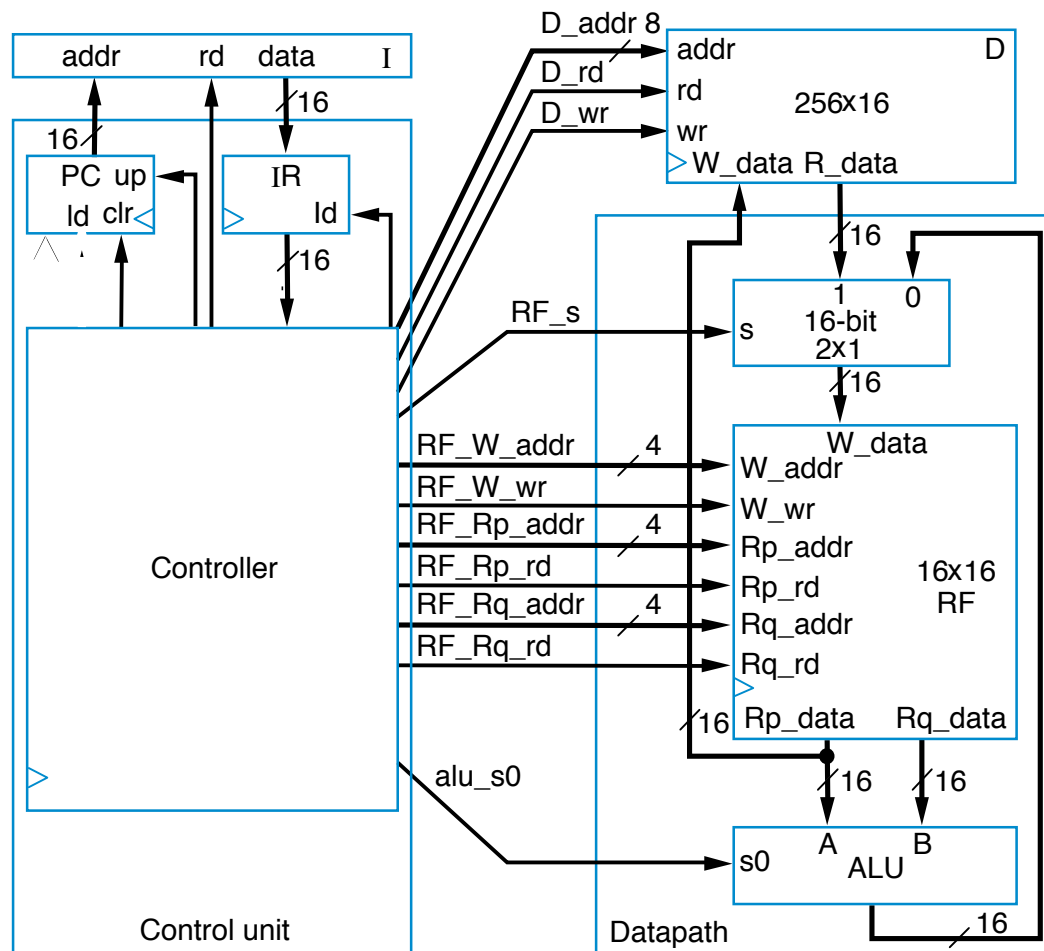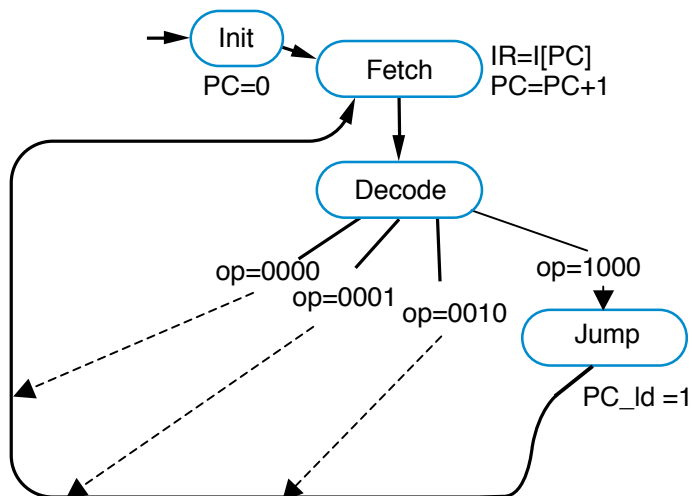Let's talk about A+B-1 a bit more...
Also, why is this instruction useful?



A Six-Instruction Programmable Processor

- Let's add three more instructions:
 - Load-constant** instruction—**0011** $r_3r_2r_1r_0$ $c_7c_6c_5c_4c_3c_2c_1c_0$
 - MOV Ra, #c**—specifies the operation $RF[a]=c$
 - Subtract** instruction—**0100** $ra_3ra_2ra_1ra_0$ $rb_3rb_2rb_1rb_0$ $rc_3rc_2rc_1rc_0$
 - SUB Ra, Rb, Rc**—specifies the operation $RF[a]=RF[b] - RF[c]$
 - Jump-if-zero** instruction—**0101** $ra_3ra_2ra_1ra_0$ $o_7o_6o_5o_4o_3o_2o_1o_0$
 - JMPZ Ra, offset**—specifies the operation $PC = PC + offset$ if $RF[a]$ is 0

TABLE 8.1 Six-instruction instruction set.

Instruction	Meaning
MOV Ra, d	$RF[a] = D[d]$
MOV d, Ra	$D[d] = RF[a]$
ADD Ra, Rb, Rc	$RF[a] = RF[b]+RF[c]$
MOV Ra, #C	$RF[a] = C$
SUB Ra, Rb, Rc	$RF[a] = RF[b]-RF[c]$
JMPZ Ra, offset	$PC=PC+offset$ if $RF[a]=0$

TABLE 8.2 Instruction opcodes.

Instruction	Opcode
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

