




# CSE 30321 Computer Architecture I

## Lecture 17 - Multi Cycle Machines

Michael Niemier  
Department of Computer Science and Engineering



## Single cycle Control Implementation

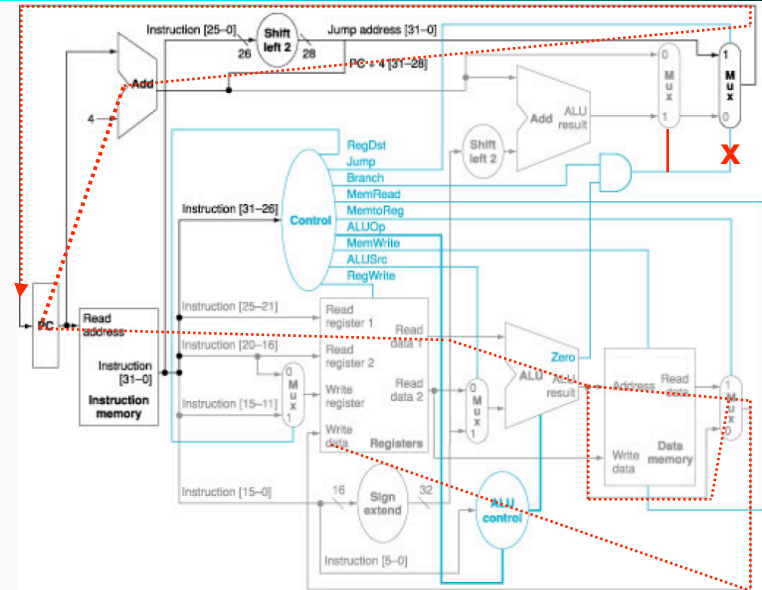

## How to Determine Cycle Length?



- Calculate cycle time assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)
  - R-type:  $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{RF}, \text{Add}\} = 6\text{ns}$
  - LW:  $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{mem} + \text{RF}, \text{Add}\} = 8\text{ns}$
  - SW:  $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{mem}, \text{Add}\} = 7\text{ns}$
  - BEQ:  $\max\{\text{mem} + \text{RF} + \text{ALU}, \max\{\text{Add}, \text{mem} + \text{Add}\}\} = 5\text{ns}$

## Some Observations



- Datapath:
  - How many times is each component used during an instruction execution?
  - Components can be combined by overlapping different instruction types
    - Register file by all instruction types
    - How about ALU?
    - How about sign-extension unit?
- Control:
  - For each type of instruction, identify control signals for each datapath component involved
  - Control signals are generated from the instruction opcode ( $\text{instr}[31:26]$ )

## Single-Cycle Implementation



- ❑ Single-cycle, fixed-length clock:
  - $CPI = 1$
  - Clock cycle = propagation delay of the longest datapath operations among all instruction types
  - Easy to implement
- ❑ Single-cycle, variable-length clock:
  - $CPI = 1$
  - Clock cycle =  $\sum (\%(\text{type-}i \text{ instructions}) * \text{propagation delay of the type-}i \text{ instruction datapath operations})$
  - better than the previous one but impractical to implement
- ❑ Disadvantages:
  - What if we have floating-point operations?
  - How about component usage?

## Multiple Cycle Alternative




- ❑ Break an instruction into smaller steps
- ❑ Execute each step in one cycle
- ❑ Execution sequence:
  - Balance the amount of work to be done, why?
  - Restrict each cycle to use only one major functional unit, why?
  - At the end of a cycle
    - store values for use in later cycles, why?
    - introduce additional “internal” registers
- ❑ The advantages:
  - Cycle time is much shorter
  - Different instructions take different number of cycles to complete
  - Allows a functional unit to be used more than once per instruction

## Multiple-Cycle Implementation



- ❑ Datapath
  - Component sharing: ALU, Instruction/Data memory
    - ALU used to compute address and to increment PC
    - Memory used for instruction and data
  - Additional elements: MUX's, Instr Register, Target Register
    - If a value needs to be alive during multiple cycles, it should stay unchanged during the whole time.
- ❑ Control:
  - Needed for each datapath element during each clock cycle

## What to be Done for Each Instruction?

 

- ❑ How many cycles should the above take?
- ❑ You are the architect so you decide!
- ❑ Less cycles => more to be done in one cycle

## Five Step Execution



### 1. Instruction Fetch (Ifetch):

- Fetch instruction at address (\$PC)
- Store the instruction in register **IR**
- Increment PC

### 2. Instruction Decode and Register Read (Decode):

- Decode the instruction type and read register
- Store the register contents in registers **A** and **B**
- Compute new PC address and store it in **ALUOut**

### 3. Execution, Memory Address Computation, or Branch Completion (Execute):

- Compute memory address (for LW and SW), or
- Perform R-type operation (for R-type instruction), or
- Update PC (for Branch and Jump)
- Store memory address or register operation result in **ALUOut**

## Five Step Execution (cont'd)



### 4. Memory Access or R-type instruction completion (MemRead/RegWrite/MemWrite):

- Read memory at address **ALUOut** and store it in **MDR**
- Write ALUOut content into register file, or
- Write memory at address ALUOut with the value in **B**

### 5. Write-back step (WrBack):

- Write the memory content read into register file

### □ Number of cycles for an instruction:

- R-type: 4
- lw: 5
- sw: 4
- Branch or Jump: 3

## Some Simple Questions



### □ How many cycles will it take to execute this code?

```
lw $t2, 0($t3)
lw $t3, 4($t3)
beq $t2, $t3, Label #assume branch is not taken
add $t5, $t2, $t3
sw $t5, 8($t3)
```

Label: ...

**5+5+3+4+4=21**

### □ What is being done during the 8th cycle of execution?

**Compute memory address: 4+\$t3**

### □ In what cycle does the actual addition of \$t2 and \$t3 takes place? **16**

## Step 1: Instruction Fetch



- Use PC to fetch instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- How about express this in RTL?

**IR=Mem[PC], PC=PC+4**

- What is the advantage of updating the PC now?
- Basic principle: do it ASAP!

## Step 2: Decode and Register Read



- ❑ Read registers *rs* and *rt* in case we need them
- ❑ Compute the branch address in case the instruction is a branch
- ❑ RTL:  

```
A = RF[IR[25:21]],  
B = RF[IR[20:16]],  
ALUOut = PC + (sign-extend(IR[15:0])) << 2
```
- ❑ Did we set any control lines based on the instruction type?

## Step 3 Execute (Instruction Dependent)



- ❑ ALU is performing one of three functions, based on instruction type
- ❑ RTL
  - Memory Reference:  

```
ALUOut = A + sign_ext(IR[15:0]);
```
  - R-type:  

```
ALUOut = A op B;
```
  - Branch:  

```
if (A=B) then (PC = ALUOut);
```

## Step 4 RegWrite/MemRead



- ❑ Loads and stores access memory

```
MDR = Mem[ALUOut];  
or  
Mem[ALUOut] = B;
```

- ❑ R-type instructions finish

```
RF[IR[15:11]] = ALUOut;
```

## Step 5: Write-Back



- ❑ Which type of instruction needs this?

- ❑ RTL

```
RF[IR[20:16]] = MDR;
```

- ❑ What about all the other instructions?

## RTL Description: Put All Together (1)



**Ifetch:** -> Decode,  
 $IR = Mem[PC], PC = PC + 4;$

**Decode:** ->Execute,  
 $A = RF[IR[25:21]], B = RF[IR[20:16]],$   
 $ALUOut = PC + Sign\_Ext(IR[15:0]) \ll 2;$

**Execute:**  
 if (opcode=lw) or (opcode=sw) then -> MRead/RegWrite,  
 $ALUOut = A + Sign\_Ext(IR[15:0]);$   
 if (opcode="R-type") then -> MRead/RegWrite,  
 $ALUOut = A \text{ op } B;$   
 if (opcode=branch) then -> Ifetch,  
 if (A=B) then  $PC = ALUOut;$   
 if (opcode=jump) then -> Ifetch,  
 $PC = PC[31:28] \parallel IR[25:0] \parallel 00;$

## RTL Description: Put All Together (2)



**MRead/RegWrite:**  
 if (opcode=lw) then -> WriteBack,  
 $MDR = Mem[ALUOut];$   
 if (opcode=sw) then -> Ifetch,  
 $Mem[ALUOut] = MDR;$   
 $RF[IR[15:11]] = ALUOut, \rightarrow \text{Ifetch};$


**WriteBack:**  
 $Mem[ALUOut] = MDR, \rightarrow \text{Ifetch};$

## Execution Sequence Summary



Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR = Mem[PC], PC = PC + 4$			
Instruction decode/register fetch	$A = RF[IR[25:21]], B = RF[IR[20:16]], ALUOut = PC + (\text{sign-extend}(IR[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut = A \text{ op } B$	$ALUOut = A + \text{sign-extend}(IR[15:0])$	if (A=B) then $PC = ALUOut$	$PC = PC[31:28] \parallel (IR[25:0] \ll 2)$
Memory access or R-type completion	$RF[IR[15:11]] = ALUOut$	Load: $MDR = Mem[ALUOut]$ or Store: $Mem[ALUOut] = B$		
Memory read completion		Load: $RF[IR[20:16]] = MDR$		

## A Multiple Cycle Datapath

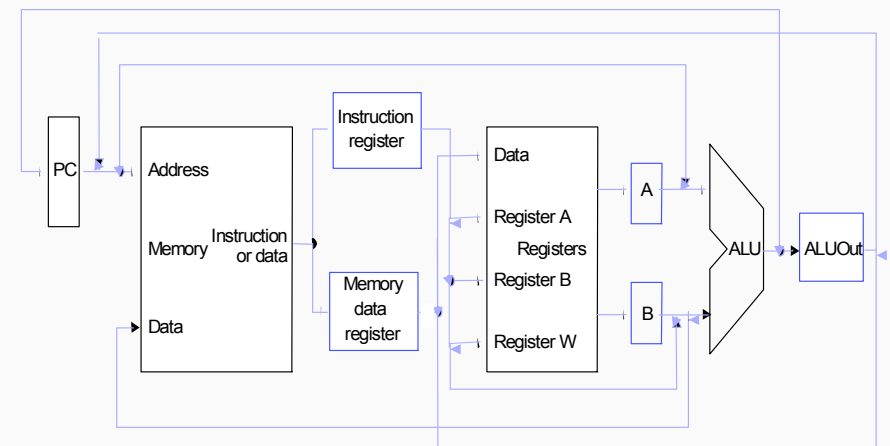


- Where do we need to insert mux's?
- Any other functional units?
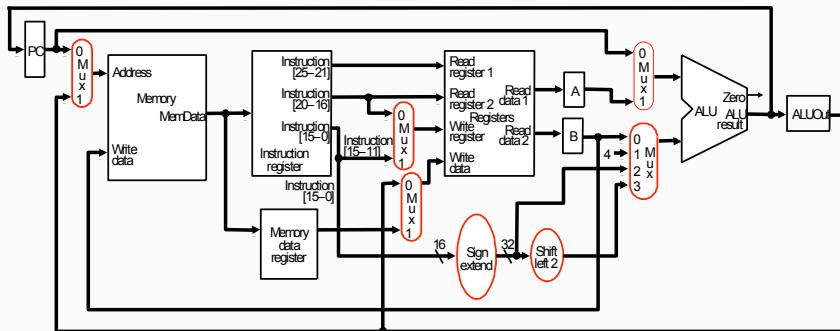
## Multiple Cycle Design



- ❑ Break up the instructions into steps, each step takes a cycle
  - balance the amount of work to be done
  - restrict each cycle to use only one major functional unit
- ❑ At the end of a cycle
  - store values for use in later cycles (easiest thing to do)
  - introduce additional “internal” registers




X.S. Hu

5-21
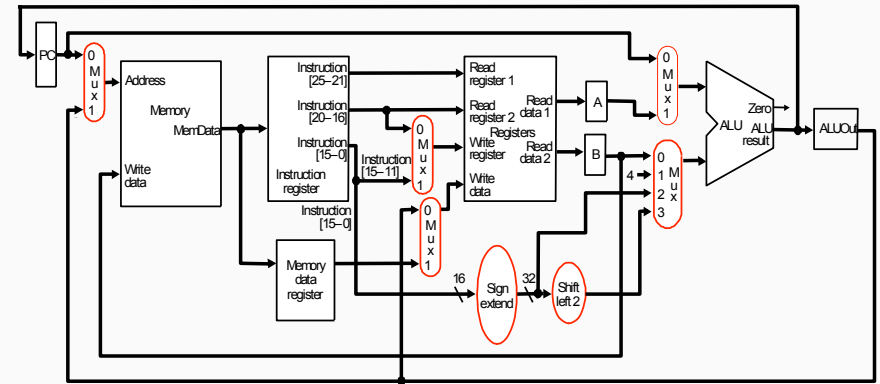
## Exercise: Add a New Instruction




- ❑ Let's try “jal”
- ❑ RTL:  $PC = (PC+4)[3:0] \parallel TargetAddr[25:0]$ ,  
 $RF[31] = PC + 4$ ;



X.S. Hu

5-22

## Control Signals

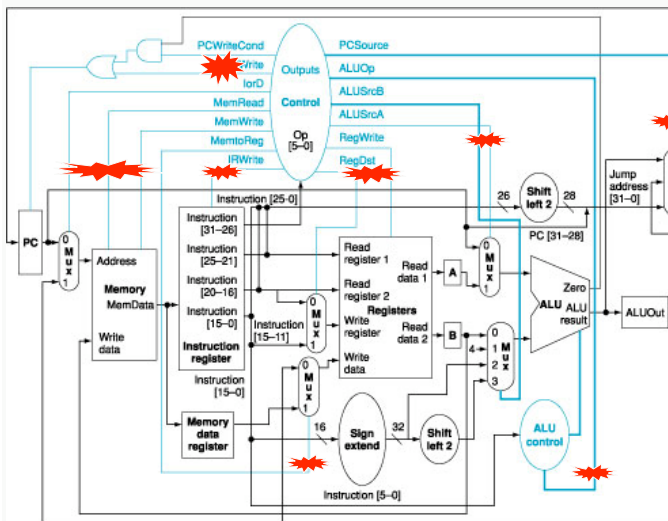

- ❑ **PC:** PCWrite, PCWriteCond, PCSource
- ❑ **Memory:** lorD, MemRead, MemWrite
- ❑ **Instruction Register:** IRWrite
- ❑ **Register File:** RegWrite, MemtoReg, RegDst
- ❑ **ALU:** ALUSrcA, ALUSrcB, ALUOp,

X.S. Hu

5-23

## Implementing the Control



- ❑ Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
- ❑ How to represent all the information?
  - finite state diagram
  - microprogramming
- ❑ Realization of a control unit is independent of the representation used
  - Control outputs: random logic, ROM, PLA
  - Next-state function: same as above or an explicit sequencer

X.S. Hu

5-24

# Finite State Diagram

