

DC and Transient Responses  
(i.e. delay)  
(some comments on power too!)

Michael Niemier

(Some slides based on lecture notes by David Harris)




# Outline

- Today...
    - 1st...
      - Quickly review material from last time
    - 2nd...
      - Briefly think about transistor operation in context of logic gates
    - 3rd...
      - Use basic logic gates to study trends relating to power & delay in context of device scaling
-

 
# MOSFET cross section...

With applied  $V_{gs}$ ,  
depletion region  
forms



 
# Review: MOS Capacitor

- Gate and body form MOS capacitor
- Operating modes



 
# Review: nMOS Cutoff

- No channel formed, so no current flows
- $I_{ds} = 0$



 
# Review: nMOS Linear

- Channel forms
- Current flows from d to s
  - $e^-$  from s to d
- $I_{ds}$  increases with  $V_{ds}$
- Similar to linear resistor



$$V_{gs} > V_t$$

$$V_{ds} = 0, \text{ no current}$$

 


$$V_{gs} > V_t$$

$$V_{ds} > 0, \text{ but } < (V_{gs} - V_t)$$

(current flows)
 
# Review: nMOS Saturation

- Channel pinches off
- $I_{ds}$  independent of  $V_{ds}$
- We say current saturates
- Similar to current source



$$V_{ds} > V_{gs} - V_t$$

Essentially, voltage difference over induced channel fixed at  $V_{gs} - V_t$   
(current flows, but saturates)  
(or  $i_{ds}$  no longer a function of  $V_{ds}$ )

# nMOS I-V Summary

- *Shockley* 1<sup>st</sup> order transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} \left( V_{gs} - V_t \right)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

---




**We'll start by considering logic gates in the context of transistor currents...**

**(for CMOS-based circuits...)**

---

# CMOS Gate Design

- 4-input CMOS NOR gate

 


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

(2-input NOR  
for reference)
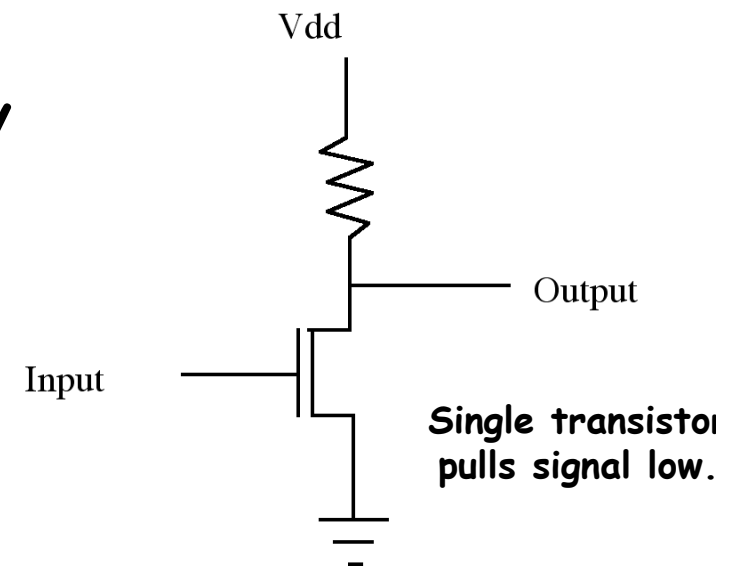
# Why CMOS?

- High noise margins:
  - Voltage swing  $\sim$  = supply voltage
- No direct path between supply and ground rails under steady-state operating conditions
  - (I.e. when input and outputs remain constant)
  - Absence of current flow = no static power
    - But this isn't exactly true as we'll see...
- All early Intel microprocessors NMOS only
  - (see NMOS inverter at right)
- Hard to achieve 0 static power
  - Put firm upper bound on # of gates
  - Necessitated move to CMOS in 1980s




# 1st, DC Response

- DC Response:  $V_{out}$  vs.  $V_{in}$  for a gate

- Ex: Inverter

- When  $V_{in} = 0$   $\rightarrow V_{out} = V_{DD}$
- When  $V_{in} = V_{DD}$   $\rightarrow V_{out} = 0$
- In between,  $V_{out}$  depends on transistor size and current
- Want:  $I_{dsn} = |I_{dsp}|$
- We could solve equations
- But graphical solution gives more insight

 

# Transistor Operation

- Current depends on region of transistor behavior
  - For what  $V_{in}$  and  $V_{out}$  are nMOS and pMOS in
    - Cutoff?
    - Linear?
    - Saturation?
-

# nMOS Operation

Recall...


Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$ Same	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

No Current

$$V_{ds} < V_{gs} - V_t$$

$$V_{ds} < V_{gs} - V_t$$

 In inverter context,  
what is  $V_{gs}$ ,  $V_{ds}$   
for NMOS device?




# nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


# nMOS Operation (in context of inverter input $V$ )

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 




# pMOS Operation (for reference)

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 
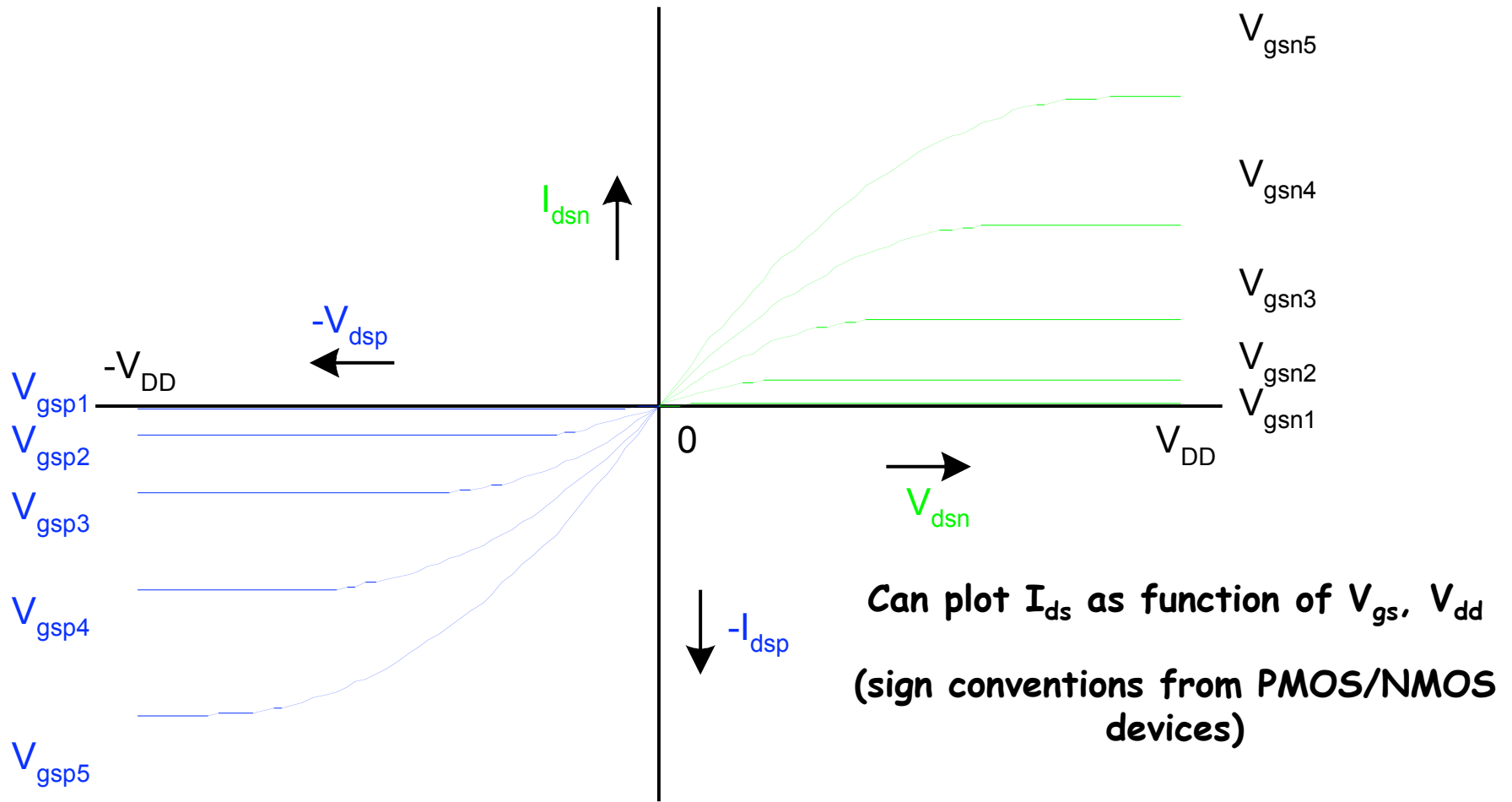
# I-V Characteristics


- Make pMOS is wider than nMOS such that  $\beta_n = \beta_p$



# Load Line Analysis



- For a given  $V_{in}$ :
  - Plot  $I_{dsn}$ ,  $I_{dsp}$  vs.  $V_{out}$
  - $V_{out}$  must be where |currents| are equal in  
(For DC operating point to be valid - consider graphical intersection of load lines...

i.e. current in pMOS > current in nMOS

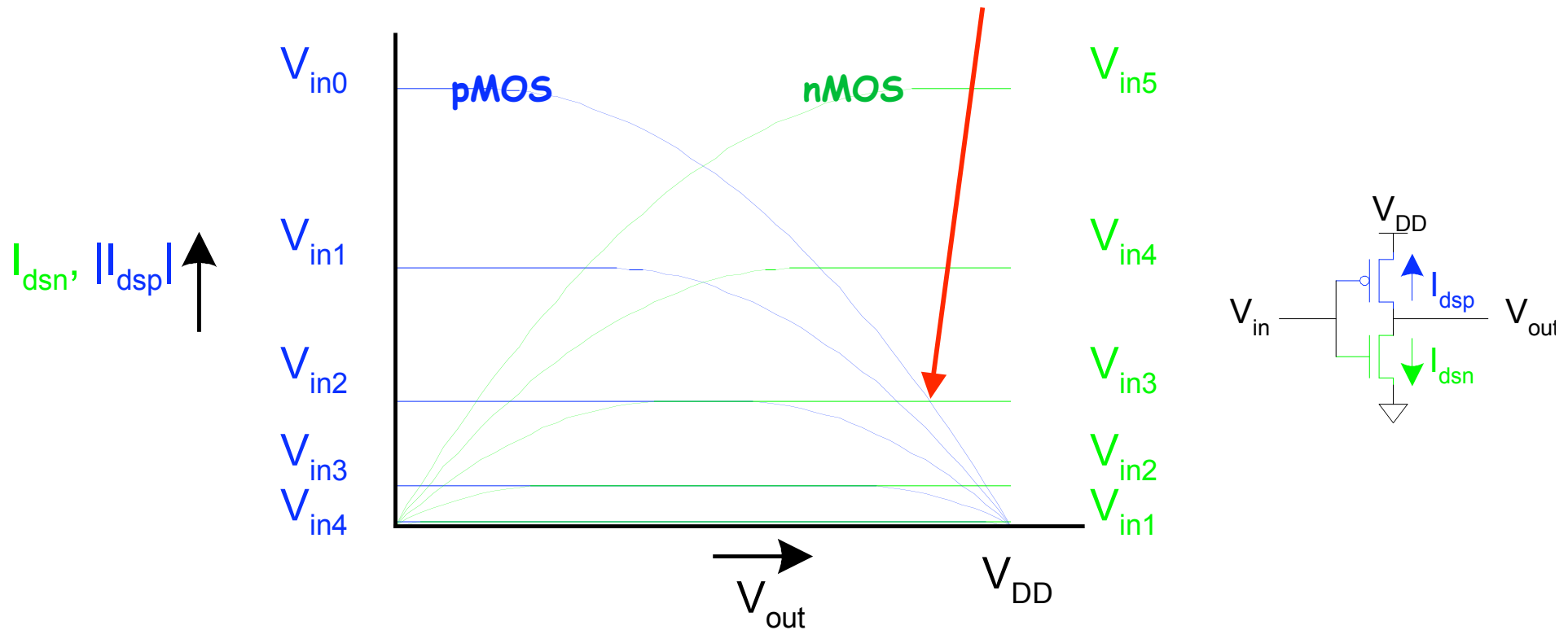
  
# DC Transfer Curve

- Transcribe points onto  $V_{in}$  vs.  $V_{out}$  plot




# Comments:

- All operating points are located near high or low output levels
  - The VTC of the inverter exhibits a very narrow transition zone
  - This results from high gain during the switching transient
    - (When both NMOS, PMOS are in saturation and on simultaneously)
    - (In this region, small change in the input voltage results in a large output variation)
-

# Operating Regions

- Revisit transistor operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 


***A few more interesting points...***

---
 
# Beta Ratio


- If  $\beta_p / \beta_n \neq 1$ , switching point will move from  $V_{DD}/2$
- Called *skewed gate*
- Other gates: collapse into equivalent inverter




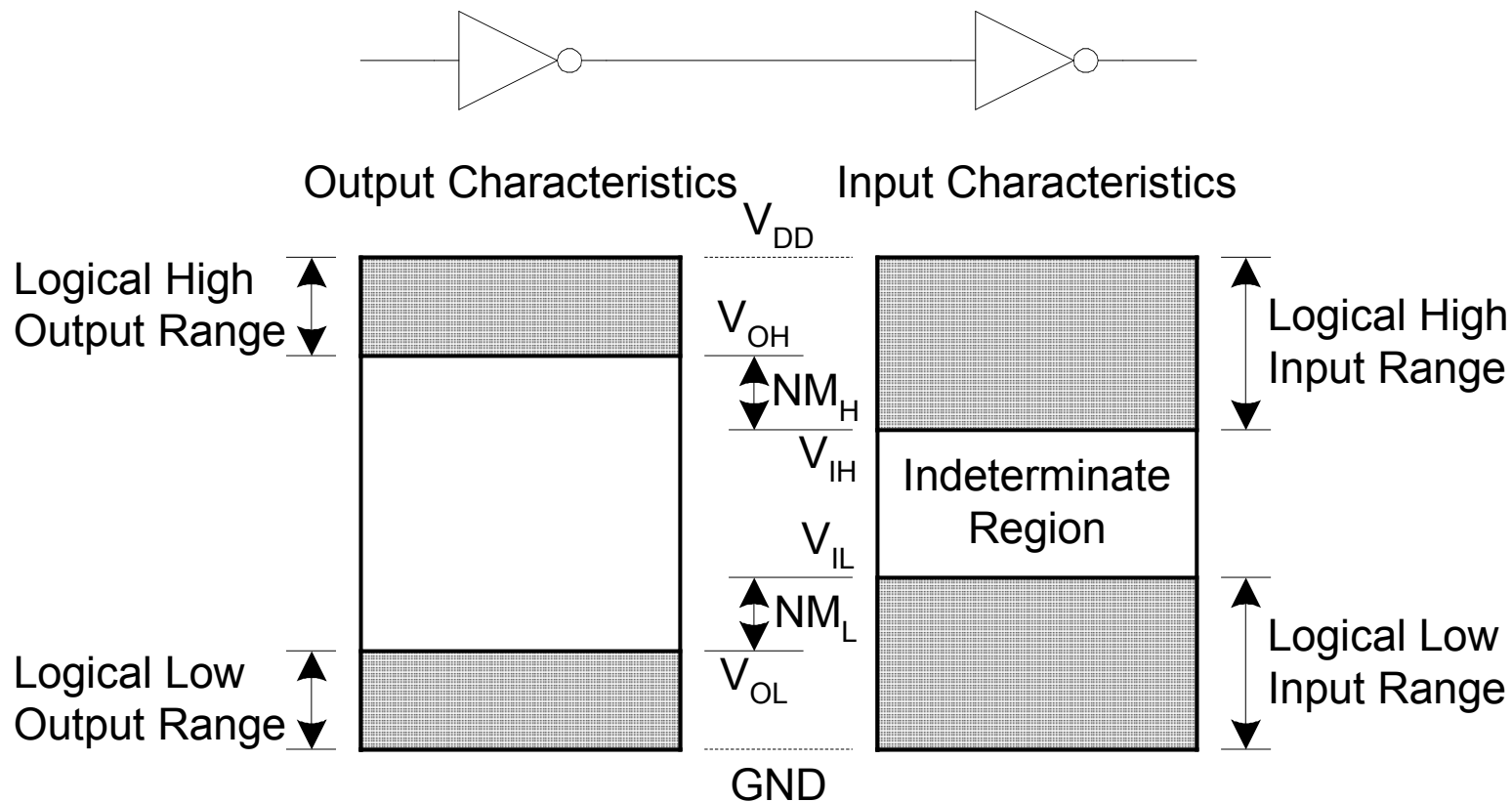
# Noise Margins


- How much noise can a gate input see before it does not recognize the input?



# Logic Levels

- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristic

Acceptable low input to get high output

 

Acceptable high input to get low output

# Supply voltage scaling

- As supply voltage scales down - which can be good as we'll see - can have problems
    - To a point ( $\sim 0.5V$ ), scaling  $V_{dd}$  improves gain
    - Beyond, DC characteristics become increasingly sensitive to variations in the device parameters
      - E.g. transistor threshold
    - Scaling supply voltages reduces signal swing
      - Makes design more sensitive to external noise sources that don't scale.
-

**Next, board discussion on  
transient response, power.**

---