

L07-L09 recap: Fundamental lesson(s)

- **Over the next 3 lectures (using the MIPS ISA as context) I'll explain:**
 - **How functions are treated and processed in assembly**
 - **How system calls are enabled in assembly**
 - **How exceptions are handled in assembly**
- **I'll also explain why it's important that register conventions be followed**

L07-L09 recap: Why it's important...

- **If you ever write a compiler or OS some day, you will need to be aware of, and code for all of the issues to be discussed over the next 3 lectures**
- **If you understand what architectural overhead may be associated with (compiled) procedure calls, you should be able to write much more efficient HLL code**


Lecture 10

The MIPS datapath


Suggested reading:
(HP Chapter 4.1 —4.4)

Processor components


Multicore processors and programming

 

Processor comparison

 

 Goal: describe the fundamental components required in a single core of a modern microprocessor as well as how they interact with each other, with main memory, and with external storage media.



Writing more efficient code



The right HW for the right application

```
for i=0; i<5; i++ {  
    a = (a*b) + c;  
}
```

```
MULT r1,r2,r3 # r1 ← r2*r3  
ADD r2,r1,r4  ↓ # r2 ← r1+r4
```

110011	000001	000010	000011
001110	000010	000001	000100

HLL code translation

Fundamental lesson(s)

- **Today we'll discuss what hardware is required to execute an instruction, as well as how to best “organize” it.**


Why it's important...

- **If you ever design the HW for a microprocessor, etc. you'll need to be aware of these types of issues**
- **Understanding organization – and how it impacts the delay of something like a memory reference - will make you a better programmer**
- **It is now more and more important to design HW/SW simultaneously**

The organization of a computer

Von Neumann Model:

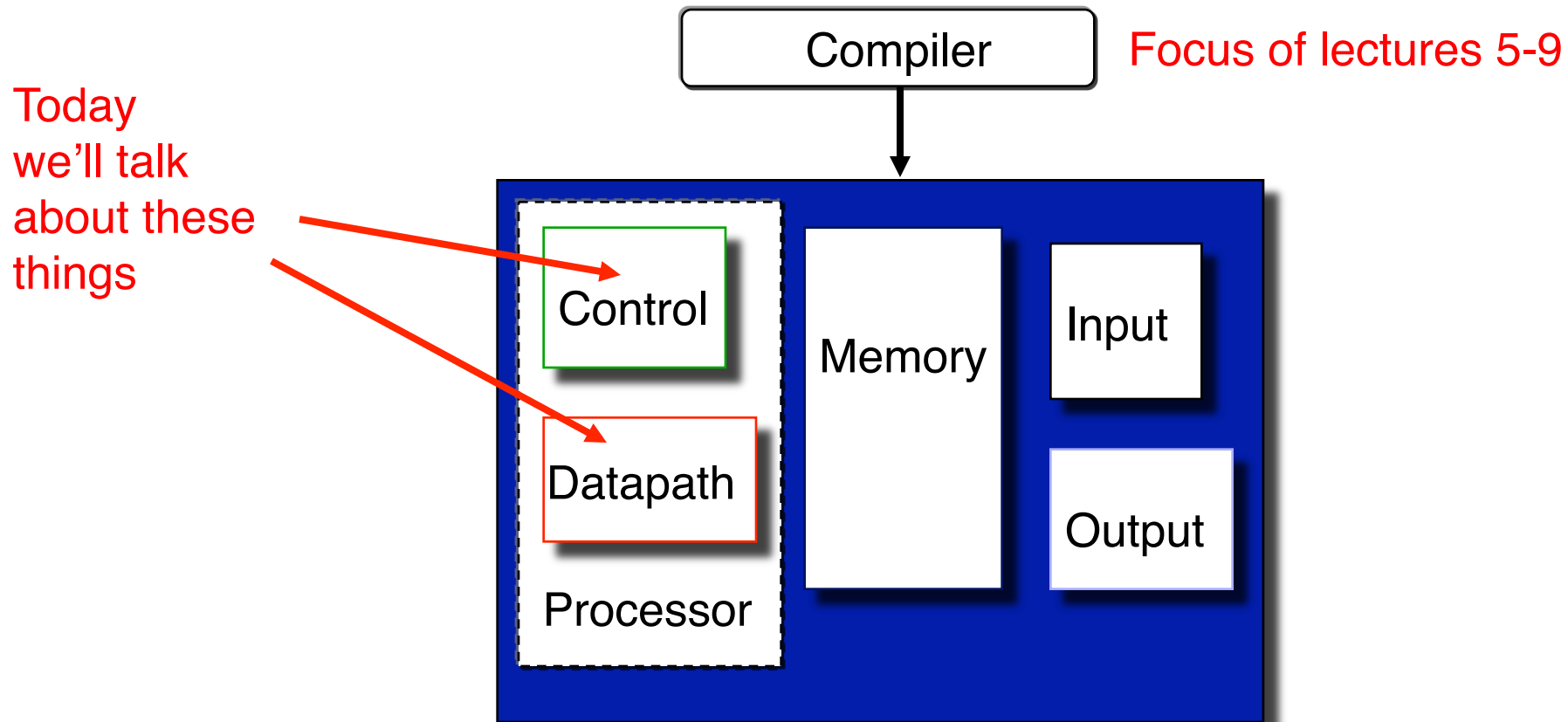- Stored-program machine instructions are represented as numbers
- Programs can be stored in memory to be read/written just like numbers.



Review: Functions of Each Component

- **Datapath: performs data manipulation operations**
 - arithmetic logic unit (ALU)
 - floating point unit (FPU)
- **Control: directs operation of other components**
 - finite state machines
 - micro-programming (to be discussed)
- **Memory: stores instructions and data**
 - random access v.s. sequential access
 - volatile v.s. non-volatile
 - RAMs (SRAM, DRAM), ROMs (PROM, EEPROM), disk
 - tradeoff between speed and cost/bit
- **Input/Output and I/O devices: interface to environment**
 - mouse, keyboard, display, device drivers

Let's “derive” the MIPS datapath:


- To simplify things a bit we'll just look at a few instructions:
 - memory-reference: **lw, sw**
 - arithmetic-logical: **add, sub, and, or, slt**
 - branching: **beq, j**

Very common instructions


- Organizational overview:

- fetch an instruction based on the content of PC
- decode the instruction
- fetch operands
 - (read one or two registers)
- execute
 - (effective address calculation/arithmetic-logical operations/comparison)
- store result
 - (write to memory / write to register / update PC)

 With Von Neumann, RISC model do similar things for each instruction



A Single Cycle Datapath

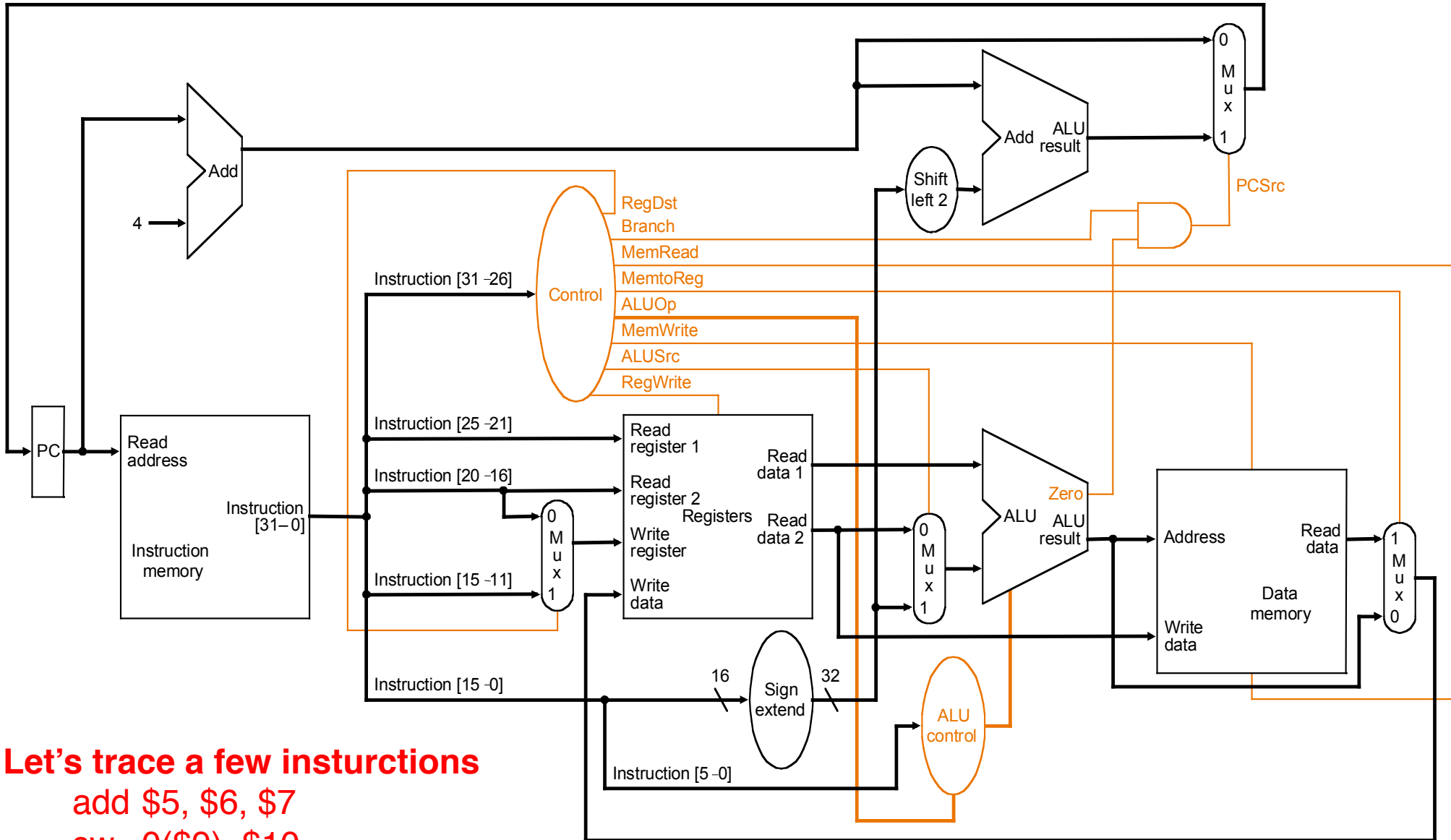

Let's trace a few instructions

- add \$5, \$6, \$7
- sw 0(\$9), \$10
- sub \$1, \$2, \$3
- lw \$11, 0(\$12)


PERFORMANCE

Single-Cycle Implementation

- **Single-cycle, fixed-length clock:**
 - **CPI = 1**
 - **Clock cycle = propagation delay of the longest datapath operations among all instruction types**
 - **Easy to implement**
- **How to determine cycle length?**
- **Calculate cycle time assuming negligible delays except:**
 - **memory (2ns), ALU and adders (2ns), register file access (1ns)**
 - **R-type: $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{RF}, \text{Add}\}$ = 6ns**
 - **LW: $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{mem} + \text{RF}, \text{Add}\}$ = 8ns**
 - **SW: $\max\{\text{mem} + \text{RF} + \text{ALU} + \text{mem}, \text{Add}\}$ = 7ns**
 - **BEQ: $\max\{\text{mem} + \text{RF} + \text{ALU}, \max\{\text{Add}, \text{mem} + \text{Add}\}\}$ = 5ns**

What is the CC time?

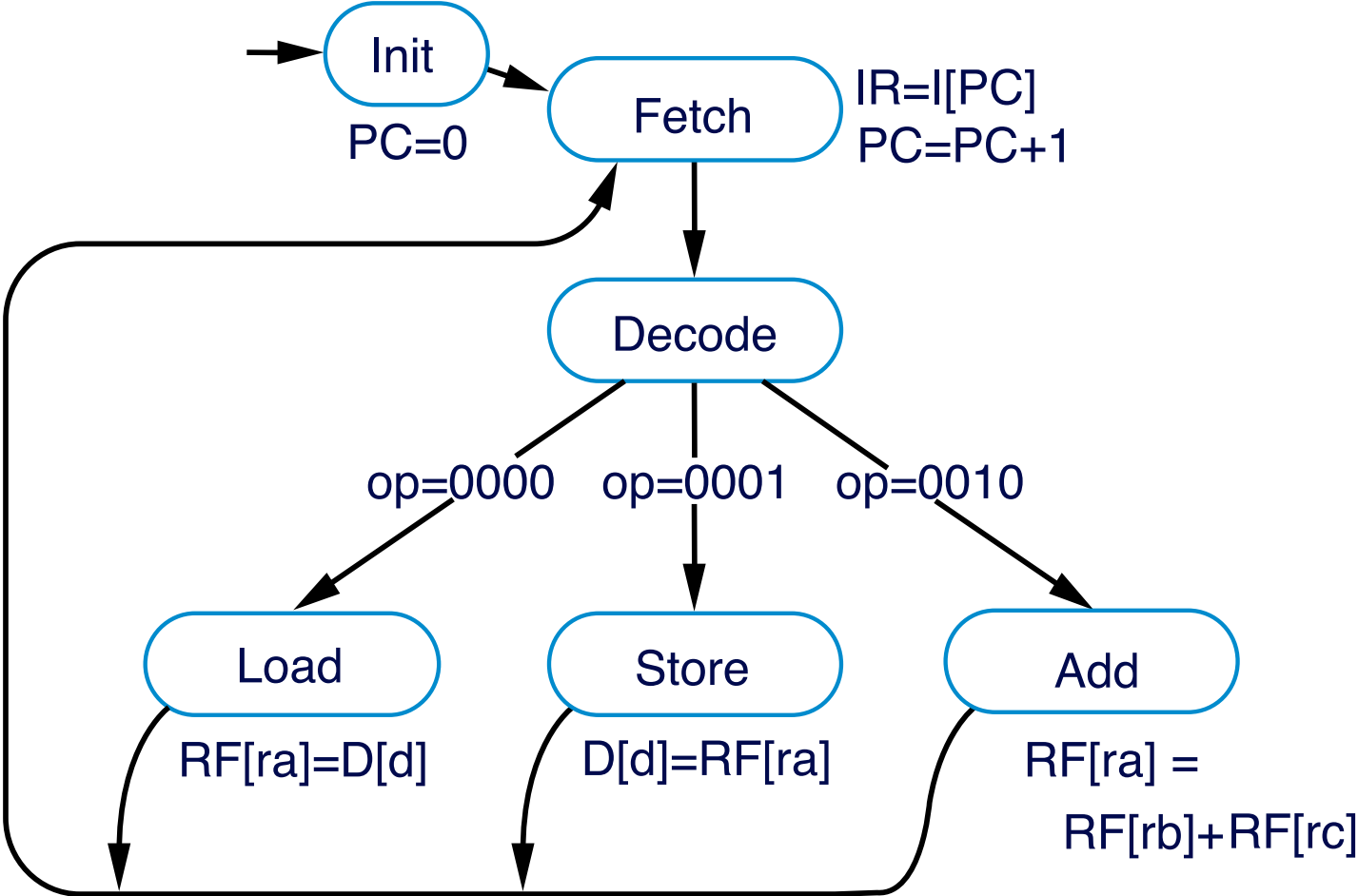
Before, spoke about “multi-cycle” datapath



The multi-cycle approach (& benefits):

- Break an instruction into smaller steps
- Execute each step in one cycle.
- Execution sequence:
 - Balance amount of work to be done
 - Restrict each cycle to use only one major functional unit
 - At the end of a cycle
 - Store values for use in later cycles
 - Introduce additional “internal” registers
- The advantages:
 - Cycle time much shorter
 - Diff. inst. take different # of cycles to complete
 - Functional unit used more than once per instruction

MIPS multi-cycle datapath

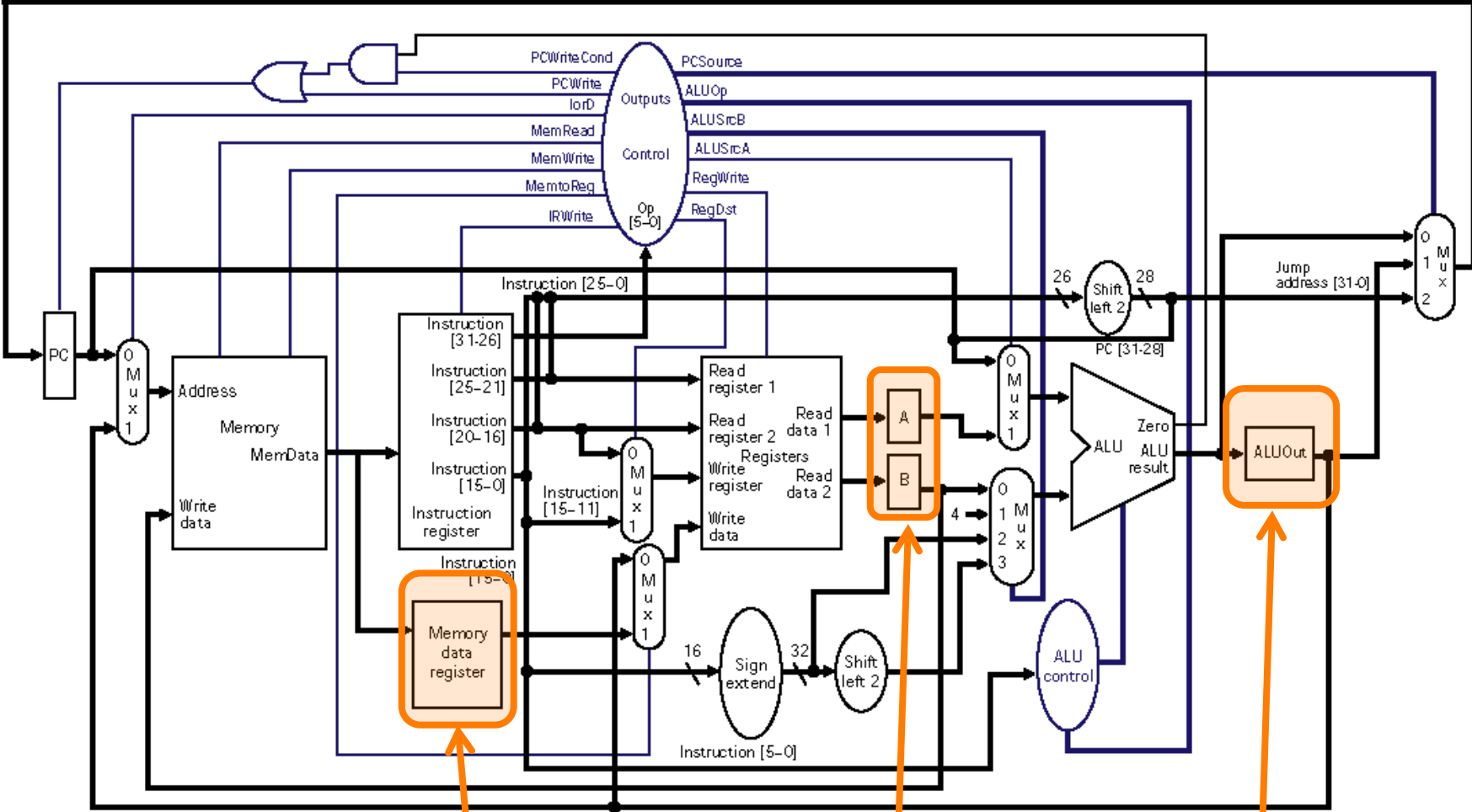

Note introduction of temporary storage registers

5 steps an instruction could take:

1. Instruction Fetch (Ifetch):

- Fetch instruction at address (\$PC)
- Store the instruction in register IR
- Increment PC

2. Instruction Decode and Register Read (Decode):

- Decode the instruction type and read register
- Store the register contents in registers A and B
- Compute new PC address and store it in ALUOut

3. Execution, Memory Address Computation, or Branch Completion (Execute):

- Compute memory address (for LW and SW), or
- Perform R-type operation (for R-type instruction), or
- Update PC (for Branch and Jump)
- Store memory address or register operation result in ALUOut

5 steps an instruction could take:

4. Memory Access or R-type instruction completion

(MemRead/RegWrite/MemWrite):

- Read memory at address **ALUOut** and store it in **MDR**
- Write **ALUOut** content into register file, or
- Write memory at address **ALUOut** with the value in **B**

5. Write-back step (WrBack):

- Write the memory content read into register file

Number of cycles for an instruction:

- R-type: 4
- lw: 5
- sw: 4
- Branch or Jump: 3

Instruction execution (summary):

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR = Mem[PC],$ $PC = PC + 4$			
Instruction decode/register fetch	$A = RF [IR[25:21]],$ $B = RF [IR[20:16]],$ $ALUOut = PC + (\text{sign-extend} (IR[1:-0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut = A \text{ op } B$	$ALUOut = A + \text{sign-extend} (IR[15:0])$	if (A =B) then $PC = ALUOut$	$PC = PC [31:28] (IR[25:0] \ll 2)$
Memory access or R-type completion	$RF [IR[15:11]] = ALUOut$	Load: $MDR = Mem[ALUOut]$ or Store: $Mem[ALUOut] = B$		
Memory read completion		Load: $RF[IR[20:16]] = MDR$		

Some questions:

- How many cycles will it take to execute this code?

lw \$t2, 0(\$t3)

lw \$t3, 4(\$t3)

beq \$t2, \$t3, Label #assume branch is not taken

add \$t5, \$t2, \$t3

sw \$t5, 8(\$t3)

Label: ...

$$5+5+3+4+4=21$$

- What is being done during the 8th cycle of execution?

Compute memory address: 4 + content of \$t3


- In what cycle does the addition of \$t2 and \$t3 takes place?

16

- How would performance compare if multi-cycle clock period is 2 ns and cycle cycle period is 10 ns?


(21 CCs x 2 ns) vs. (5 CCs x 10 ns): 42 ns vs. 50 ns

Foreshadowing: pipelines

 

Note: Some extra HW needed.

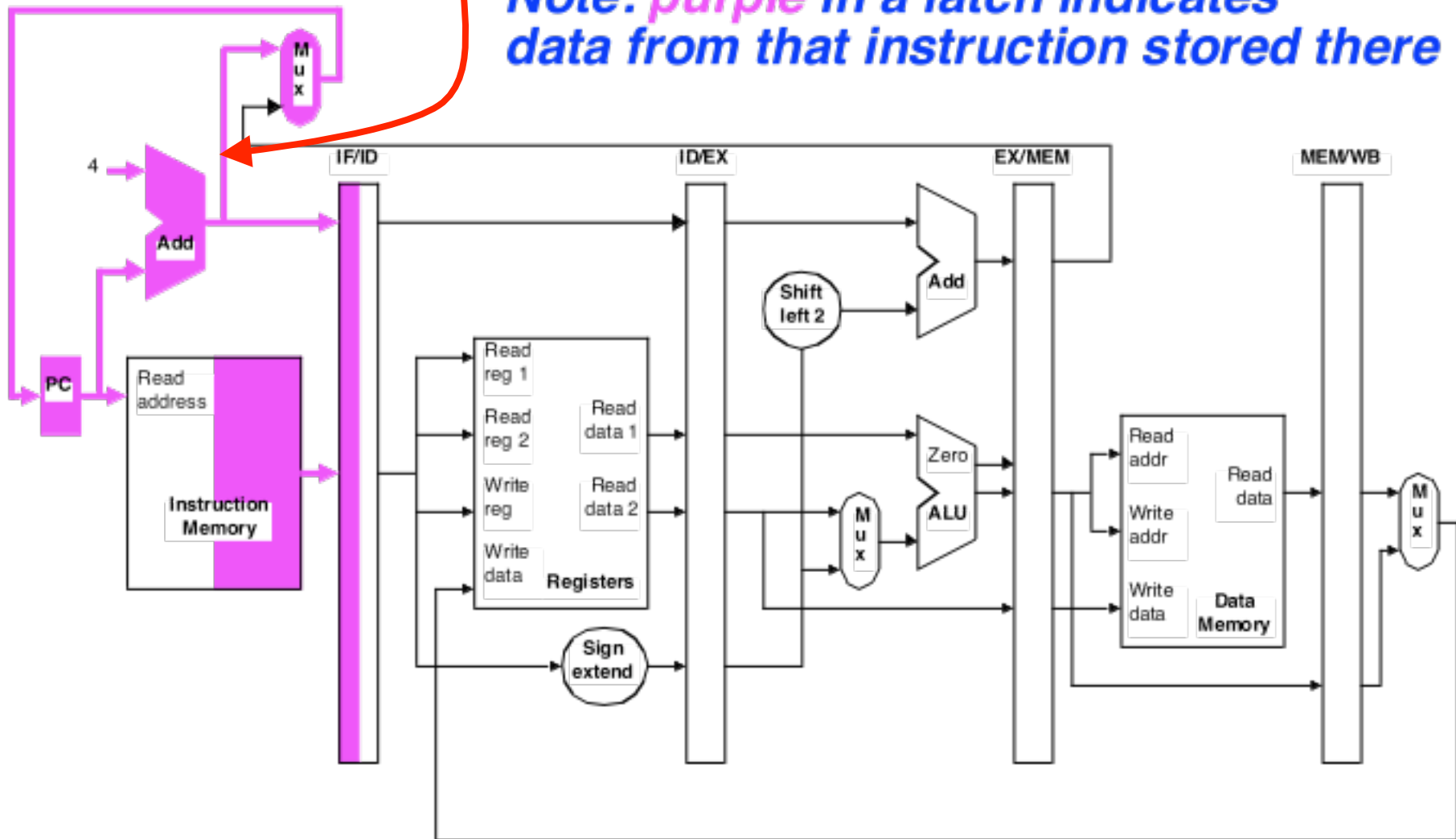
Note: purple in a latch indicates data from that instruction stored there



Data must be stored from one stage to the next in pipeline registers/latches. hold temporary values between clocks and needed info. for execution.

Another way to look at it...

	Clock Number							
Inst. #	1	2	3	4	5	6	7	8
Inst. i	IF	ID	EX	MEM	WB			
Inst. i+1		IF	ID	EX	MEM	WB		
Inst. i+2			IF	ID	EX	MEM	WB	
Inst. i+3				IF	ID	EX	MEM	WB

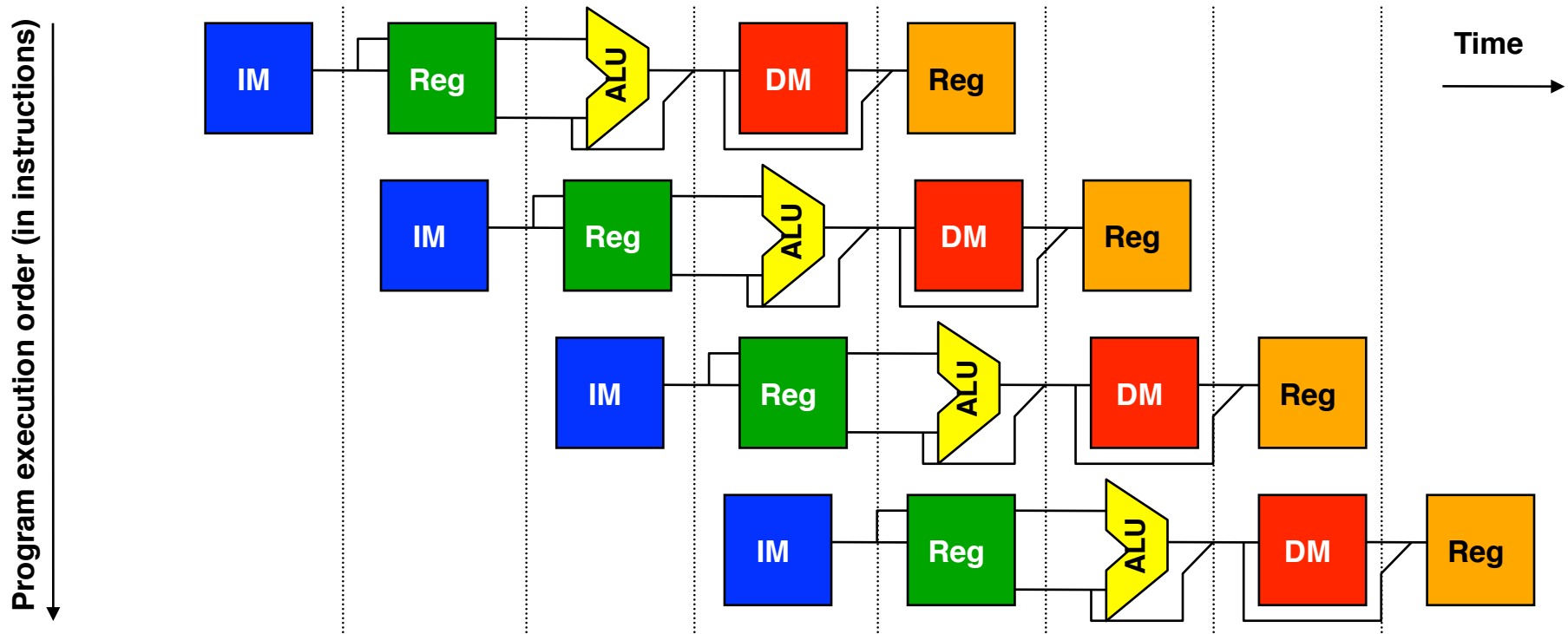


(Tying computer architecture to logic design...)

A SHORT DISCUSSION ABOUT CONTROL LOGIC

The HW needed, plus control

Single cycle MIPS machine

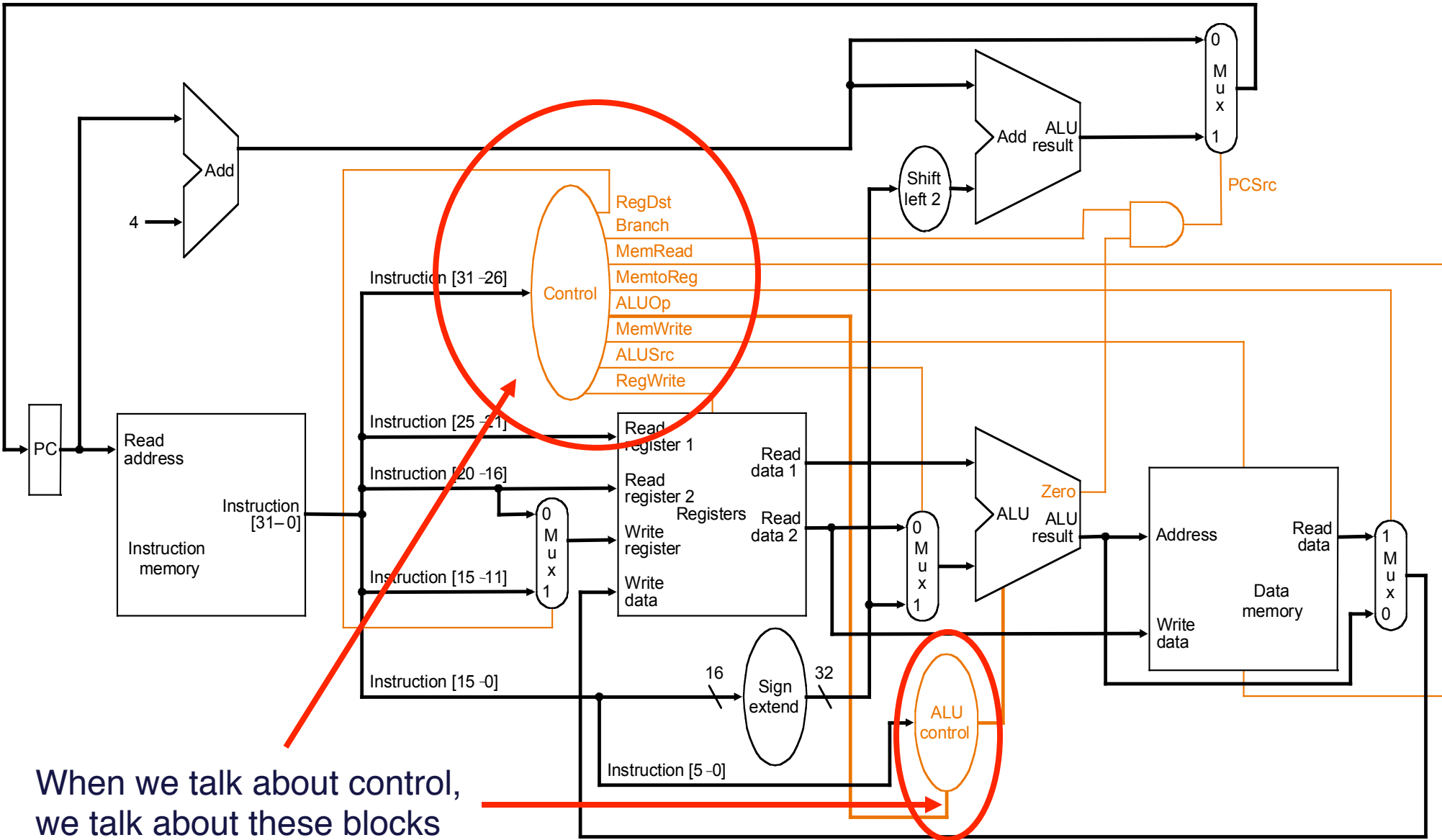

When we talk about control, we talk about these blocks

Single cycle control: inputs & outputs

Step 1:
Identify inputs & outputs

Control Inputs:

- Opcode (6 bits)
- How about R-type instructions?

} columns

Control Outputs:

- RegDst
- ALUSrc
- MemtoReg
- RegWrite
- MemRead
- MemWrite
- Branch
- Jump
- ALUctr

rows

Step 2:
Make a control signal table for each cycle

Control Signal Table

R-type


(inputs)

	Add	Sub	LW	SW	BEQ
Func (input)	100000	100010	xxxxxx	xxxxxx	xxxxxx
Op (input)	000000	000000	100011	101011	000100
RegDst	1	1	0	X	X
ALUSrc	0	0	1	1	0
Mem-to-Reg	0	0	1	X	X
Reg. Write	1	1	1	0	0
Mem. Read	0	0	1	0	0
Mem. Write	0	0	0	1	0
Branch	0	0	0	0	1
ALUOp	Add	Sub	00	00	01

(outputs)


The HW needed, plus control

Single cycle MIPS machine

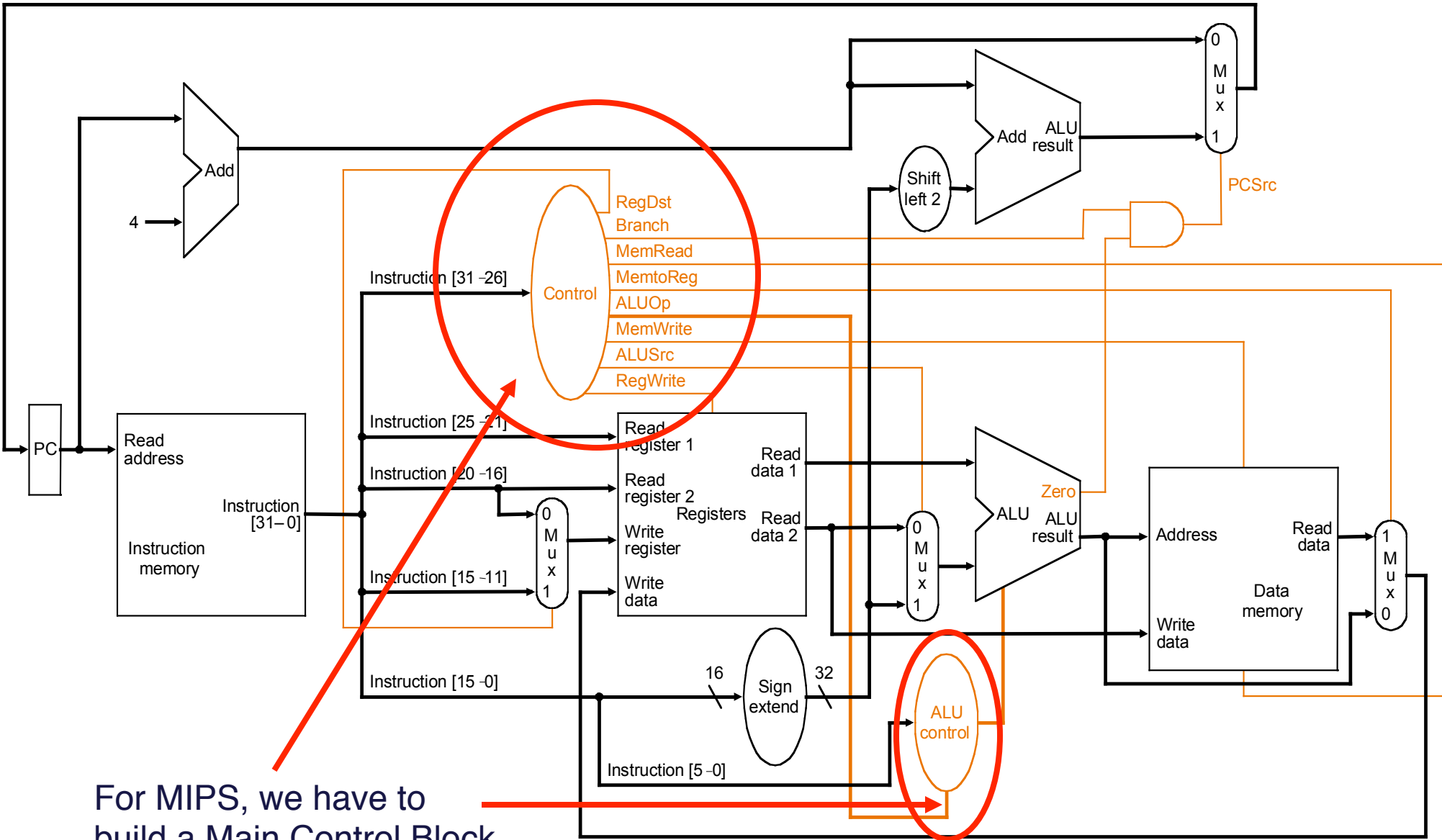


For MIPS, we have to build a Main Control Block and an ALU Control Block

Main control, ALU control

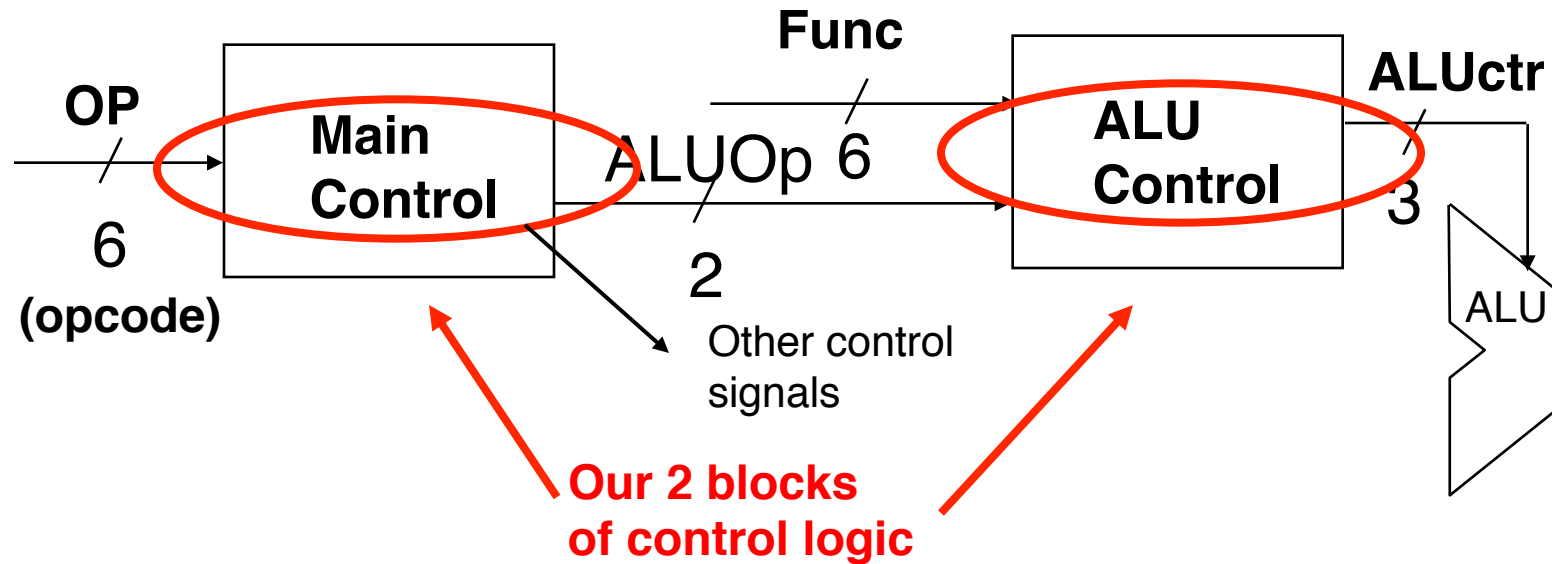

- Use OP field to generate ALUOp (encoding)
 - Control signal fed to ALU control block
- Use Func field and ALUOp to generate ALUctr (decoding)
 - Specifically sets 3 ALU control signals
 - B-Invert, Carry-in, operation

Main control, ALU control

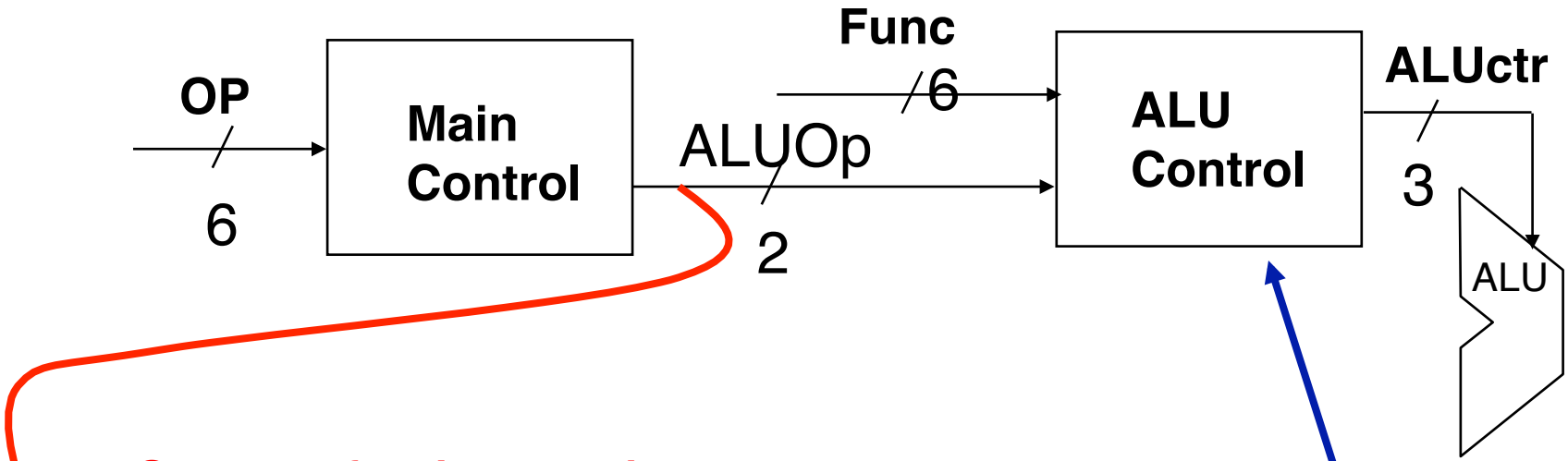

Outputs of main control, become *inputs* to ALU control

	R-type	lw	sw	beq
ALU Operation	"R-type"	add	add	subtract
ALUOp<1:0>	10	00	00	01


We have 8 bits of input to our ALU control block; we need 3 bits of output...

- Or in other words...
- 00 = ALU performs add
 - 01 = ALU performs sub
 - 10 = ALU does what function code says

Generating ALUctr

- We want these outputs:

ALU Operation	and	or	add	sub	slt
ALUctr<2:0>	000	001	010	110	111

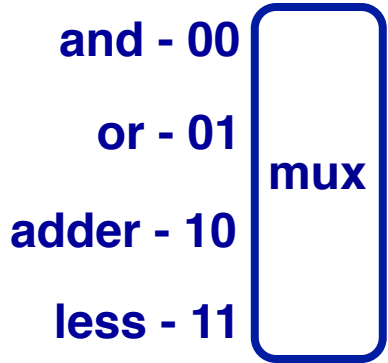

ALUctr<2> = B-negate (C-in & B-invert)
 ALUctr<1> = Select ALU Output
 ALUctr<0> = Select ALU Output

Invert B and C-in must be a 1 for subtract

- We have these **inputs**...

func<5:0>

36 (and)	=	1 0 0 1 0 0
37 (or)	=	1 0 0 1 0 1
32 (add)	=	1 0 0 0 0 0
34 (sub)	=	1 0 0 0 1 0
42 (slt)	=	1 0 1 0 1 0

can ignore these bits
(they're the same for all...)


		Inputs							Outputs	
		ALUOp		Func field					ALUctr	
		ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
lw/sw	→	0	0	X	X	X	X	X	X	010 (add)
beq	→	0	1	X	X	X	X	X	X	110 (sub)
R-type	}	1	X	X	X	0	0	0	0	010 (add)
		1	X	X	X	0	0	1	0	110 (sub)
		1	X	X	X	0	1	0	0	000 (and)
		1	X	X	X	0	1	0	1	001 (or)
		1	X	X	X	1	0	1	0	111 (slt)

The logic:

This table is used to generate the actual Boolean logic gates that produce ALUctr.


Could generate gates by hand, often done w/SW.

		Inputs						Outputs		
		ALUOp		Func field				ALUctr		
		ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
lw/sw	→	0	0	X	X	X	X	X	X	010 (add)
beq	→	0	1	X	X	X	X	X	X	110 (sub)
R-type	}	1	X	X	X	0	0	0	0	010 (add)
		1	X	X	X	0	0	1	0	110 (sub)
		1	X	X	X	0	1	0	0	000 (and)
		1	X	X	X	0	1	0	1	001 (or)
		1	X	X	X	1	0	1	0	111 (slt)

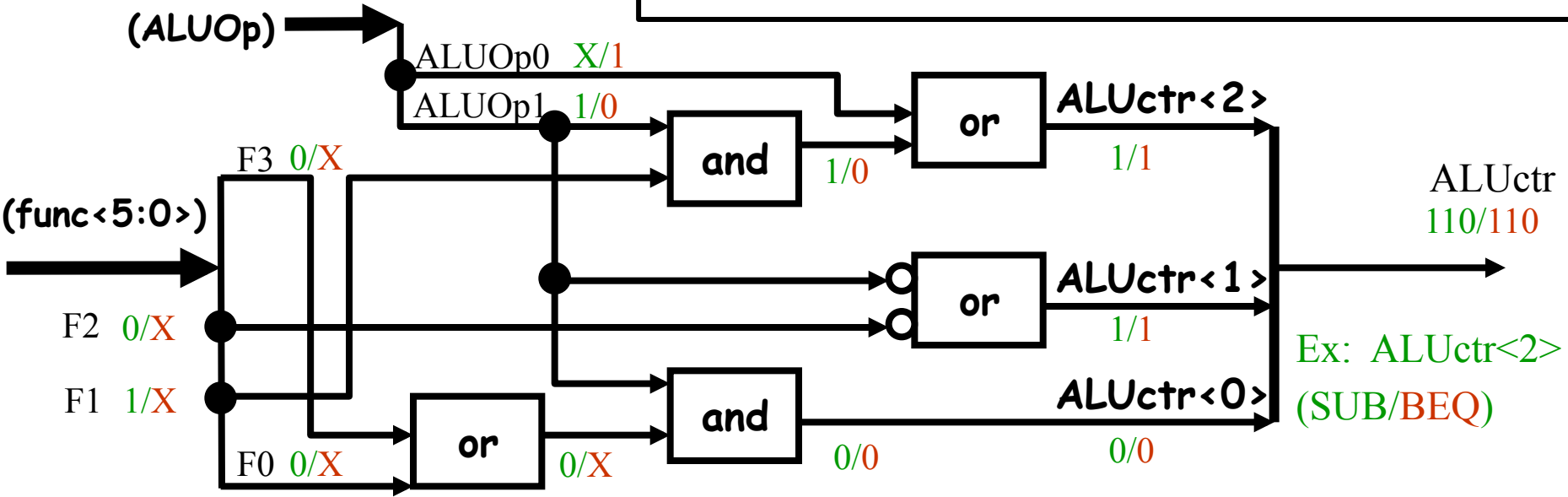

The HW needed, plus control

Single cycle MIPS machine


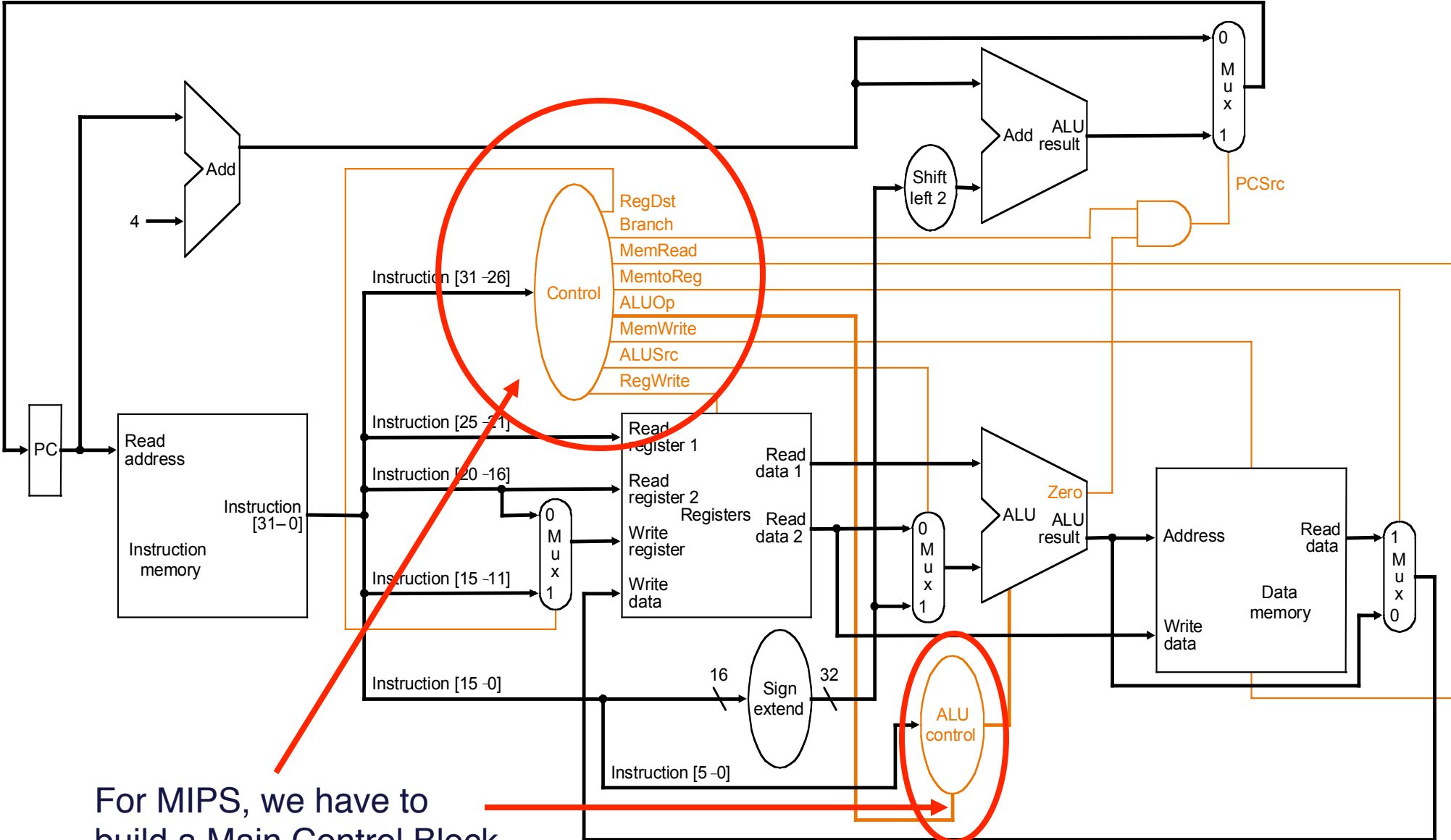


For MIPS, we have to build a Main Control Block and an ALU Control Block

Well, here's what we did...

Single cycle MIPS machine

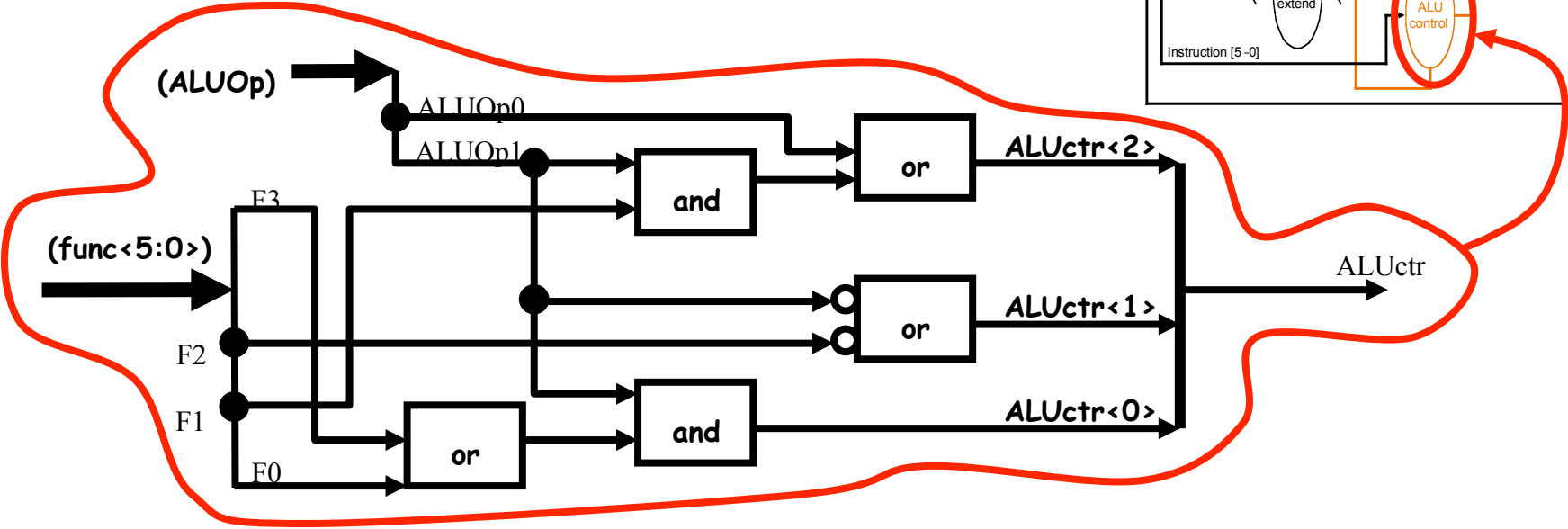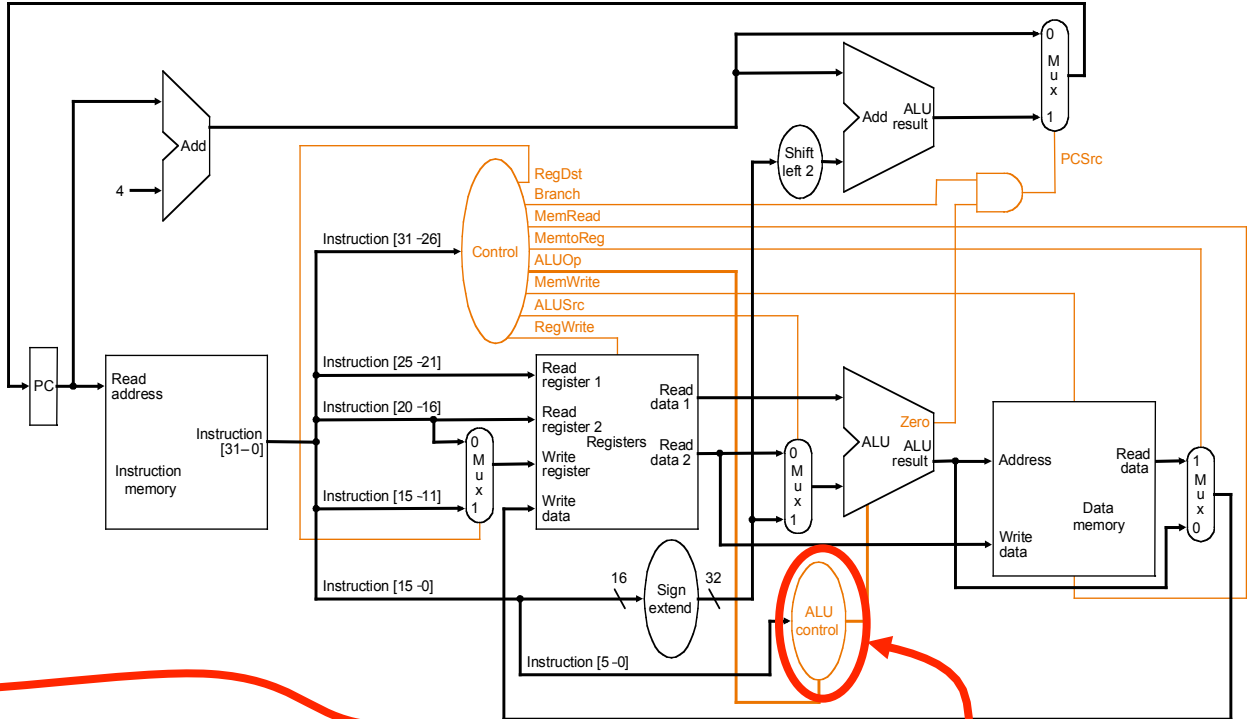We came up with the information to generate this logic which would fit here in the datapath.




Controller FSM for 6-instruction processor

Recall:


- With multi-cycle, need to generate control signals at right time
- Captured by FSM
- Each level analogous to 1 CC

TABLE 8.2 Instruction opcodes.



Instruction	Opcode
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

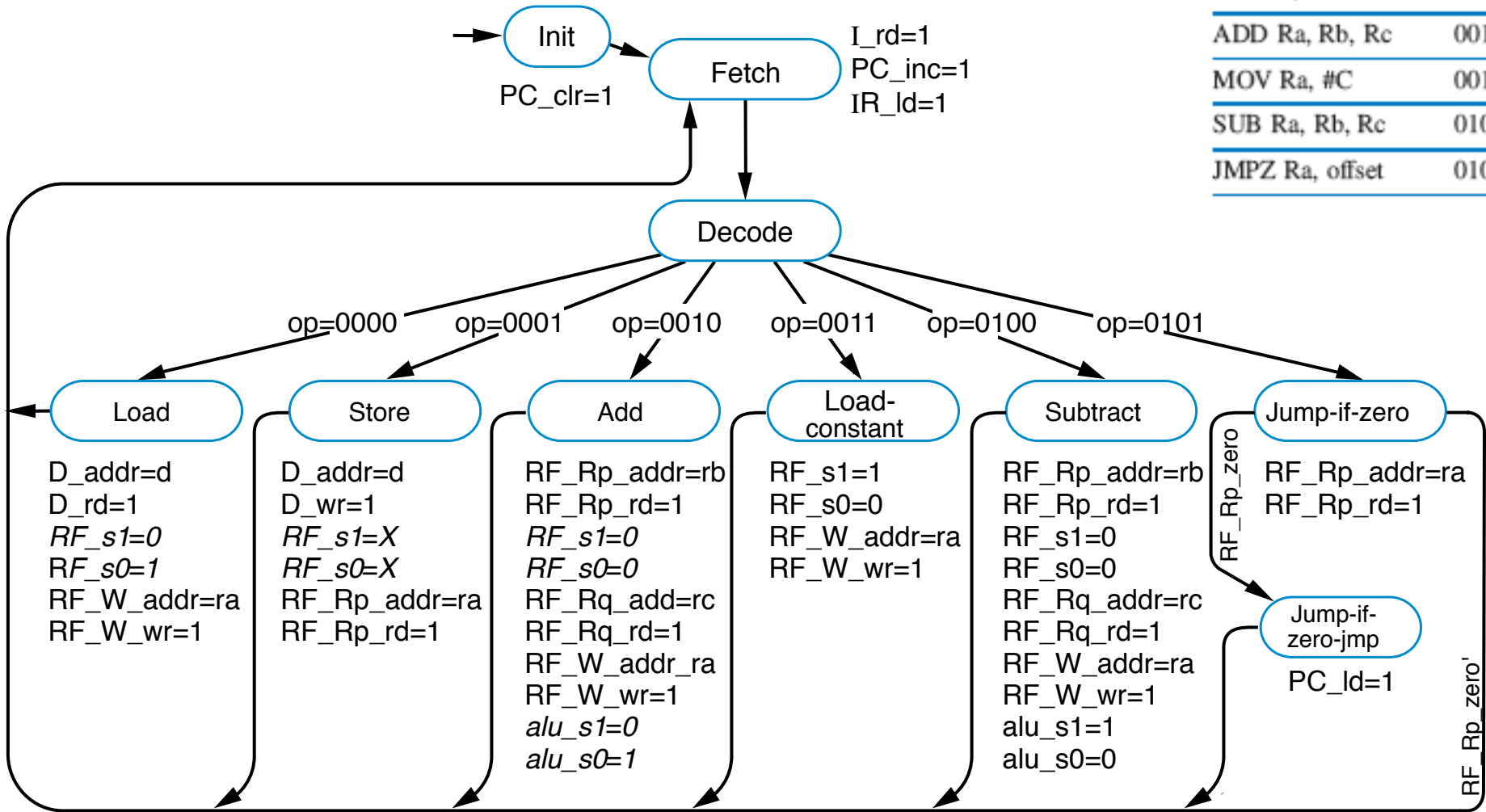

MIPS FSM diagram

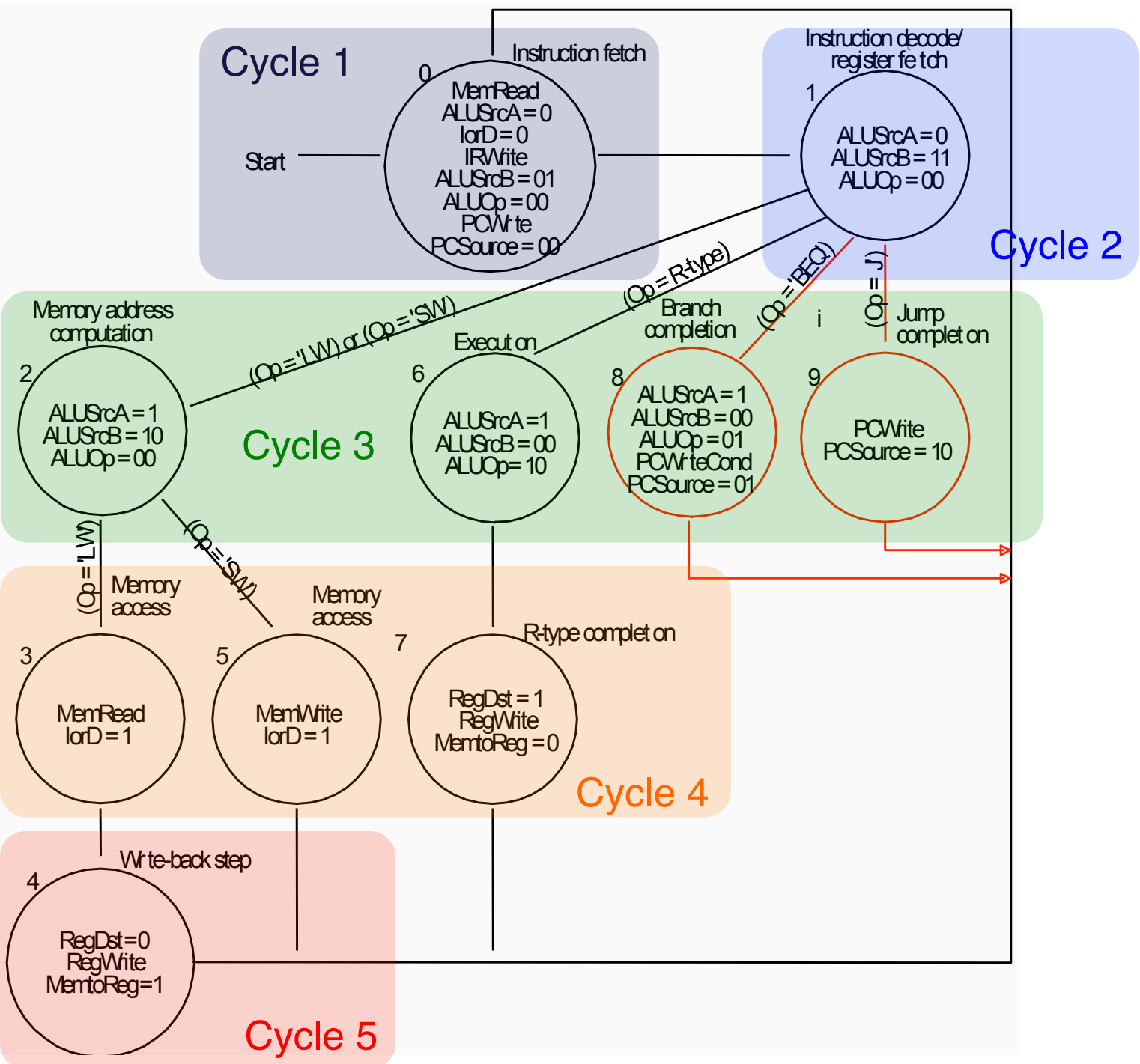

Might also store control signals in ROM

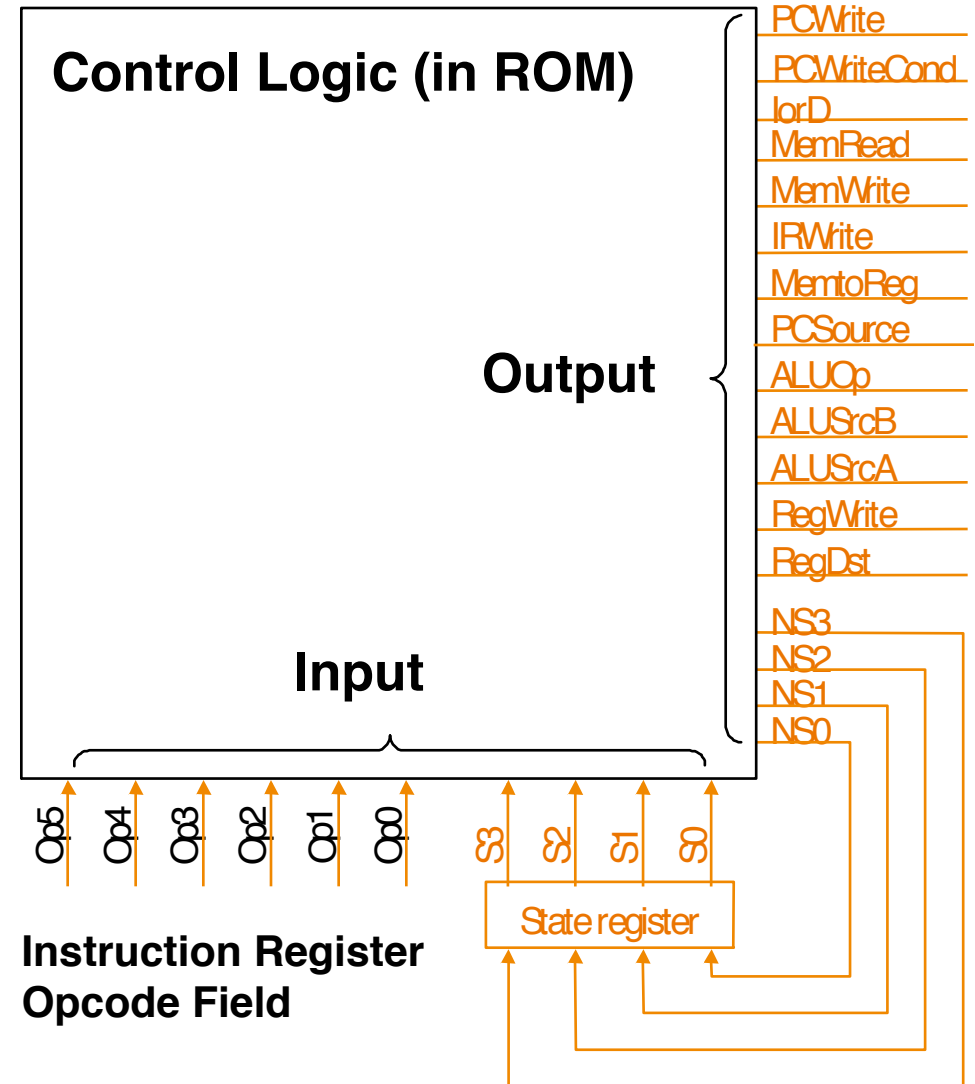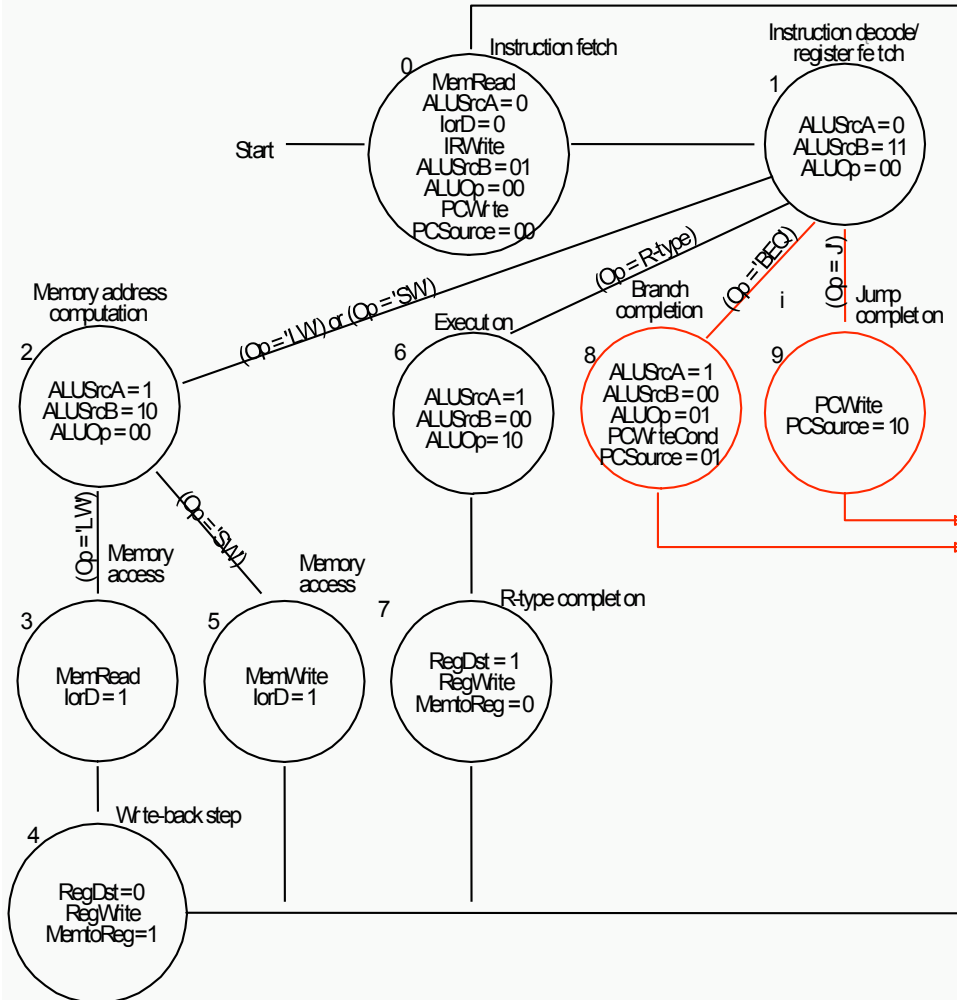


Exceptions

- **Exceptions: unexpected events from within the processor**
 - arithmetic overflow
 - undefined instruction
 - switching from user program to OS
- **Interrupts: unexpected events from outside of the processor**
 - I/O request
- **Consequence: alter the normal flow of instruction execution**
- **Key issues:**
 - detection
 - action
 - save the address of the offending instruction in the EPC
 - transfer control to OS at some specified address
- **Exception type indication:**
 - status register
 - interrupt vector



Another reason that register naming conventions are important.

FSM with Exception Handling

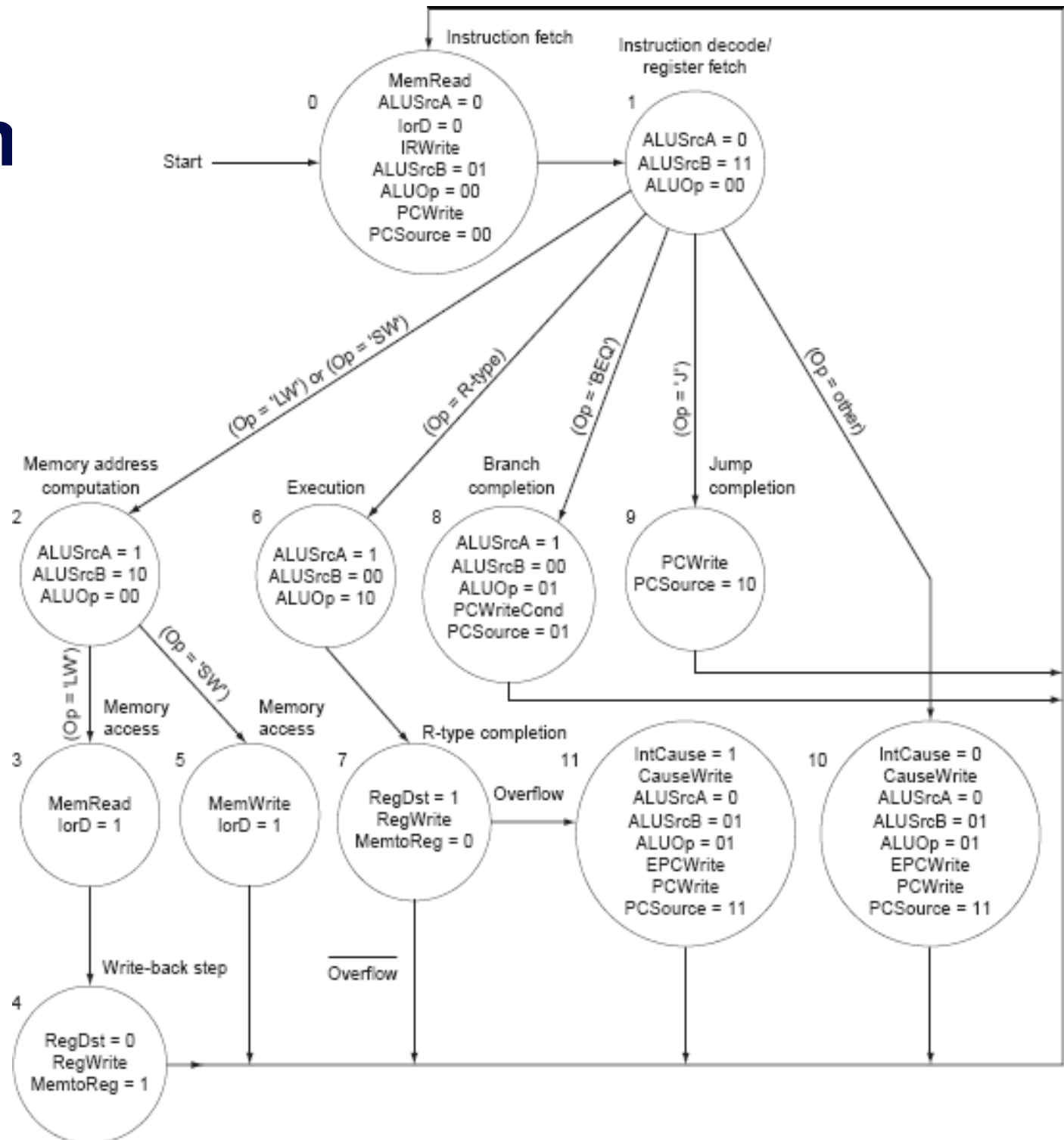

Datapath with Exception Handling

