

$$I_D = 1 \text{ mA} = \frac{1}{2} K_n V_{ov}^2 \Rightarrow V_{ov} = 1 \text{ V}$$

$$V_G = 3 \text{ V} - V_t = V_{ov} = 1 \text{ V} \Rightarrow V_G = 5 \text{ V}$$

$$\frac{5 \text{ V}}{9 \text{ V}} = \frac{R_{G2}}{R_{G1} + R_{G2}} = \frac{22 \text{ M}\Omega}{R_{G1} + 22 \text{ M}\Omega} \Rightarrow R_{G1} = 17.6 \text{ M}\Omega (18 \text{ M}\Omega)$$

$$R_D = R_S = \frac{3 \text{ V}}{1 \text{ mA}} = 3 \text{ k}\Omega \quad R_{G2} = 22 \text{ M}\Omega$$

$$V_G = \frac{22}{18+22} \times 9 \text{ V} = 4.95 \text{ V}$$

$$I_D = \frac{1}{2} K_n V_{ov}^2 = \frac{1}{2} \times 2 \text{ mA/V}^2 \times (4.95 \text{ V} - I_D \cdot 3 \text{ k}\Omega - 1 \text{ V})^2 \Rightarrow I_D = 0.985 \text{ mA}$$

$$V_D = 9 \text{ V} - I_D R_D = 9 \text{ V} - 0.985 \text{ mA} \times 3 \text{ k}\Omega = 6.045 \text{ V}, \quad V_{GD} = -1.09 \text{ V}$$

At the edge of saturation!  $V_{GD} = V_t = 1 \text{ V}$ , so  $V_D$  is 2.09 V from the edge of saturation.

$$5.111 \text{ (a)} \quad A_{vo} = -\frac{2(V_{DD} - V_D)}{V_{ov}} = -\frac{2(10 - 2.5)}{1} = -15 \text{ V/V}$$

$$\text{(b)} \quad I_D = \frac{1}{2} K_n V_{ov}^2 \Rightarrow I_D = \frac{0.5}{4} = 0.125 \text{ mA}, \quad R_D = \frac{(V_D - 2.5) \text{ V}}{0.125} = 60 \text{ k}\Omega,$$

$$g_m = \frac{2 I_D}{V_{ov}} = 0.5 \text{ mA/V}, \quad r_o = \frac{V_A}{I_D} \Rightarrow r_o = 4 \times \frac{75}{0.5} = 600 \text{ k}\Omega$$

$$A_{vo} = 2 \times (-15 \text{ V/V}) = -30 \text{ V/V}$$

$$\text{(c)} \quad A_{vo} = -g_m (r_o || R_o) = -0.5 (600 \text{ k}\Omega || 60 \text{ k}\Omega) = -27.3 \text{ V/V}$$

$$R_{out} = R_o || R_o = 54.5 \text{ k}\Omega$$

$$\text{(d)} \quad R_{in} = R_g = 4.7 \text{ M}\Omega, \quad R_o = 54.5 \text{ k}\Omega$$

$$G_V = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o} = \frac{4.7}{4.7 + 0.1} \times 27.3 \times \frac{15}{15 + 54.5} = 5.77 \text{ V/V}$$

(e) As we can see by reducing  $V_{ov}$  to half of its value or equivalently multiply drain current by 4.  $A_{vo}$  is almost doubled, while  $R_{out}$  is multiplied by 4. As a result,  $G_V$  which is proportional to both  $A_{vo}$  and  $R_{out}$  is only slightly reduced.

$$13.1 \quad NM_L = V_{IL} - V_{OL} = 1.2 - 0.2 = 1V$$

$$NM_H = V_{OH} - V_{IH} = 2.5 - 1.5 = 1V$$

13.4 (a) Worse case

$$NM_H = V_{OH,\min} - V_{IH} = 2.4 - 2 = 0.4V$$

$$NM_L = V_{H,\max} - V_{OL} = 0.8 - 0.4 = 0.4V$$

$$(b) P_{avg} = \frac{1}{2} [5 \times 3m + 5 \times 1m] = 10mW$$

$$(c) \text{Dynamic power dissipation} = f C V_{DD}^2 = 10^6 \times 45 \times 10^{12} \times 25 = 1.13mW$$

$$(d) t_p = \frac{1}{2} (t_{PHL} + t_{PLH}) = \frac{1}{2} (7n + 11n) = 9ns \\ (\text{typical})$$


$$t_p = \frac{1}{2} (15n + 22n) = 18.5ns \\ (\text{maximum})$$

$$13.35. \quad t_{PHL} = 0.69 R_N C \quad t_{PLH} = 0.69 R_P C$$

$$\left(\frac{W}{L}\right)_N = \left(\frac{W}{L}\right)_P = 1 \quad R_N = \frac{12.5}{\left(\frac{W}{L}\right)_N} = 12.5 \text{ k}\Omega \quad R_P = \frac{30}{\left(\frac{W}{L}\right)_P} = 30 \text{ k}\Omega$$

$$\Rightarrow t_p = \frac{1}{2} (t_{PLH} + t_{PHL}) = \frac{0.69 \times 10 \times 10^{-15}}{2} (30 \times 10^3 + 12.5 \times 10^3) = 146.6ps$$

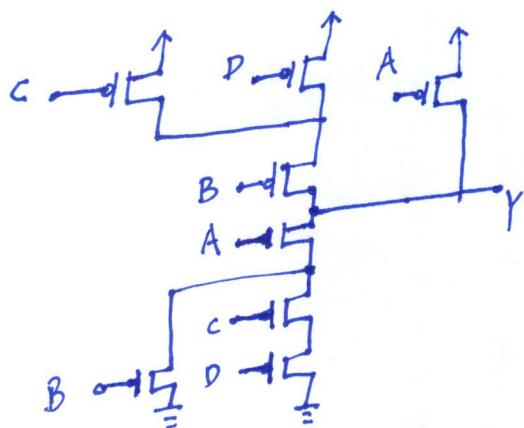13.45. For  $Y = \overline{A + B(C \cdot C + D)}$ , the PDN can be drawn directly, then we can draw its PUN as direct dual:



$$13.46. Y = \bar{A}BC + A\bar{B}C + AB\bar{C}$$

$2(3 \times 3) = 18$  MOS for the gate itself,  $3 \times 2 = 6$  for the required inverters, which needs 24 transistors in total.



For PUN directly: (Inverting variables)

For PDN,  $Y = \bar{A}BC + A\bar{B}C + AB\bar{C}$ . Correspondingly:

$$\bar{Y} = \overline{\bar{A}BC + A\bar{B}C + AB\bar{C}} = \overline{\bar{A}BC} \cdot \overline{A\bar{B}C} \cdot \overline{AB\bar{C}}$$

$$= (\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C) = ABC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}BC,$$



and replicating  $\bar{A}\bar{B}\bar{C}$

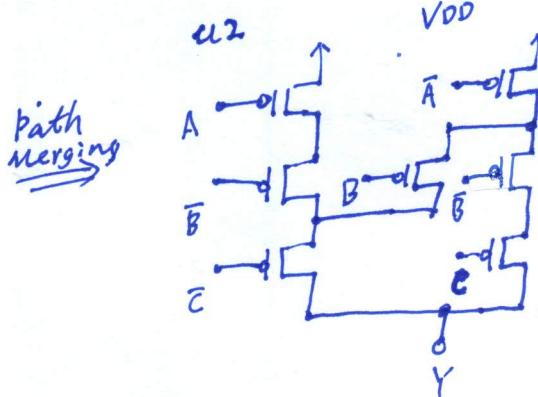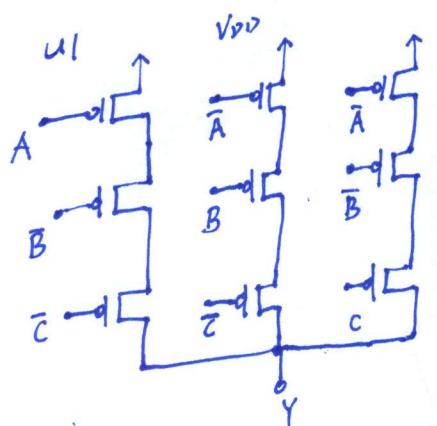



For the PDN directly:

$$\text{From 1, } \bar{Y} = (\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$
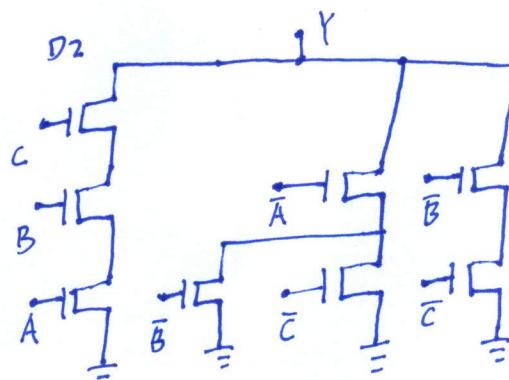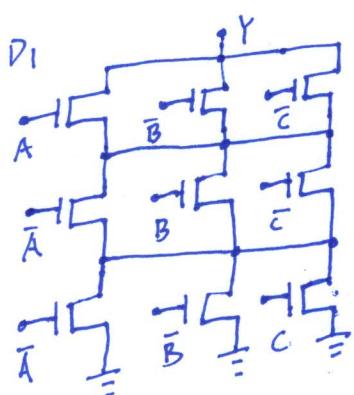
$$\text{From 2, } \bar{Y} = ABC + A\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}, \text{ see D2 where path merging is included.}$$





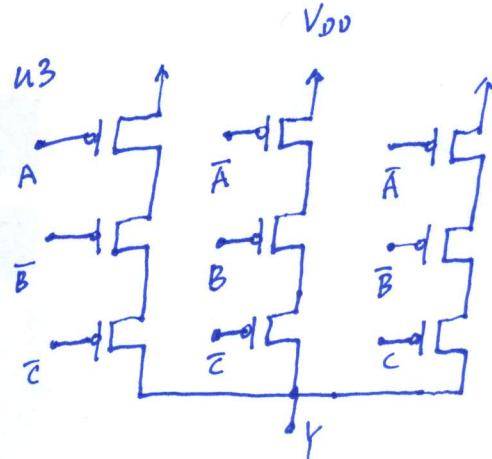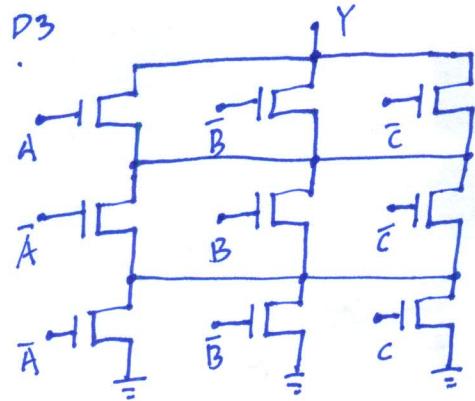Simply, replacing series connections with parallel connections.



see that  $D_3$  is identical to  $D_1$  in detail.

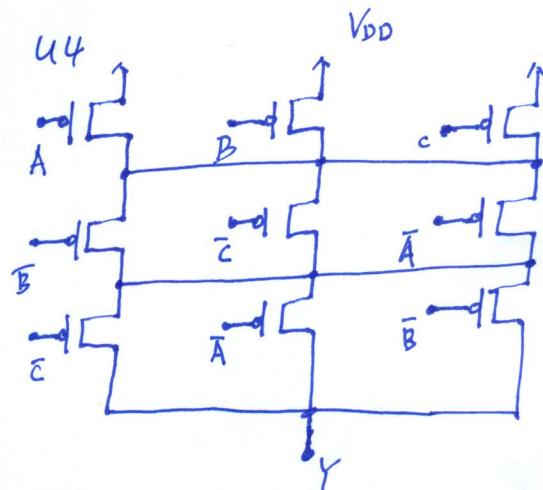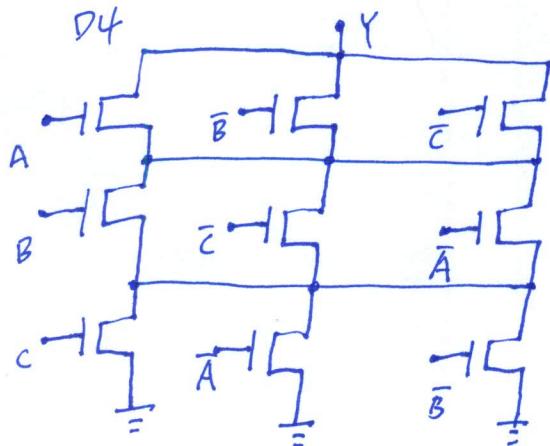For the PUN from PND. See that both parallel and series connections can be identified for transformation, but that the series one contain variables and their complements are therefore always open. Thus, converting parallel paths to serial ones. See this the same as  $U_1$



See that  $U_4$ , while note the same as  $U_1$ , is highly related, having some variable exchange in the middle and right columns. clearly, there are lots of variations of the completely-connected array.