

4.23




$$\textcircled{1} V_o = 2.4 \text{ V. } I_s = 10^{-16} \text{ A} \quad V_D = \frac{V_o}{3} = 0.8 \text{ V}$$

$$I_D = I_s e^{V_D/V_T} = 10^{-16} \times e^{(0.8/0.025)} = 7.9 \text{ mA}$$

$$\textcircled{2} I_D = 6.9 \text{ mA} \Rightarrow V_D = 0.794 \text{ V} \quad V_o = 3 \times V_D = 2.39 \text{ V}$$

$$\Delta V = 2.4 \text{ V} - 2.39 \text{ V} = \Delta V = 2.39 - 2.4 = -10.15 \text{ mV}$$

4.26

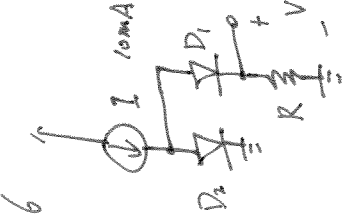

$$V = 80 \text{ mV}$$

$$V = V_{D2} - V_{D1}, \quad I_D = V/R = I_s e^{V_{D1}/V_T}, \quad \cancel{V_{D2}}$$

$$I_{D2} = I - I_{D1} = I_s e^{V_{D1}/V_T}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{10 \text{ mA} - 0.08/R}{0.08/R} = e^{0.08/0.025} = 23.3$$

$$\Rightarrow R = 194 \Omega$$

4.34.



$$\text{(a)} I_D = \frac{1V - 0.7V}{200 \Omega} = 1.5 \text{ mA}$$

$$\text{(b) i)} V = 0.7 \text{ V} \quad i = \frac{1 - 0.7}{200} = 1.5 \text{ mA}$$

$$\text{ii)} V = 0.7 + 2.3 \times 0.025 \log\left(\frac{1.5}{1}\right) = 0.7101 \text{ V}$$

$$i = \frac{1 - 0.7101}{200} = 1.4494 \text{ mA}$$

$$\text{iii)} V = 0.7 + 2.3 \times 0.025 \log\left(\frac{1.4494}{1}\right) = 0.7093 \text{ V}$$

$$i = \frac{1 - 0.7093}{200} = 1.4537 \text{ mA}$$

$$\text{iv)} V = 0.7 + 2.3 \times 0.025 \log\left(\frac{1.4537}{1}\right) = 0.7093 \text{ V}$$

$$i = \frac{1 - 0.7093}{200} = 1.4537 \text{ mA} \quad \text{same as iii)}$$

4.39. (a)

$$V = -5V + 0.7V = -4.3V$$


$$I = \frac{5V + 4.3V}{10k\Omega} = 0.93mA$$



(b)

$$V = 5V$$

$$I = 0$$

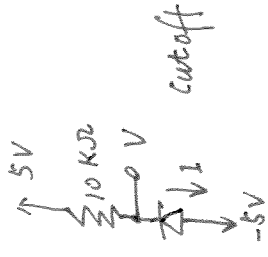

(c)

$$V = 5V - 0.7V = 4.3V$$


$$I = \frac{4.3V + 5V}{10k\Omega} = 0.93mA$$



(d)

$$V = -5V$$


$$I = 0$$

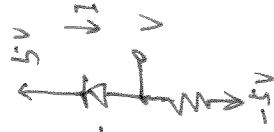

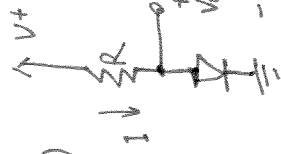4.52. (a)


$$I = \frac{V^+ - V_0}{R}$$

$$\frac{\Delta V_0}{\Delta V^+} = \frac{R_d}{R + R_d} = \frac{V_T / I}{R + \frac{V_T}{I}} = \frac{V_T}{V^+ - V_0 + V_T} = \frac{V_T}{V^+ + V_T - 0.7}$$



(b)
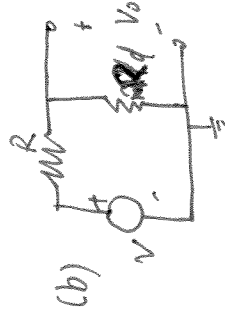
$$\frac{\Delta V_0}{\Delta V^+} = \frac{mR_d}{mR_d + R} = \frac{mV_T}{IR + mV_T} = \frac{mV_T}{mV_T + V^+ - 0.7m}$$



(c) (i) $m = 1$ $V^+ = 10V$

$$\frac{\Delta V_o}{\Delta V^+} = \frac{V_T}{V_T + V^+ - 0.7} = 2.68 \text{ mV/V}$$


(ii) $m = 3$ $V^+ = 10V$

$$\frac{\Delta V_o}{\Delta V^+} = \frac{3V_T}{3V_T + 10V - 0.7} = 9.4 \text{ mV/V}$$

4.54

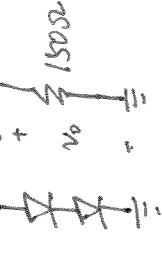0.7V drop at $I_D = 10 \text{ mA}$:

$$I_S = \frac{I_D}{e^{\frac{V_D}{V_T}}} = \frac{10 \text{ mA}}{e^{\frac{0.7}{0.025}}} = 6.91 \times 10^{-15} \text{ A}$$



when $V_D = 1.5V$ $V_D = \frac{1.5V}{2} = 0.75V$

$$I_D = I_S e^{\frac{V_D}{V_T}} = 6.91 \times 10^{-15} \text{ A} \cdot e^{\frac{0.75}{0.025}} = 73.84 \text{ mA}$$

$$I_L = \frac{V_o}{R_L} = \frac{1.5V}{150\Omega} = 10 \text{ mA}$$

$$I = I_D + I_L = 83.84 \text{ mA}$$

$$R = \frac{5V - 1.5V}{83.84 \text{ mA}} = 41.75\Omega$$

"If the diode is disconnected, use the small signal ~~and~~ diode model

$$r_d = \left(\frac{dV_D}{dI_D} \right) \Big|_{I_D = 73.84 \text{ mA}} = \frac{V_T}{I_D} = \frac{0.025V}{73.84 \text{ mA}} = 0.34\Omega$$


The change of output voltage is $\Delta V_o = 2 \Delta I_D \cdot r_d = 2 \times 10 \text{ mA} \times 0.34\Omega = 6.8 \text{ mV}$

If the load resistance reduced to 100Ω : $\Delta V_o = 2 \times \left(\frac{1.5}{150} - \frac{1.5}{100} \right) \times 0.34 = 3.4 \text{ mV}$

If the load resistance reduced to 75Ω : $\Delta V_o = 2 \times \left(\frac{1.5}{150} - \frac{1.5}{75} \right) \times 0.34 = 6.8 \text{ mV}$

If the load resistance reduced to 50Ω : $\Delta V_o = 2 \times \left(\frac{1.5}{150} - \frac{1.5}{50} \right) \times 0.34 = 13.6 \text{ mV}$

4.59

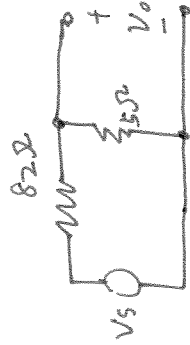

small-signal model

$$\frac{\Delta V_o}{\Delta V_s} = \frac{5}{82 + 5} = \frac{5}{87}$$

$$\Delta V_o = \Delta V_s \cdot \frac{5}{87} = 1V \times \frac{5}{87} = 57.5 \text{ mV}$$