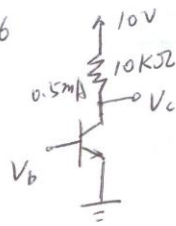


EE20 242

HW 7

6.86



$$V_c = V_{cc} - I_c R_c = 10 - 0.5 \times 10 = 5V$$

$$\Delta V_{BE} = V_T \ln(I_{c2}/I_{c1})$$

$$(705mV - 700mV) = 25mV \ln(I_{c2}/0.5mA)$$

$$\Rightarrow I_{c2} = 0.61mA$$

$$V_{c2} = 10V - 0.61mA \times 10k\Omega = 3.98V$$

$$A_v = \frac{-(0.61mA - 0.5mA) \times 10k\Omega}{705mV - 700mV} = -220V/V$$

$$A_v = -g_m R_c = -\frac{I_c R_c}{V_T} = \frac{-0.5mA \times 10k\Omega}{0.025V} = -200V/V$$

6.87

$$g_m = \frac{I_c}{V_T} = \frac{0.6mA}{0.025V} = 24mA/V$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{120}{24} = 5k\Omega$$


$$r_e = \frac{r_{\pi}}{\beta+1} = \frac{5k\Omega}{121} = 41.3\Omega$$

$$g_m = \frac{60\mu A}{0.025V} = 2.4mA/V$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{120}{2.4} = 50k\Omega$$

$$r_e = \frac{r_{\pi}}{\beta+1} = \frac{50k}{121} = 413\Omega$$

6.95

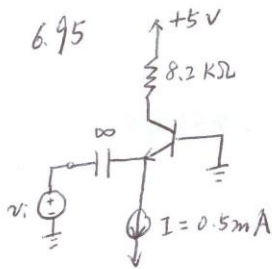


for a very high β ,

$$I_c \approx I_E = 0.5mA$$

$$g_m = \frac{I_c}{V_T} = \frac{0.5mA}{0.025} = 20mA/V$$
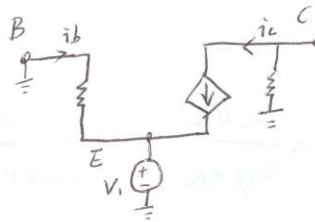
$$V_c = 5V - 8.2k\Omega \times 0.5mA = 0.9V$$





$$V_{\pi} = -V_i$$

$$V_c = -g_m R_c V_{be}$$

$$= -20 \times 8.2 \times (-V_i)$$

$$\frac{V_c}{V_i} = 20 \times 8.2 = 164V/V$$

6.100

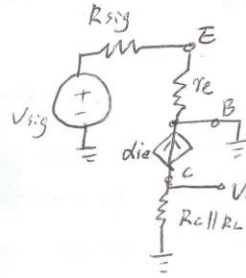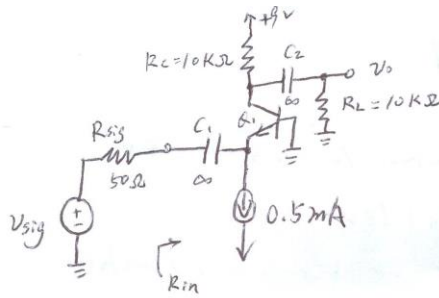

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$R_{in} = r_e = 50 \Omega$$

$$v_o = -0.99 i_c (R_c \parallel R_L) = -0.99 \frac{-v_{sig} (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)}{R_{in}}$$

$$\frac{v_o}{v_{sig}} = + \frac{0.99 \times 5 \text{ k}\Omega}{50 \text{ k}} = 99 \text{ V/V}$$

6.122 $v_{be}(t) = r_e i_e$, $v_o(t) = -\alpha i_e (R_c \parallel R_L)$


$$\Rightarrow v_{be}(t) = -r_e \frac{v_o(t)}{\alpha (R_c \parallel R_L)}$$

$$|v_o(t)| = \frac{\alpha (R_c \parallel R_L)}{r_e} |v_{be}(t)| = \frac{\alpha (R_c \parallel R_L) \cdot I_E}{V_T} |v_{be}(t)| = \frac{1 \times (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega) \times 0.25 \text{ mA}}{0.025 \text{ V}} |v_{be}(t)|$$

$$= 0.5 \text{ V}$$

$$G_v = \frac{v_o(t)}{v_{sig}(t)} = \alpha \frac{R_c \parallel R_L}{R_{sig} + r_e} = \frac{1 \times (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)}{1 \text{ k}\Omega + \frac{0.025 \text{ V}}{0.25 \text{ mA}}} = 4.55 \text{ V/V}$$

$$|v_{sig}(t)| = \frac{v_o(t)}{G_v} = 0.5 \text{ V} / 4.55 = 0.11 \text{ V}$$

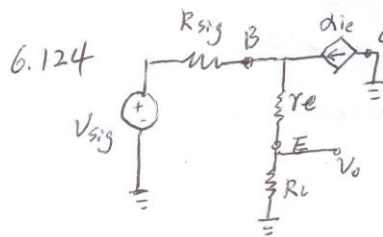

(a) $I_E = \frac{\beta + 1}{\beta} I_C = \frac{101}{100} \times 10^{-3} \text{ A} = 1.01 \text{ mA}$

$$r_e = \frac{V_T}{I_E} = \frac{0.025 \text{ V}}{1.01 \text{ mA}} = 24.752 \Omega$$

$$R_{in} = (\beta + 1) (r_e + R_L) = 101 \times (24.752 \Omega + 1 \text{ k}\Omega) = 103.5 \text{ k}\Omega$$

$$G_v = v_o / v_{sig} = \frac{(\beta + 1) R_L}{(\beta + 1) R_L + (\beta + 1) r_e + R_{sig}} = \frac{101 \times 1 \text{ k}\Omega}{101 \times 1 \text{ k}\Omega + 101 \times 24.752 + 20 \text{ k}\Omega} = 0.8178$$

$$i_c(t) = v_o(t) / R_L = \frac{G_v \cdot v_{sig}}{R_L}$$

$$V_{be}(t) = r_e i_e(t) = (r_e / R_L) G_v v_{sig}(t) \Rightarrow \frac{V_{be}(t)}{v_{sig}(t)} = \frac{r_e G_v}{R_L} = \frac{24.752 \times 0.8178}{1000} = 0.02024$$

$$v_b(t) = v_o(t) + V_{be}(t)$$

$$\frac{v_b(t)}{v_{sig}(t)} = \frac{v_o(t)}{v_{sig}(t)} + \frac{V_{be}(t)}{v_{sig}(t)} = G_v + \frac{r_e G_v}{R_L} = 0.8178 + 0.02024 = 0.838$$

(b) $v_{be}(t) / v_{sig}(t) = 0.02024$

$$\Rightarrow |v_{sig}(t)|_{\max} = |v_{be}(t)|_{\max} / 0.02024 = 10 \times 10^{-3} / 0.02024 = 0.494 \text{ V}_{\text{oid}}$$

$$|v_o(t)|_{\max} = G_v |v_{sig}(t)|_{\max} = 0.494 \times 0.8178 = 0.404 \text{ V}$$


(c) If R_L is removed, $i_e = 0 \Rightarrow v_e = v_{sig} \Rightarrow G_{vo} = 1$

$$\left. \begin{aligned} R_{out} &= -\frac{v_o(t)}{i_e(t)} & i_e(t) &= \frac{v_b(t) - v_e(t)}{r_e} = \frac{v_b(t) - v_{sig}(t)}{r_e} \\ v_b(t) &= -i_e(t) (1-\alpha) R_{sig} \Rightarrow i_e(t) &= \frac{-i_e(t) (1-\alpha) R_{sig} - v_{sig}(t)}{r_e} \\ r_e i_e(t) &= -i_e(t) (1-\alpha) R_{sig} - v_{sig}(t) \\ i_e(t) &= \frac{-v_{sig}(t)}{r_e + (1-\alpha) R_{sig}} \end{aligned} \right\}$$

$$\Rightarrow R_{out} = r_e + (1-\alpha) R_{sig} = r_e + \frac{1}{\beta+1} R_{sig} = 24.752 + \frac{20 \times 10^3}{101} = 222.772$$

$$\frac{v_o(t)}{v_{sig}(t)} = \frac{1000}{1000 + 222.772} = 0.8178 \text{ It agrees with } G_v \text{ in (a).}$$

6.130

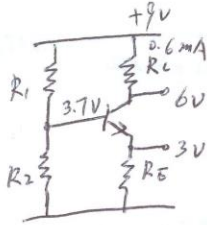

For $\beta = \infty, I_B = 0, V_B = V_E + 0.7 = 3.7V,$

$I_E \approx I_C = 0.6mA.$

$I_{R1} = \frac{I_E}{10} = 0.06mA, R_1 = \frac{9 - 3.7}{0.06} = 88.3k\Omega$

$R_2 = \frac{3.7}{0.06} = 61.7k\Omega$

use $R_1 = 82k\Omega, R_2 = 68k\Omega$

Now $V_{BB} = \frac{9 \times 68}{82 + 68} = 4.08V, R_{BB} = \frac{68 \times 82}{150} = 37.2k\Omega$

$R_E = R_C = \frac{3V}{0.6mA} = 5k\Omega$ use $5.1k\Omega$

For $\beta = 90, I_E = \frac{V_{BB} - 0.7}{\frac{R_{BB}}{\beta + 1} + R_E} = \frac{3.39}{0.41 + 5.1} = 0.615mA$


$V_E = 0.615mA \times 5.1 = 3.14V$

$V_B = V_E + 0.7 = 3.84V$

$V_C = 9 - 5.1 \times 0.65 \times 90 / 90 = 5.9V$

(check $V_B = V_{BB} - R_{BE} \times I_E / 91 = 3.83V$)

6.138

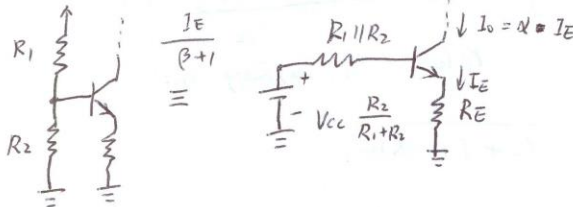

$V_{CC} \cdot \frac{R_2}{R_1 + R_2} = \frac{I_E}{\beta + 1} (R_1 || R_2) + V_{BE} + I_E R_E$

$\Rightarrow I_E = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{R_E + \frac{R_1 || R_2}{\beta + 1}}$

$\Rightarrow I_0 = \alpha I_E = \frac{\alpha (V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE})}{R_E + \frac{R_1 || R_2}{\beta + 1}}$