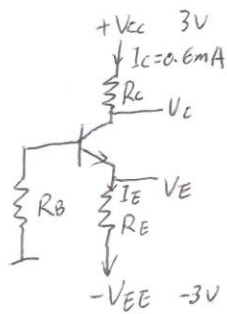


HW 8

EE 20243

6.133



(a) $\beta = \infty$

$$I_B = 0, V_B = 0, V_E = -0.7V$$

$$V_C = \frac{V_{CC} + V_E}{2} = \frac{3V + (-0.7V)}{2} = 1.15V$$

$$R_C = \frac{3V - 1.15V}{0.6mA} = 3.08K\Omega$$

$$R_E = \frac{3V - 0.7V}{0.6mA} = 3.83K\Omega$$

(b) $\beta = 90$ $V_B = \frac{3V - 0.7V}{10} = 0.23V$

$$I_B = I_C / \beta = 0.6mA / 90 = 0.00667mA$$

$$R_B = \frac{V_B}{I_B} = \frac{0.23V}{0.00667mA} = 34.48K\Omega$$

(c) selected R's : $R_C = 3.0K\Omega$ $R_E = 3.6K\Omega$, $R_B = 33K\Omega$

(d) for $\beta = \infty$: $I_B = 0$, $V_B = 0$, $V_E = -0.7V$

$$V_C = V_{CC} - I_C R_C = 3V - \frac{3V - 0.7V}{3.6K\Omega} \times 3K\Omega = 1.08V$$

$$I_C = (3V - 0.7V) / 3.6K\Omega = 0.64mA$$

$$\text{For } \beta = 90: I_E = \frac{3V - 0.7V}{3.6K\Omega + 33K\Omega / 91} = 0.58mA$$

$$I_C = I_E \cdot \frac{\beta}{\beta + 1} = 0.58 \times \frac{90}{91} = 0.57mA$$

$$V_E = -V_{EE} + I_E R_E = -3V + 0.58mA \times 3.6K\Omega = -0.91V$$


$$V_B = V_E + 0.7V = -0.21V$$

$$V_C = V_{CC} - I_C R_C = 3V - 0.57mA \times 3.0K\Omega = 1.29V$$

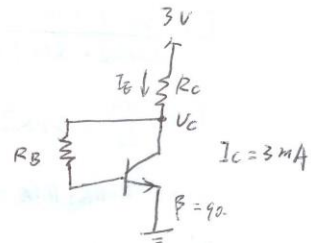6.136 (a) $V_C = \frac{V_{CC}}{2} = 1.5V$ $\beta = 90$

$$I_E = \frac{3V - 1.5V}{R_C} = \frac{1.5V}{R_C} = \frac{I_C}{\alpha} \Rightarrow R_C = 494.5\Omega$$

$$R_B = \frac{1.5V - 0.7V}{I_C / \beta} = \frac{0.8V}{3mA / 90} = 24K\Omega$$



(b) selected R's

$$R_B = 24 \text{ K}\Omega \quad R_C = 495 \Omega \rightarrow 510 \Omega$$

$$\text{then } I_E = \frac{3V - 0.7V}{510 \Omega + \frac{24 \text{ K}\Omega}{91}} = 2.97 \text{ mA}$$


$$I_C = \alpha I_E = 2.94 \text{ mA}$$

$$V_C = 3V - 2.97 \text{ mA} \times 510 = 1.485 \text{ V}$$

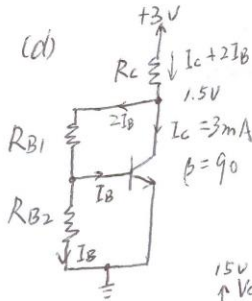(c) $\beta = \infty, I_B = 0, V_B = 0.7 \text{ V}$

$$I_C = I_E = \frac{3V - 0.7V}{510 \Omega} = 4.5 \text{ mA}$$

$$V_C = 3V - 4.5 \text{ mA} \times 510 \Omega = 0.705 \text{ V}$$





$$I_B = \frac{I_C}{\beta} = \frac{3 \text{ mA}}{90} = 0.033 \text{ mA}$$

$$1.5V - 0.7V = 2 I_B \times R_{B1} \Rightarrow R_{B1} = \frac{0.8V}{2 \times 0.033 \text{ mA}} = 12.12 \text{ K}\Omega$$

$$0.7V = I_B \times R_{B2} \Rightarrow R_{B2} = \frac{0.7V}{0.033 \text{ mA}} = 21.21 \text{ K}\Omega$$
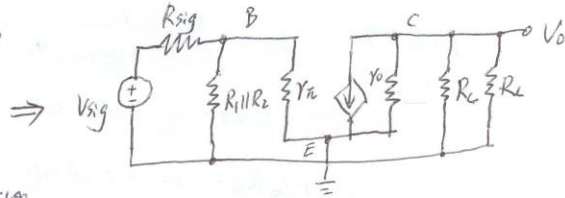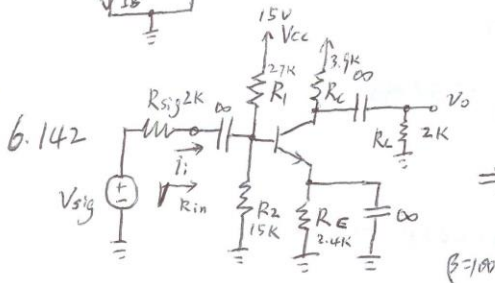
$$(I_C + 2 I_B) R_C = 3V - 1.5V \Rightarrow R_C = \frac{1.5V}{3 \text{ mA} + 2 \times 0.033 \text{ mA}} = 489 \Omega$$




$$V_{BB} = 15V \cdot \frac{R_2}{R_1 + R_2} = 15V \cdot \frac{15}{15 + 27} = 5.36 \text{ V}, \quad R_{1||R_2} = 9.64 \text{ K}\Omega$$

$$I_E = \frac{5.36V - 0.7V}{2.4 \text{ K}\Omega + \frac{9.64 \text{ K}\Omega}{101}} = 1.87 \text{ mA}, \quad g_m = \frac{I_C}{V_T} = \frac{1.87 \text{ mA} \times \frac{100}{101}}{0.025 \text{ V}} = 74 \text{ A/V}$$

$$r_o = \frac{V_A}{I_C} = 54 \text{ K}\Omega, \quad r_{\pi} = \frac{\beta}{g_m} = 1.35 \text{ K}\Omega,$$

$$R_{in} = R_{1||R_2} || r_{\pi} = 1.18 \text{ K}\Omega$$

$$\frac{V_o}{V_{sig}} = - \frac{R_{in}}{R_{in} + R_{sig}} g_m (r_o || R_C || R_L) = - \frac{1.18}{3.18} \times 74 \times 1.29 = -35.4 \text{ V/V}$$

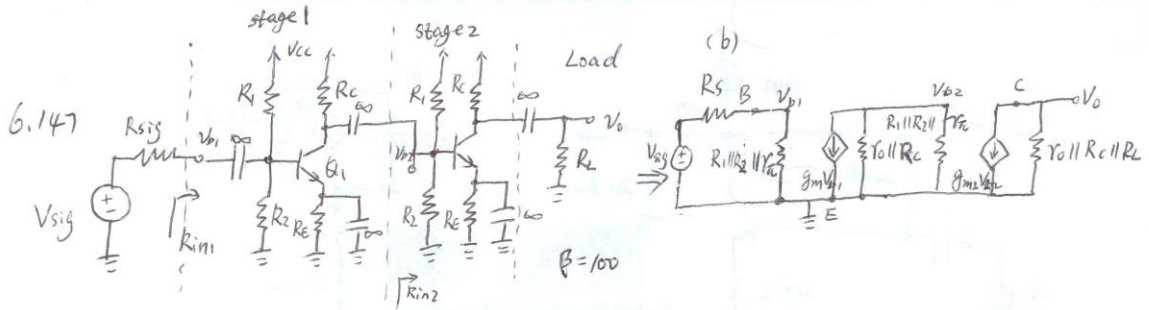

$$(a) \quad V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 9V \times \frac{47}{47 + 100} = 2.88V, \quad R_1 || R_2 = 31.97k\Omega$$

$$I_E = \frac{(2.88 - 0.7)V}{3.9k\Omega + 31.97k\Omega / 101} = 0.517mA, \quad I_C = \frac{100}{101} \times 0.517mA = 0.512mA$$

$$V_C = V_{CC} - I_C R_C = 9V - 0.512mA \times 6.8k\Omega = 5.52V$$

$$(b) \quad g_m = \frac{I_C}{V_T} = \frac{0.512mA}{25mV} = 0.020A/V, \quad r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.020} = 5k\Omega$$

$$r_o = \frac{V_A}{I_C} = 195.3k\Omega$$

$$(c) \quad R_{sig} = 5k\Omega$$

$$R_{in1} = R_1 || R_2 || r_{\pi} = 4.32k\Omega$$

$$\frac{V_{b1}}{V_{sig}} = \frac{R_{in1}}{R_{in1} + R_{sig}} = \frac{4.32}{4.32 + 5} = 0.464$$


$$(d) \quad R_{in2} = R_1 || R_2 || r_{\pi} = 4.32k\Omega \quad R_C \ll r_o$$

$$\frac{V_{b2}}{V_{b1}} = -g_m (r_o || R_C || R_{in2}) = 0.020A/V (6.57k\Omega || 4.32k\Omega) = 52.13V/V$$

$$(e) \quad R_L = 2k\Omega$$

$$\frac{V_o}{V_{b2}} = -g_m (r_o || R_C || R_L) = 0.020A/V (6.57k\Omega || 2k\Omega) = 30.67V/V$$
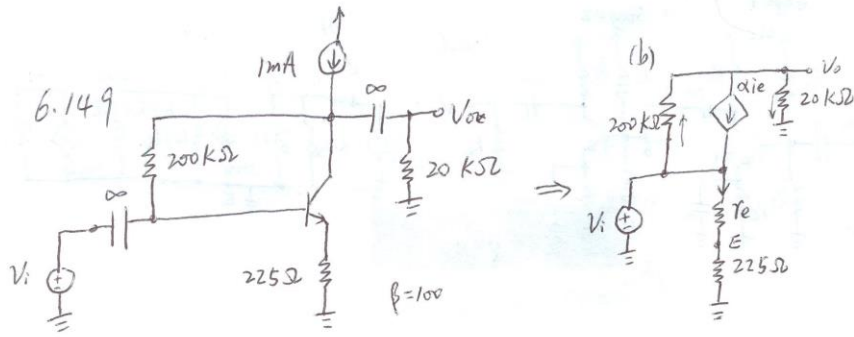
$$(f) \quad \frac{V_o}{V_{sig}} = \frac{V_o}{V_{b2}} \cdot \frac{V_{b2}}{V_{b1}} \cdot \frac{V_{b1}}{V_{sig}} = 741.86$$




(a) $I_C = \alpha I_E = \frac{100}{101} \times 1\text{mA} = 0.99\text{mA}$

$V_C = I_E R_E + 0.7\text{V} + I_B R_B = 1\text{mA} \times 225\Omega + 0.7\text{V} + 0.01\text{mA} \times 200\text{k}\Omega = 2.93\text{V}$

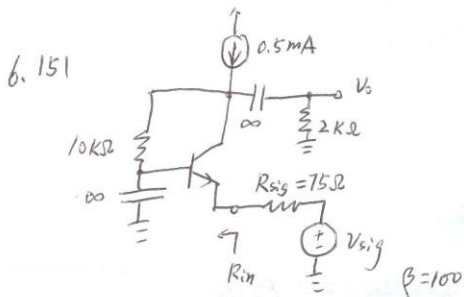(b) $r_e = \frac{V_T}{I_E} = 25\Omega$, $i_e = \frac{V_i}{r_e + R_E} = \frac{V_i}{250\Omega}$

$\frac{V_o - V_i}{R_B} + \frac{V_o}{R_L} = -\alpha i_e = -\frac{\alpha V_i}{250\Omega}$

$\Rightarrow \frac{V_o}{V_i} = \frac{(\frac{1}{R_B} - \frac{\alpha}{250})}{(\frac{1}{R_B} + \frac{1}{R_L})} = -71.92\text{ V/V}$





$R_{in} = r_e = \frac{V_T}{I_E} = \frac{25\text{mV}}{0.5\text{mA}} = 50\Omega$,

$\frac{V_o}{V_s} = \frac{r_e}{R_s + r_e} \cdot g_m (R_B \parallel R_L \parallel Y_o)$

$= \frac{50}{75 + 50} \cdot \frac{0.495\text{mA}}{25\text{mV}} \times (10\text{k}\Omega \parallel 2\text{k}\Omega \parallel 202\text{k}\Omega)$

$I_C = \frac{100}{101} I_E = \frac{100}{101} \times 0.5\text{mA} = 0.495\text{mA}$, $= 13.7\text{ V/V}$

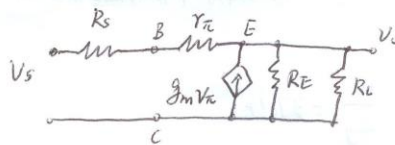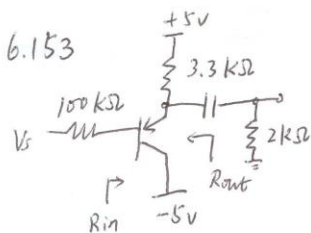$Y_o = 202\text{k}\Omega$, could be ignored



$$I_E = \frac{(5-0.7)V}{3.3k\Omega + 100k\Omega/101} = 1mA, \quad I_C = 0.99mA, \quad g_m = \frac{I_C}{V_T} = 0.0396A/V$$

$$r_e = \frac{V_T}{I_E} = 25\Omega, \quad r_{\pi} = \frac{\beta}{g_m} = 2.525k\Omega, \quad r_o = 101k\Omega$$

$$R_{in} = (\beta + 1) [r_e + (R_E \parallel R_L)] = 101 (0.025 + 1.25) = 128k\Omega$$

$$\frac{V_o}{V_s} = \frac{128}{128 + 100} \cdot \frac{1.25}{1.25 + 0.025} = 0.55V/V$$

$$\frac{i_o}{i_b} = \frac{V_o/R_L}{V_s/(R_s + R_{in})} = \frac{V_o}{V_s} \cdot \frac{R_s + R_{in}}{R_L} = 63.8A/A$$

$$R_{out} = 3.3k\Omega \parallel [r_e + 100/(\beta + 1)] = 0.78k\Omega$$