

5.9  $V_{DS, sat} = V_{GS} - V_t = 2.5V - 1V = 1.5V$

$$I_{D, sat} = \frac{1}{2} k_n (V_{GS} - V_t)^2 = \frac{1}{2} \times \frac{1mA}{V^2} \times (1.5V)^2 = 1.125mA$$

5.17  $r_{DS} = \left[ k_n \frac{W}{L} (V_{GS} - V_t) \right]^{-1} \Rightarrow \frac{r_{DS1}}{r_{DS2}} = \frac{V_{GS2} - V_t}{V_{GS1} - V_t} \Rightarrow V_{GS2} = 3.5V.$

For a device with twice the width:

$$\frac{r_{DS1}}{r_{DS2}} = \frac{W_2 (V_{GS2} - V_t)}{W_1 (V_{GS2} - V_t)}$$


For  $V_{GS} = 1.5V$

$$\frac{r_{DS1}}{r_{DS2}} = 2 \Rightarrow r_{DS2} = \frac{1000}{2} = 500\Omega$$

For  $V_{GS} = 3.5V$

$$r_{DS2} = \frac{200}{2} = 100\Omega$$

5.38

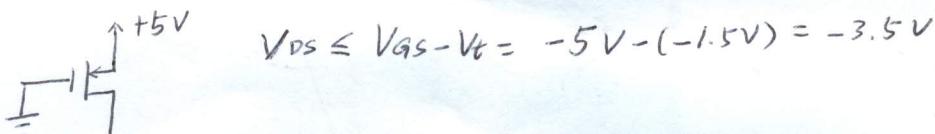

For  $V_D = 4V$ ,  $V_{DS} = -1V > -3.5V \Rightarrow$  triode region

$$I_D = k_p \frac{W}{L} [(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2] = 80 [(-5 - (-1.5)) \times (-1) - \frac{1}{2} \times 1] = 0.24mA$$

For  $V_D = 1.5V$ ,  $V_{DS} = -3.5V = -3.5V \Rightarrow$  edge of saturation

$$I_D = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = \frac{80}{2} (3.5)^2 (1 + 0.02 \times 3.5) = 0.52mA$$


For  $V_D = 0$ ,  $V_{DS} = -5V < -3.5V \Rightarrow$  saturation region

$$I_D = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = \frac{80}{2} (3.5)^2 (1 + 0.02 \times 5) = 0.54mA$$

For  $V_D = -5V$ ,  $V_{DS} = -10V < -3.5V \Rightarrow$  saturation region

$$I_D = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = \frac{80}{2} \times (3.5)^2 (1 + 0.02 \times 10) = 0.59mA$$

5.41

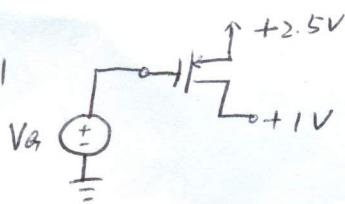

$$V_{SD} = 1.5V$$


$$V_{tp} = -0.5V$$

when  $V_{GS} \geq V_{tp} \Rightarrow V_G \geq 2V$  cutoff

when  $V_{GD} \leq V_{tp} \Rightarrow V_G \leq 0.5V$  triode

when  $-0.5V \leq V_{GS} \leq 2V$  saturation

5.48

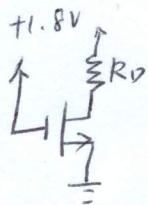


$$V_{GS} = 1.8 \text{ V}$$

$$V_t = 0.5 \text{ V}$$

$$V_{DS, sat} = V_{GS} - V_t = 1.3 \text{ V} \Rightarrow V_D = 1.3 \text{ V}$$

$$R_D = \frac{1.8 \text{ V} - V_D}{I_D} = \frac{(1.8 - 1.3) \text{ V}}{1 \text{ mA}} = 500 \Omega$$

5.49

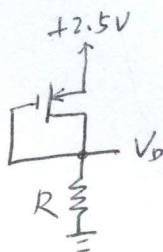

make  $i_D = 0.8 \text{ mA}$  @  $V_D = 1.5 \text{ V}$ .





$$R = \frac{V_D}{i_D} = \frac{1.5 \text{ V}}{0.8 \text{ mA}} = 1.875 \text{ k}\Omega$$

$$V_{SG} = 2.5 \text{ V} - 1.5 \text{ V} = 1 \text{ V}$$

$$i_D = \frac{1}{2} k_m \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.8 \text{ mA} = \frac{1}{2} \times 100 \mu\text{A/V}^2 \times \frac{W}{L} (1 - 0.6)^2 \Rightarrow \frac{W}{L} = 100$$

$$\Rightarrow W = 25 \mu\text{m}$$

5.55.

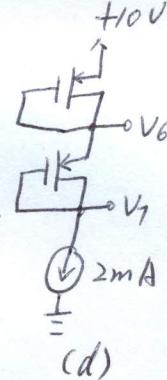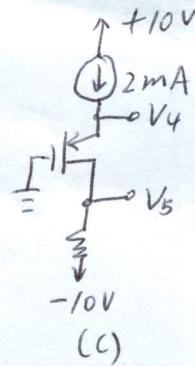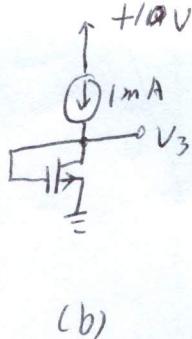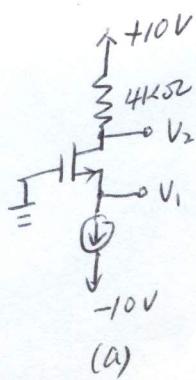

$$\text{In (a), } V_2 = 10 - 4 \times 2 = 2 \text{ V}$$

$$\text{Assume Saturation. } I_D = 2 = \frac{1}{2} \times 1 \times (V_{GS} - 2)^2 \Rightarrow V_{GS} = 4 \text{ V. } V_1 = -4 \text{ V.}$$

$V_{DS} = 6 \text{ V} > V_{GS} - V_t$ , so our assumption was correct.

In (b),

$$I_D = 1 = \frac{1}{2} \times 1 \times (V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.41 \text{ V } V_3 = 3.41 \text{ V.}$$

In (c),

$$I_D = 2 \text{ mA} \Rightarrow V_{GS} = -4 \text{ V} \Rightarrow V_S = 4 \text{ V} = V_4 \quad V_5 = -10 \times 2.5 \times 2 = -5 \text{ V}$$

In (d)

$$I_D = 2 \text{ mA} \Rightarrow V_{GS} = -4 \text{ V} \Rightarrow V_6 = 6 \text{ V. } \Rightarrow V_7 = V_6 - 4 = 2 \text{ V.}$$

If we replace the current source with a resistor in each of those circuits:

In circuit (a):  $R = \frac{-4 - (-10)}{2} \approx 3.01\text{ k}\Omega$  (From the table for 1% resistors)

$$I_D = \frac{1}{2} \times 1 \times (V_{GS} - V_t)^2 \quad V_{GS} - V_t = 0 - (-10 + 3.01 I_D) - 2 = 8 - 3.01 I_D \Rightarrow I_D = 1.99\text{ mA}$$

$$\Rightarrow V_2 = 2.04\text{ V} \quad V_1 = -4.01\text{ V}$$

In (b):  $R = \frac{10 - 3.41}{1} = 6.59\text{ k} \approx 6.65\text{ k}\Omega$

$$V_{GS} = 10 - 6.65I = \frac{1}{2} \times 1 \times (10 - 6.65I - 2)^2 \Rightarrow I = 0.99\text{ mA}$$

$$V_3 = 10 - 6.65 \times 0.99 = 3.41\text{ V}$$

In (c):  $R = \frac{10 - 4}{2} \approx 3.01\text{ k}\Omega, \quad V_{GS} = -(10 + 3.01I)$

$$I = \frac{1}{2} \times 1 \times (-10 + 3.01I + 2)^2 \quad I_D = 1.99\text{ mA}$$

$$V_4 = 10 - 3.01 \times 1.99 = 4.01\text{ V}, \quad V_5 = -10 + 2.5 \times 1.99 = -5.03\text{ V}$$

In (d):  $R = \frac{2}{2} = 1\text{ k} \quad V_1 = 2\text{ V}, \quad V_6 = 6\text{ V}$