
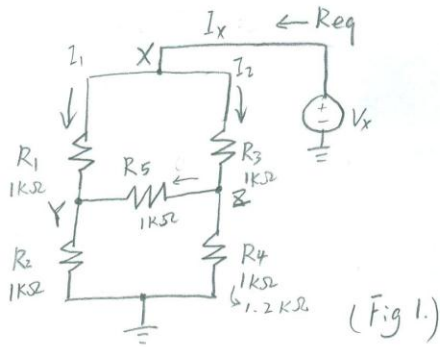


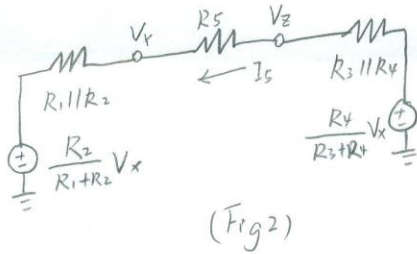1.18 For the symmetric circuit, there's no current in R_5



$$R_{eq} = (R_1 + R_2) \parallel (R_3 + R_4) = 1 \text{ k}\Omega$$

After raising R_4 to $1.2 \text{ k}\Omega$, the circuit is not symmetric any more. There's a current I_5 in R_5 , as shown in Fig 1. Using Thevenin's theorem, we can draw a equivalent circuit in Fig 2.



$$I_5 = \frac{\frac{R_4}{R_3 + R_4} V_x - \frac{R_2}{R_1 + R_2} V_x}{(R_1 \parallel R_2) + R_5 + (R_3 \parallel R_4)} = \frac{(0.545 - 0.5) V_x}{(0.5 + 1 + 0.545) \text{ k}\Omega} = 0.022 V_x$$

$$V_Y = \frac{R_2}{R_1 + R_2} V_x + (R_1 \parallel R_2) \cdot I_5 = 0.511 V_x$$

$$V_Z = V_Y + R_5 \cdot I_5 = 0.533 V_x$$

Back to Fig 1, we can see


$$I_1 = \frac{V_x - V_Y}{R_1} = 0.489 V_x$$

$$I_2 = \frac{V_x - V_Z}{R_3} = 0.467 V_x$$

$$I_x = I_1 + I_2 = 0.956 V_x$$

$$\text{so, } R_{eq} = \frac{V_x}{I_x} = 1.05 \text{ k}\Omega$$

1.23

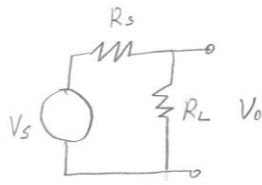


(Fig 3)

$$V_o = \frac{R_L}{R_s + R_L} V_s$$

$$\Rightarrow \begin{cases} 30 \text{ mV} = \frac{100 \text{ k}\Omega}{R_s + 100 \text{ k}\Omega} V_s \\ 10 \text{ mV} = \frac{10 \text{ k}\Omega}{R_s + 10 \text{ k}\Omega} V_s \end{cases} \Rightarrow \begin{cases} R_s = 28.6 \text{ k}\Omega \\ V_s = 38.6 \text{ mV} \end{cases}$$

$$i_s = \frac{V_s}{R_s} = 1.35 \mu\text{A}$$

1.41

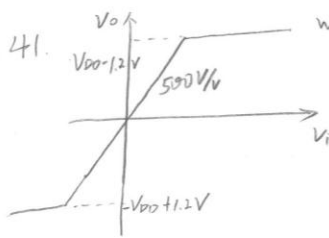

(Fig 4)

When $V_{DD} = 5\text{V}$, peak amplitude: $5\text{V} - 1.2\text{V} = 3.8\text{V}$ or $3.8/\sqrt{2} = 2.7\text{V}_{\text{rms}}$

$$\text{input: } \frac{3.8\text{V}}{500\text{V/V}} = 7.6\text{mV} \text{ or } 5.4\text{mV}_{\text{rms}}$$


When $V_{DD} = 10\text{V}$, peak amplitude: $10\text{V} - 1.2\text{V} = 8.8\text{V}$ or $8.8/\sqrt{2} = 6.2\text{V}_{\text{rms}}$

$$\text{input: } \frac{8.8\text{V}}{500\text{V/V}} = 17.6\text{mV} \text{ or } 12.4\text{mV}_{\text{rms}}$$

When $V_{DD} = 15\text{V}$, peak amplitude: $15\text{V} - 1.2\text{V} = 13.8\text{V}$ or $13.8/\sqrt{2} = 9.8\text{V}_{\text{rms}}$

$$\text{input: } \frac{13.8\text{V}}{500\text{V/V}} = 27.6\text{mV} \text{ or } 19.6\text{mV}_{\text{rms}}$$

1.43

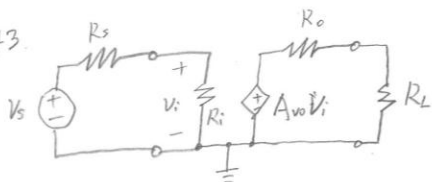

from figure 1.16 (b) "Sedra/Smith Micro-Circuits"

$$A_{v0} = 10\text{V/V}, \quad \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} \cdot A_{v0} \cdot \frac{R_L}{R_L + R_o}$$

$$(a) R_i = 10R_s, R_L = 10R_o$$

$$\frac{V_o}{V_s} = \frac{10R_s}{10R_s + R_s} \cdot 10\text{V/V} \cdot \frac{10R_o}{10R_o + R_o} = 8.26\text{V/V}$$

$$20 \log 8.26 = 18.3\text{dB}$$

$$(b) R_i = R_s, R_L = R_o$$

$$\frac{V_o}{V_s} = \frac{R_s}{R_s + R_s} \cdot 10\text{V/V} \cdot \frac{R_o}{R_o + R_o} = 2.5\text{V/V}$$

$$20 \log 2.5 = 8\text{dB}$$

$$(c) R_i = R_s/10, R_L = R_o/10$$

$$\frac{V_o}{V_s} = \frac{R_s/10}{R_s/10 + R_s} \cdot 10\text{V/V} \cdot \frac{R_o/10}{R_o/10 + R_o} = 0.083\text{V/V}$$

$$20 \log 0.083 = -21.6\text{dB}$$

1.45

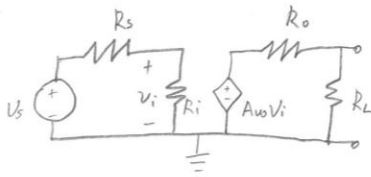


Fig 5 (a)

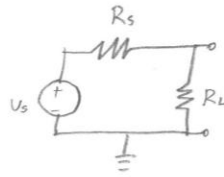


Fig 5 (b)

In Fig 5 (a),

$$\frac{v_o}{v_s} = \frac{R_i}{R_i + R_s} \cdot A_{vo} \cdot \frac{R_L}{R_L + R_o} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 100 \text{ k}\Omega} \times 1000 \text{ V/V} \times \frac{100 \Omega}{100 \Omega + 1 \text{ k}\Omega} = 8.26 \text{ V/V}$$

$1 - \frac{R_i}{R_i + R_s} \approx 90\%$ The signal loses 90% of its strength when it passes through the Amp.
 $1 - \frac{R_L}{R_L + R_o} \approx 90\%$ Then it loses 90% of its rest strength after passing the load.

In Fig 5 (b),

$$\frac{v_o}{v_s} = \frac{R_L}{R_L + R_s} = \frac{100 \Omega}{100 \Omega + 100 \text{ k}\Omega} \approx 0.001 \text{ V/V} \text{ even worse}$$

$$\text{Ratio: } \frac{8.26 \text{ V/V}}{0.001 \text{ V/V}} = 8260$$