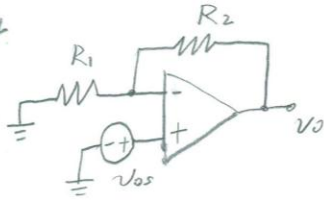


2.94



(Fig 1)


$$V_o = V_{0S} \left(1 + \frac{R_2}{R_1}\right)$$

$$\Rightarrow V_{0S} = \frac{V_o}{1 + \frac{R_2}{R_1}} = \frac{0.4V}{1 + \frac{100K\Omega}{1K\Omega}} \approx 4mV$$

2.95

$$V_o = 0.01 \sin \omega t \times 200 \pm 2mV \times 200 = 2 \sin \omega t \pm 0.4V$$

2.99

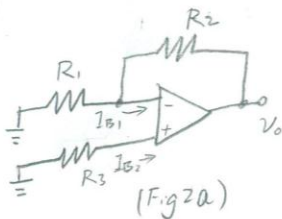

(Fig 2a)

$$10V/V = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = \frac{1}{9} R_2 = \frac{100}{9} K\Omega$$

$$\begin{cases} I_{B1} + I_{B2} = 2\mu A \\ I_{B1} - I_{B2} = \pm 0.1\mu A \end{cases} \Rightarrow \begin{cases} I_{B1} = 1 \pm 0.05\mu A \\ I_{B2} = 1 \pm 0.05\mu A \end{cases}$$

$$\text{For } I_{B1} = 0.95\mu A \text{ \& } I_{B2} = 0.95\mu A, V_o = -I_{B2}R_3 + R_2 \left(I_{B1} - I_{B2} \frac{R_3}{R_1} \right) = 57.5mV$$


$$\text{For } I_{B1} = 0.95\mu A \text{ \& } I_{B2} = 1.05\mu A, V_o = -I_{B2}R_3 + R_2 \left(I_{B1} - I_{B2} \frac{R_3}{R_1} \right) = 42.5mV$$

$$\Rightarrow 42.5mV \leq V_o \leq 57.5mV$$


The negative input terminal sees a resistance of $R_1 || R_2 = 10K\Omega$. To get the minimum dc output voltage, we need to make the resistance seen at the positive input terminal equal to that in the negative terminal.

So we should add $5K\Omega$ series resistor R_4 in the positive input terminal.

$$\begin{aligned} \text{(Fig 2b), } V_o &= -I_{B2} \times (5K\Omega + 5K\Omega) + 100K\Omega \times \left(I_{B1} - I_{B2} \times \frac{10K\Omega}{100/9 K\Omega} \right) = (I_{B1} - I_{B2}) \times 100 \\ &= 10\mu \times 100 = \pm 10mV \end{aligned}$$

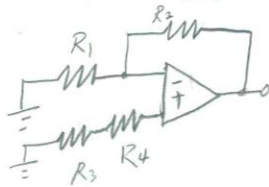

(Fig 2b)

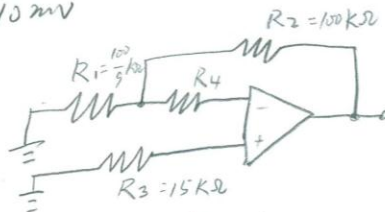

(Fig 2c)

$$\text{For the same reason, } (R_1 || R_2) + R_4 = R_3 \Rightarrow R_4 = 5K\Omega$$

2.104 (a) $1 + \frac{R_2}{R_1} = 100 \Rightarrow R_1 = 10.1 \text{ k}\Omega$


$V_0 = I_B \times R_2 = 100 \text{ nA} \times 1 \text{ M}\Omega = 0.1 \text{ V}$

(b) $V_0 = 1 \text{ mV} \times 100 + 0.1 \text{ V} = 0.2 \text{ V}$

(c) As shown in Fig 2a, $R_3 = R_1 \parallel R_2 = 10.1 \text{ k}\Omega \parallel 1 \text{ M}\Omega \approx 10 \text{ k}\Omega$

output offset voltage: $I_{os} \cdot R_2 = 10 \text{ nA} \times 1 \text{ M}\Omega = 10 \text{ mV}$

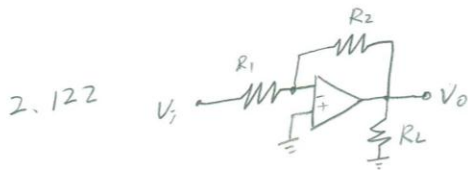(d) $V_0 = 1 \text{ mV} \times 100 + 10 \text{ mV} = 110 \text{ mV}$



(a) $R_1 = 1 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_L = 1 \text{ k}\Omega$

$V_{p, \text{max}} = \frac{10 \text{ V}}{100 \text{ V/V}} = 0.1 \text{ V}$, here $i_o = \frac{10 \text{ V}}{R_L} + \frac{10 \text{ V}}{R_2} = 10.1 \text{ mA} < 20 \text{ mA}$

(b) $R_L = 100 \Omega$

if $V_p = 0.1 \text{ V}$ $i_o = \frac{10 \text{ V}}{R_L} + \frac{10 \text{ V}}{R_2} > 20 \text{ mA}$

so let $i_o = 20 \text{ mA}$, $i_o = \frac{V_o}{R_L} + \frac{V_o}{R_2} \Rightarrow V_o = 2 \text{ V} \Rightarrow V_p = \frac{2 \text{ V}}{100 \text{ V/V}} = 20 \text{ mV}$

(c) $i_o = \frac{V_o}{R_L} + \frac{V_o}{R_2}$ $V_o = 10 \text{ V}$, $R_2 = 100 \text{ k}\Omega$



$R_{L, \text{min}} = \frac{V_o}{i_{o, \text{max}} - \frac{V_o}{R_2}} = \frac{10 \text{ V}}{20 \text{ mA} - \frac{10 \text{ V}}{100 \text{ k}\Omega}} = 502.5 \Omega$

2.126 $v_o = 10 \sin \omega t$ $\frac{dv_o}{dt} = 10 \omega \cos \omega t$

slew rate = $\left. \frac{dv_o}{dt} \right|_{\text{max}} = 60 \text{ V}/\mu\text{s} = 10 \omega_{\text{max}}$ $\omega_{\text{max}} = 6 \times 10^6 \text{ rad/s}$

$f_{\text{max}} = \frac{\omega}{2\pi} = 0.956 \text{ MHz}$

4.9

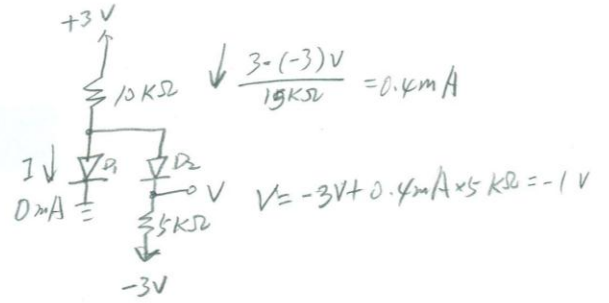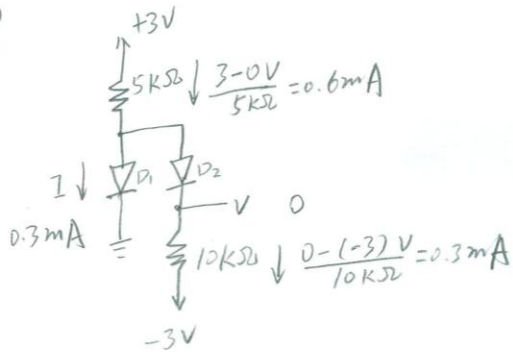

4.16

