

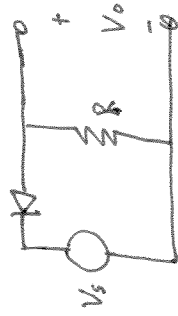


4.65

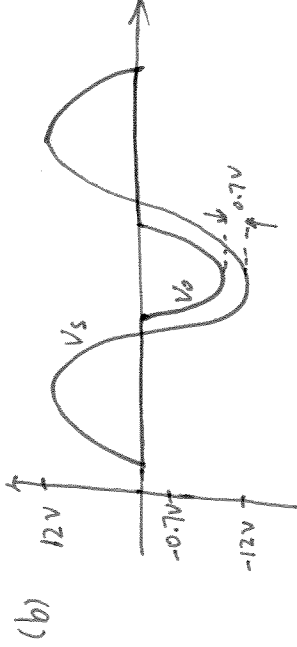

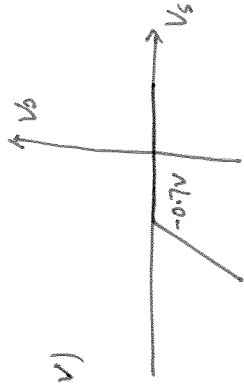(A)  $V_o = V_s + 0.7V$  ( $V_s \leq +0.7V$ )  
 $V_o = 0$  ( $V_s \geq +0.7V$ )



(c)  $\theta = \sin^{-1}\left(\frac{0.7}{12}\right) = 3.34^\circ$   
 $\pi - \theta = 176.65^\circ$

}  $\Rightarrow$  The diode conducts ( $3.34^\circ \sim 176.65^\circ$ )  
 $\Rightarrow$  conduction angle is  $\pi - 2\theta = 173.31^\circ$  or  $3.025$  rad


$$V_{o,avg} = \frac{-1}{2\pi} \int_{\theta}^{\pi-\theta} (12 \sin\phi - 0.7) d\phi$$

$$= \frac{-1}{2\pi} [12 \times 2.0080 - 0.7(\pi - 2\theta)] = -3.98V$$

(d) Peak current in the diode:  $\frac{12 - 0.7V}{1.5 \times 10^{-3} \Omega} = 7.53 \text{ mA}$

(e) PIV = 12V (PIV occurs when  $V_s$  is at its peak &  $V_o = 0V$ )

4.70

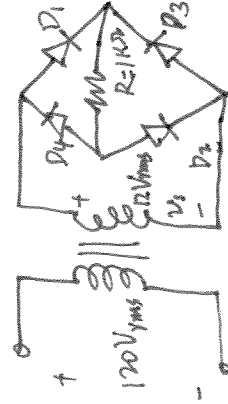

Peak voltage across the load =  $12\sqrt{2} - 2V_D = 15.57V$

$$\theta = \sin^{-1} \frac{1.4}{12\sqrt{2}} = 0.0826 \text{ rad}$$

Fraction of cycle that  $D_1$  &  $D_2$  conduct:

$$\frac{\pi - 2\theta}{2\pi} = 47.4\% \text{ which is the same as } D_3 \text{ \& } D_4$$

$\Rightarrow$  For each diode, the fraction of cycle ... is 23.7%

The average voltage across the load:

$$V_{o, \text{avg}} = \frac{2}{2\pi} \int_0^{\pi-\theta} (12\sqrt{2} \sin\phi - 2V_o) d\phi = \frac{1}{\pi} [-12\sqrt{2} \cos\phi - 1.4\phi]_0^{\pi-\theta} = 9.44 \text{ V}$$

$$i_{R, \text{avg}} = \frac{V_{o, \text{avg}}}{R} = \frac{9.44 \text{ V}}{1 \text{ k}\Omega} = 9.44 \text{ mA}$$

4.77 i)  $V_r = 0.1 (V_p - V_o \times 2) = \frac{V_p - 2V_o}{2fCR}$  discharge occurs over  $\frac{1}{2}T = \frac{1}{2f}$

$$C = \left( \frac{V_p - 2V_o}{V_p - 2V_o} \right) \frac{1}{2(0.1)fR} = 83.3 \text{ }\mu\text{F}, \quad V_{\text{avg}} = V_p - \frac{1}{2}V_r = 14.86 \text{ V}$$

ii)  $C = \left( \frac{V_p - 2V_o}{V_p - 2V_o} \right) \frac{1}{2(0.01)fR} = 833 \text{ }\mu\text{F},$

$$V_{\text{avg}} = V_p - \frac{1}{2}V_r = 15.49 \text{ V}$$

(b) (i) Fraction of cycle:  $\frac{2W\Delta t}{2\pi} = 14.2\%$   
 (ii) Fraction of cycle:  $\frac{2W\Delta t}{2\pi} = \sqrt{\frac{2(0.01)}{\pi}} = 4.5\%$


(c) (i)  $i_{D, \text{avg}} = \frac{14.79}{1} (1 + \pi\sqrt{\frac{1}{0.2}}) = 119 \text{ mA}$

(ii)  $i_{D, \text{avg}} = \frac{15.49}{1} (1 + \pi\sqrt{\frac{1}{0.2}}) = 356 \text{ mA}$

(d)  $i_D = \frac{14.79}{1} (1 + 2\pi\sqrt{\frac{1}{0.2}}) = 223 \text{ mA}$

$i_D = \frac{15.49}{1} (1 + 2\pi\sqrt{\frac{1}{0.2}}) = 704 \text{ mA}$

4.83.

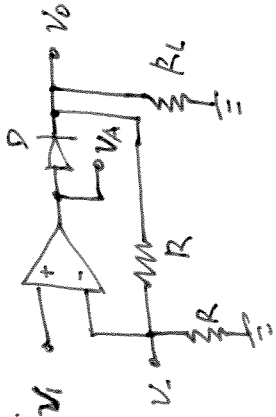

$$V_0 = V_1 \left(1 + \frac{R}{R}\right) = 2V_1$$

(a)  $V_1 = +1V$   $V_0 = 2V$ ,  $V_A = 2.7V$ ,  $V_0 = V_1 = 1V$


(b)  $V_1 = 2V$   $V_0 = 4V$ ,  $V_A = 4.7V$ ,  $V_0 = 2V$

(c)  $V_1 = -1V$   $V_A = -1.2V$  diode is cut off


$$V_0 = 0V \quad V_0 = 0V$$

(d)  $V_1 = -2V$   $V_A = -1.2V$  diode is cut off


$$V_0 = 0V \quad V_0 = 0V$$

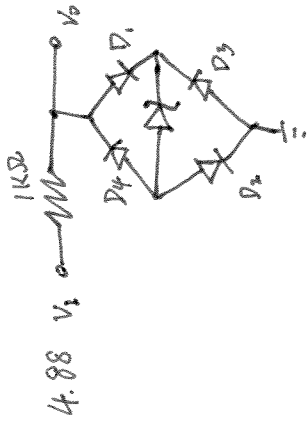

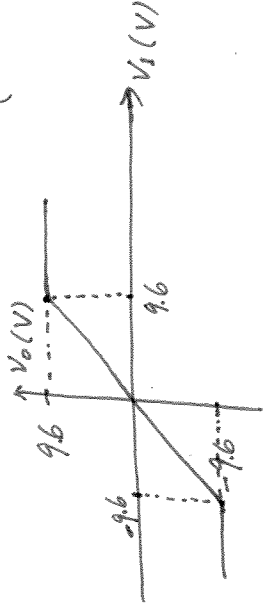
The limited thresholds are  $\pm(0.7 \times 2 + 8.2) = \pm 9.6V$




4.90 (a)  $-0.7V$  and above

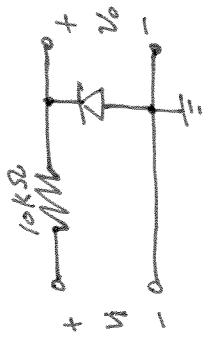


(b)  $-2.1V$  and above

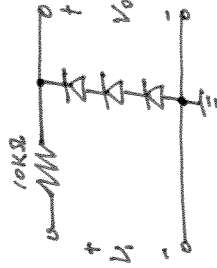

(c)  $\pm 1.4V$

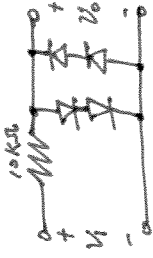

4.93.

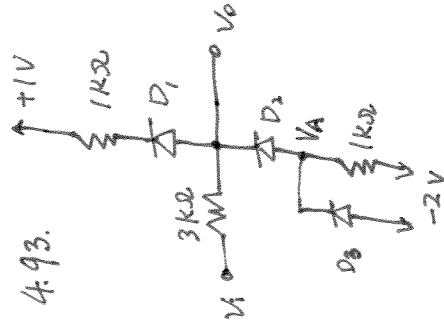

For current  $i_{D1} > 1mA$

$$V_{D1} \approx 0.7V \quad \text{let } V_{D1} = 0.71V \Rightarrow V_1 > 5.7V$$

$$V_0 = 1.71 + 1k \times i_{D1} = \frac{V_1}{4} + 1.2825 \quad \text{slope is } 1/4.$$

for  $V_1 > 5.7V$

$V_1 (V)$	5.8	6	7	8	9	10
$V_0 (V)$	2.7325	2.7825	3.0325	3.2825	3.5325	3.7825

For  $-10 \leq V_1 \leq 6V$ , Diode exhibit a 0.7V drop at  $i_D = 1mA$

$$i_D = I_S e^{V_D/V_T} \quad I_S = \frac{i_D}{V_D/V_T} = \frac{1 \times 10^{-3} A}{0.7V/0.025V} = 6.91 \times 10^{-16} A$$

when  $V_1 > 0$ , diode  $D_2$  does NOT conduct, so  $i_{D2} = 0$

$$V_{D1} = V_T \ln\left(\frac{i_{D1}}{I_S}\right), \quad V_0 = V_{D1} + 1K \times i_{D1}, \quad V_1 = (3K + 1K) i_{D1} + V_{D1}$$

$i_{D1}$ (A)	$10^{-10}$	$10^{-6}$	$10^{-5}$	$10^{-4}$	$10^{-3}$	$0.2 \times 10^{-2}$	$0.5 \times 10^{-2}$
$V_{D1}$ (V)	0.297	0.527	0.584	0.642	0.7	0.717	0.74
$V_0$ (V)	1.297	1.528	1.595	1.742	2.7	2.717	5.74
$V_1$ (V)	~1.297	1.5313	1.625	2.042	5.7	8.717	20.74

when  $V_1 < -2.5$

$$V_{D3} = V_A + 2, \quad i_{D3} = I_S e^{V_{D3}/V_T}, \quad i_{D2} = i_{D3} + \frac{V_A + 2}{1K\Omega}, \quad V_{D2} = V_T \ln\left(\frac{i_{D2}}{I_S}\right)$$

$$V_0 = V_A - V_{D2}, \quad V_1 = V_0 - 3K\Omega \times i_{D2}$$


$V_A$ (V)	-2.001	-2.10	-2.2	-2.5	-2.7	-2.71
$i_{D3}$ (A)	$7.2 \times 10^{-16}$	$3.8 \times 10^{-14}$	$2.1 \times 10^{-13}$	$33.5 \times 10^{-8}$	$18 \times 10^{-6}$	$1 \times 10^{-3}$
$i_{D2}$ (A)	$10 \times 10^{-6}$	$10^{-4}$	$0.2 \times 10^{-3}$	$0.5 \times 10^{-3}$	$0.6 \times 10^{-3}$	$1.7 \times 10^{-3}$
$V_{D2}$ (V)	0.527	0.585	0.642	0.659	0.682	0.713
$V_0$ (V)	-2.528	-2.595	-2.724	-3.128	-3.287	-3.443
$V_1$ (V)	-2.531	-2.625	-3.024	-4.628	-5.087	-8.516

A: for a small  $i_{D2}$ ,  $D_3$  is off and  $D_2$  is on,  $i_2$  flows through  $1K\Omega$  resistor

B:  $D_3$  starts conducting when there's 0.5V drop across  $D_3$ .

C:  $V_A = 2.7V$ .

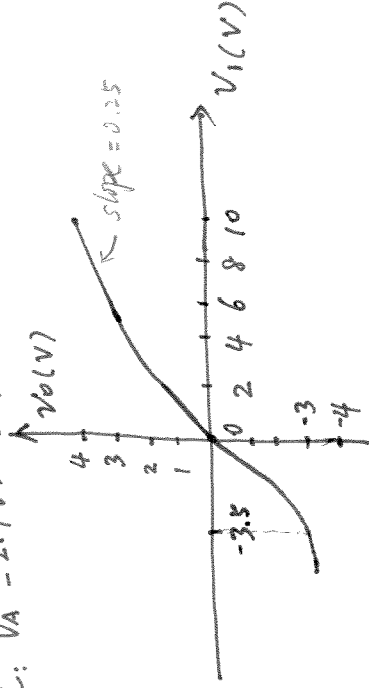0.7V across  $D_3$  and  $D_3$  controls  $i_{D2}$



4.94.



⇒



⇒



$10\text{ V rms}$

$10\sqrt{2}\text{ V, peak}$

Average (dc) voltage of output :  $10\sqrt{2}\text{ V} = 14.14\text{ V}$