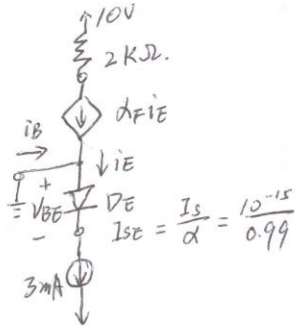


6.13.  $i_c = I_s e^{V_{BE}/V_T} = (5 \times 10^{-15}) e^{0.650/0.025} = 977 \mu A$

$i_B = \frac{i_c}{\beta}$  from  $\frac{i_c}{\beta} = \frac{977 \times 10^{-6}}{50} = 19.6 \mu A$  to  $\frac{i_c}{\beta} = \frac{977 \times 10^{-6}}{200} = 4.89 \mu A$

$i_E = \frac{\beta+1}{\beta} i_c$  from  $\frac{\beta+1}{\beta} i_c = \frac{51}{50} \times 977 \times 10^{-6} = 998 \mu A$  to  $\frac{\beta+1}{\beta} i_c = \frac{201}{200} \times 977 \times 10^{-6} = 983 \mu A$

6.17.




$\beta = 100, I_s = 10^{-15} \Rightarrow \alpha = \frac{100}{101} = 0.99$

$I_E = I_S e^{V_{BE}/V_T} \Rightarrow 3 \times 10^{-3} = \frac{10^{-15}}{0.99} e^{V_{BE}/0.025} \Rightarrow V_{BE} = 0.718 V$

$V_E = 0 - 0.718 = -0.718 V$

$i_C = \alpha I_E = 0.99 \times 3 mA, V_C = 10 - 2 i_C = 10 - 2 \times 0.99 \times 3 = 4.06 V$

6.25.

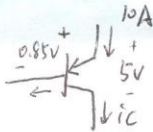


$I_E = (\beta+1) I_B \Rightarrow 10 A = (15+1) I_B \Rightarrow I_B = 0.625 A$

$i_C = \frac{\beta}{\beta+1} I_E = I_S e^{V_{BE}/V_T} \Rightarrow \frac{15}{16} \times 10 = I_S e^{0.85/0.025} \Rightarrow I_S = 1.6 \times 10^{-16} A$

$I_{S2} = i_C e^{-V_{BE}/V_T} = 10^{-3} e^{-0.7/0.025} = 6.9 \times 10^{-16}$


$\frac{Area_1}{Area_2} = \frac{I_{S1}}{I_{S2}} = \frac{1.6 \times 10^{-16} A}{6.9 \times 10^{-16} A} = 23.3$

6.28 (a)

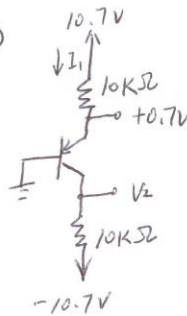


$I_1 = \frac{10.7 - 0.7}{10 k\Omega} = 1 mA$

$V_2 = -0.7 V$

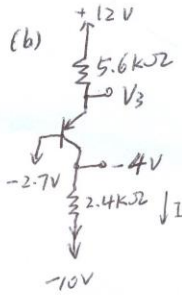

$I = \frac{-4 + 10}{2.4} = 2.5 mA$


$V_3 = 12 - 5.6 \times 2.5 = -2 V$

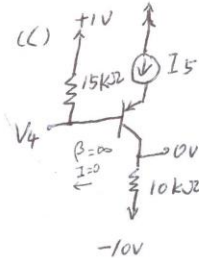

$I_5 = \frac{0 - (-10)V}{10 k\Omega} = 1 mA$

$V_4 = 1V - 0V = 1V$

P<sub>i</sub>

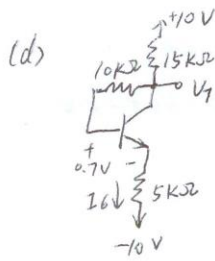


$$I_E = I_C \quad V_B = 0$$


$$\frac{V_B - 0.7V + 10V}{5k\Omega} = \frac{10 - V_E}{15k\Omega}$$

$$\Rightarrow V_T = V_E = -4.475V$$
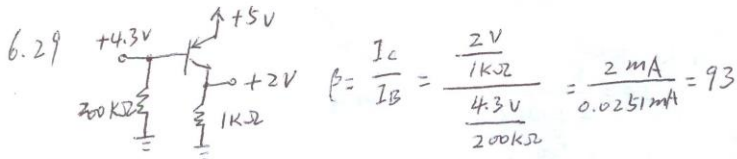
$$I_B = \frac{V_T - 0.7V + 10V}{5k\Omega} = 0.965mA$$



(a)

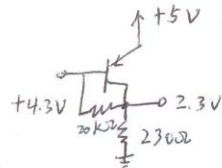


(b)

$$(I_C + I_B) \times 230\Omega = 2.3V$$

$$I_B = \frac{4.3V - 2.3V}{20k\Omega} = 0.1mA$$
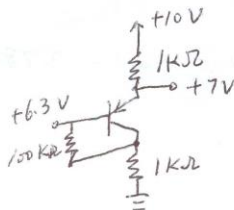
$$\Rightarrow \beta = \frac{I_C}{I_B} = \frac{10mA - 0.1mA}{0.1mA} = 99$$



(c)


$$I_E = I_B + I_C = \frac{10V - 7V}{1k\Omega} = 3mA$$

$$V_C = 3mA \times 1k\Omega = 3V$$

$$I_B = \frac{6.3V - 3V}{100k\Omega} = 33\mu A$$

$$1 + \beta = \frac{I_E}{I_B} = \frac{3mA}{33\mu A} = 90.9 \Rightarrow \beta = 89.9$$

6.53

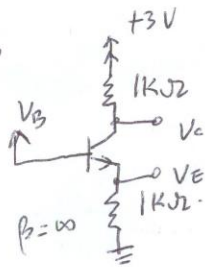

maximum  $V_B = V_C$ , assume  $V_{BE} = 0.8V$  or  $V_{BE} = 0.7V$

$$V_E = V_B - V_{BE} = V_B - 0.8V \quad V_B = V_E + 0.8V$$

$$V_E = I_E \times (1K\Omega)$$

for high  $\beta \Rightarrow I_E = I_C$

$$3 - I_C \times (1K) = V_C$$

$$I_C(1K) + 0.8V = V_B$$

$$V_C = V_B$$

$$\Rightarrow I_C = 1.1mA$$


$$V_C = V_B = 3 - 1.1m(1K) = 1.9V$$

With  $\beta = 1$   $I_C = I_B \Rightarrow I_E = I_C + I_B = 2I_C$   $2 \left( \frac{-V_C + 3}{1K\Omega} \right) = \frac{V_E}{1K}$   $\Rightarrow V_E = 1.9V$

$$V_{CE} = 0.2$$

$$V_B = 1.9V + 0.8V = 2.7V \quad \text{or } V_B = 1.9V + 0.7V = 2.6V$$

6.59

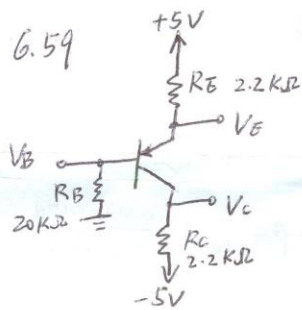

for  $R_B = 20K\Omega$

$$I_E = \frac{5 - 0.7}{2.2 + 20/51} = 1.66mA$$

$$I_C = I_E \frac{50}{51} = 1.63mA$$

$$V_C = -5 + 2.2 \times 1.63 = -1.42V$$

$$V_E = +5 - 2.2 \times 1.66 = +1.35V$$

$$V_B = V_E - 0.7 = -0.65V$$


for  $R_B = 100K\Omega$

$$I_E = \frac{5 - 0.7}{2.2 + 100/51} = 1.03mA, \quad V_E = 5 - 1.03 \times 2.2 = +2.73V$$

$$V_B = 0 + \frac{1.03}{51} \times 100 = +2.03V, \quad V_C = -5 + 1.03 \times \frac{50}{51} \times 2.2 = -2.78V$$

for same  $I_B$ :  $\beta = 51 \times \frac{100}{20} - 1 = 255$

6.72

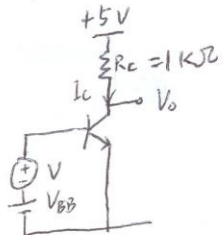

For  $I_C \approx 0.5mA$

$$A_V = \frac{I_C R_C}{V_T} = \frac{0.5}{0.025} = 20 V/V$$

$$V_{CE} = V_{CC} - I_C R_C = 5 - 0.5 = 4.5V$$

$$\text{max } +\Delta V_o = 5 - 4.5 = 0.5V$$

$$\text{min } -\Delta V_o = 0.3 - 4.5 = -4.2V$$

$I_C (mA)$	$A_V (V/V)$	$+\Delta V_o$	$-\Delta V_o$
0.5	-20	0.5	4.2
1.0	-40	1.0	3.7
2.5	-100	2.5	2.2
4.0	-160	4.0	0.7
4.5	-180	4.5	0.2