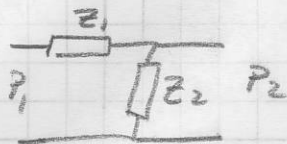


# Problem 1



Part a) S-parameters:

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \rightarrow \text{Port 2 terminated with } Z_0$$

$$\Rightarrow Z_{in} = Z_1 + (Z_2 \parallel Z_0)$$

$$S_{11} = \frac{Z_1 + (Z_2 \parallel Z_0) - Z_0}{Z_1 + (Z_2 \parallel Z_0) + Z_0} = \frac{(Z_1 - Z_0)(Z_2 + Z_0) + Z_2 Z_0}{(Z_1 + Z_0)(Z_2 + Z_0) + Z_2 Z_0}$$

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+ = 0} \rightarrow \text{Port 1 terminated with } Z_0$$

$$Z_{in} = Z_2 \parallel (Z_1 + Z_0)$$

$$S_{22} = \frac{[Z_2 \parallel (Z_1 + Z_0)] - Z_0}{[Z_2 \parallel (Z_1 + Z_0)] + Z_0} = \frac{Z_2(Z_1 + Z_0) - Z_0(Z_1 + Z_2 + Z_0)}{Z_2(Z_1 + Z_0) + Z_0(Z_1 + Z_2 + Z_0)}$$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} \quad V_2 = V_2^- + V_2^+ \rightarrow V_2^+ = 0 \Rightarrow V_2 = V_2^-$$

Part 2 terminated with \$Z\_0\$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{V_2}{V_1} \cdot \frac{V_1}{V_1^+}$$

$$\frac{V_2}{V_1} = \frac{Z_2 \parallel Z_0}{Z_1 + (Z_2 \parallel Z_0)} = \frac{Z_2 Z_0}{Z_1(Z_2 + Z_0) + Z_2 Z_0}$$

$$\frac{V_1}{V_1^+} = \frac{V_1^+ + V_1^-}{V_1^+} = \frac{V_1^+ (1 + S_{11})}{V_1^+} = 1 + S_{11}$$

$$S_{21} = [1 + S_{11}] \frac{Z_2 Z_0}{Z_1(Z_2 + Z_0) + Z_2 Z_0}$$

$$S_{12} = S_{21} \text{ by reciprocity}$$

Part b)

$$Z_1 = 30 \Omega, Z_2 = 75 \Omega, Z_0 = 50 \Omega$$

$$S_{11} = \frac{(30 - 50)(75 + 50) + 75 \cdot 50}{(30 + 50)(75 + 50) + 75 \cdot 50} = 0.0909$$

$$S_{22} = -0.1273, \quad S_{21} = 0.5455, \quad S_{12} = 0.5455$$

$$S = \begin{bmatrix} 0.0909 & 0.5455 \\ 0.5455 & -0.1273 \end{bmatrix}$$

Part c)

Port 2 terminated in  $50\Omega (= Z_0)$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\Gamma = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0 \text{ for } Z_L = Z_0$$

$$\Rightarrow |\Gamma| = 0.0909$$

$$\underline{VSWR = 1.2}$$


## Problem 2

Part a) Reciprocal? Yes -  $S = S^T$ .

Part b) Input return loss:

$$RL = -20 \log_{10} |\Gamma| \quad (\text{dB})$$

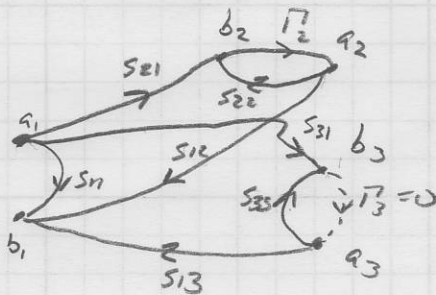$\Gamma = b_1/a_1 \rightarrow$  Flow graph approach:



$$\Gamma_2 = \frac{0 - Z_0}{0 + Z_0} = -1 \quad (\text{short})$$

$$\Gamma_3 = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0 \quad (\text{open})$$

First-order loops:  $\Gamma_2 S_{22}$

$T = b_1/a_1 \rightarrow$  Paths:  $S_{11}$ ,  $S_{21} \Gamma_2 S_{12}$

$$T = \frac{b_1}{a_1} = \frac{S_{11} [1 - \Gamma_2 S_{22}] + S_{21} \Gamma_2 S_{12}}{1 - \Gamma_2 S_{22}} = S_{11} + \frac{S_{21} \Gamma_2 S_{12}}{1 - \Gamma_2 S_{22}} = 0.0174$$
$$= 0.00536 - j0.0166 = 0.0174 \angle -72^\circ$$

$$RL = -20 \log_{10} 0.0174 = -35.2 \text{ dB}$$

Part c) Input impedance?

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow \Gamma(Z_{in} + Z_0) = Z_{in} - Z_0$$
$$Z_{in} = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$


$$\Gamma = 0.0174 \angle -72^\circ$$

$$\Rightarrow Z_{in} = 50.5 - j1.68 \Omega = 50.53 \angle -1.9^\circ$$

### Problem 3

Shunt-stab matching network:

All lines have  
 $Z_0 = 50 \Omega$

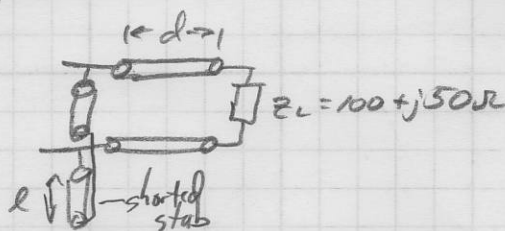

$$\Rightarrow z_L = \frac{Z_L}{Z_0} = 2 + j$$

$$y_L = \frac{1}{z_L} = 0.4 - j0.2$$

Terminated line input impedance:

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d}$$

normalized:

$$z_{in} = \frac{z_L + j \tan \beta d}{1 + j z_L \tan \beta d}$$

$$y_{in} = \frac{1 + j z_L \tan \beta d}{z_L + j \tan \beta d}$$

At end of "d" line,  $y_{in} = 1 + jb$

$$\Rightarrow 1 + jb = \frac{1 + j(2+j) \tan \beta d}{2 + j + j \tan \beta d}$$

$$(1 + jb)(2 + j(1 + \tan \beta d)) = 1 - \tan \beta d + j2 \tan \beta d$$

Real part:

$$2 - b(1 + \tan \beta d) = 1 - \tan \beta d$$

Imag. part:

$$j2b + j(1 + \tan \beta d) = j2 \tan \beta d$$

2 eq., 2 unknowns ( $b, \tan \beta d$ )

From Imag. part:  $b = \frac{\tan \beta d - 1}{2}$

From Imag. part:

$$2 - \frac{\tan \beta d - 1}{2} (1 + \tan \beta d) = 1 - \tan \beta d$$

$$\frac{5}{2} - \frac{1}{2} \tan^2 \beta d = 1 - \tan \beta d$$

$$\frac{1}{2} \tan^2 \beta d - \tan \beta d - \frac{3}{2} = 0$$

$$\tan \beta d = \frac{1 \pm \sqrt{1 + 4 \cdot \frac{1}{2} \cdot \frac{3}{2}}}{1} = 1 \pm 2 = -1, 3.$$

Two solutions

$$\tan \beta d = 3 \rightarrow b = 1$$

$$\tan \beta d = -1 \rightarrow b = -1$$



$$\tan \beta d = 3 \rightarrow \text{atan } 3 = \beta d = \frac{2\pi}{\lambda} d$$

$$\hookrightarrow \frac{d}{\lambda} = \frac{\text{atan } 3}{2\pi} = 0.199$$

$$\tan \beta d = -1 \rightarrow \frac{d}{\lambda} = -0.125 \Rightarrow \frac{d}{\lambda} = 0.375 \text{ for length } > 0$$

(periodic  $\forall$  period  $\lambda/2$ )

Stub design:

$$y_{in} = 1 + jb \rightarrow \text{so stub provides } -jb$$

$$y_{in \text{ stub}} = \frac{1 + j \tan \beta l}{z_t + j \tan \beta l}, \quad z_t = \text{stub termination impedance}$$

$$\text{short: } z_t = 0$$

$$y_{in \text{ stub}} = \frac{1}{j \tan \beta l}$$

$$\text{For } d = 0.199\lambda \rightarrow b = +1 \Rightarrow y_{in \text{ stub}} = -j \rightarrow \tan \beta l = 1$$

$$l = 0.125\lambda$$

$$\text{For } d = 0.375\lambda, b = -1 \rightarrow y_{in \text{ stub}} = +j \rightarrow \tan \beta l = -1$$

$$l = -0.125 + 0.5 = 0.375\lambda$$

Solutions:

$$d_1 = 0.199\lambda, \quad l_1 = 0.125\lambda$$

OR

$$d_2 = 0.375\lambda, \quad l_2 = 0.375\lambda$$

Bonus

match  $150\Omega$  to  $50\Omega$  with series line

$\rightarrow \lambda/4$  transformer

$$Z_1 = \sqrt{Z_0 \cdot Z_L} = \sqrt{50 \cdot 150} = 86.6\Omega$$

$$\text{length} = \lambda/4$$

For lines available,

$$R=0, G=0 \rightarrow \text{lossless}$$

$$L = 8 \text{ nH/cm}$$

$$C = ?$$

$$Z_1 = 86.6\Omega = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L}{C}} \text{ for } R, G=0$$

$$\Rightarrow C = \frac{L}{Z_1^2} = 1.07 \text{ pF/cm} = C$$

Length of  $\lambda/4$  transformer? (in physical units, e.g. cm)

$$\text{Propagation constant } \gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = \alpha + j\beta$$

$$R, G=0 \rightarrow \gamma = j\beta = j\omega\sqrt{LC}$$

$$\beta = \omega\sqrt{LC} = \frac{2\pi}{\lambda}$$

$$\lambda = \frac{2\pi}{\omega\sqrt{LC}} = \frac{1}{f\sqrt{LC}}$$

$$f = 10 \text{ GHz}, L = 8 \text{ nH/cm}, C = 1.07 \text{ pF/cm}$$

$$\Rightarrow \lambda = 1.0825 \text{ cm}$$

$$\Rightarrow \text{length of line} = \underline{\underline{\lambda/4 = 0.271 \text{ cm}}}$$