

Introduction to CMOS VLSI Design Delay Part A

Lecture by Jay Brockman
University of Notre Dame Fall 2008

Modified by Peter Kogge Fall 2010,2011, 2015, 2018

Based on lecture slides by David Harris, Harvey Mudd College
<http://www.cmosvlsi.com/coursematerials.html>

Delay A

Slide 1

Outline

- Delay Part A**
 - **Capacitance**
 - **Effective Resistance**
 - **RC Delay**
- Delay Part B**
 - Review
 - Inverter Delay
 - The Elmore Model
 - Effect of Load Capacitance


Delay A

CMOS VLSI Design

Slide 2

Capacitance

 - ❑ Conductors separated by insulator have capacitance
- ❑ **Gate to channel capacitor** is *very important*
 - Creates channel charge necessary for operation
- ❑ Source and drain have capacitance to body
 - Across reverse-biased diodes
 - Called **diffusion capacitance** because it is associated with source/drain diffusion




Delay A

CMOS VLSI Design

Slide 3

Gate Capacitance

 - ❑ Approximate channel as “connected to source”
- ❑ $C_{gs} = \epsilon_{ox} WL/t_{ox} = C_{ox} WL = C_{permicron} W$
 - *proportional to “width” ONLY*
- ❑ $C_{permicron} = \epsilon_{ox}(L/t_{ox})$ typically $\sim 2 \text{ fF}/\mu\text{m}$ of gate width
 - L and t_{ox} both scale with process
- ❑ Often just C_g



Delay A

CMOS VLSI Design

Slide 4

Caveat

- ❑ Statement that C_{gs} is proportional ONLY to width is true ONLY as long as Length and t_{ox} scale together
- ❑ We will assume this for rest of course
- ❑ BUT: **NOT TRUE** for really small feature sizes!


Delay A

CMOS VLSI Design

Slide 5

Denoting “Width”

 - ❑ Assume width of smallest transistor is W_s
- ❑ If actual width of a transistor is “ W ”
- ❑ Then relative width “ k ” is W/W_s
- ❑ **Write “ k ” inside transistor**




Delay A

CMOS VLSI Design

Slide 6

Diffusion Capacitance

- ❑ C_{sb}, C_{db} = “source/drain to bulk”
- ❑ Undesirable, called *parasitic* capacitance
- ❑ Capacitance depends on area and perimeter
 - Comparable to C_g for **contacted diffusion**
 - $\frac{1}{2} C_g$ for **uncontacted**
 - Varies with process
 - Often just C_d
- ❑ “Contacted diffusion” occurs when there is a metal contact “touching” the diffusion
 - i.e. there’s a “wire” on the source or drain
- ❑ Appears on both source & drain
 - But ignore when connected to V_{dd} or Gnd
 - Capacitance is “shorted out”

 


Delay A

CMOS VLSI Design

Slide 7

Contacted vs. Uncontacted Capacitance

 - ❑ Transistor Layout
 - Contacted Source/Drain – Physically Larger => more cap
 - Uncontacted Source/Drain – Smaller
- ❑ Example nmos transistors in NAND




Delay A

CMOS VLSI Design

Slide 8

 Let's Do An Example: How Many Diffusion Caps Are There? And Where?




Answer: ____

Delay A

CMOS VLSI Design

Slide 9

OK- How Many "Don't Count"?

 


Delay A

CMOS VLSI Design

Slide 10

OK- Which are Contacted?

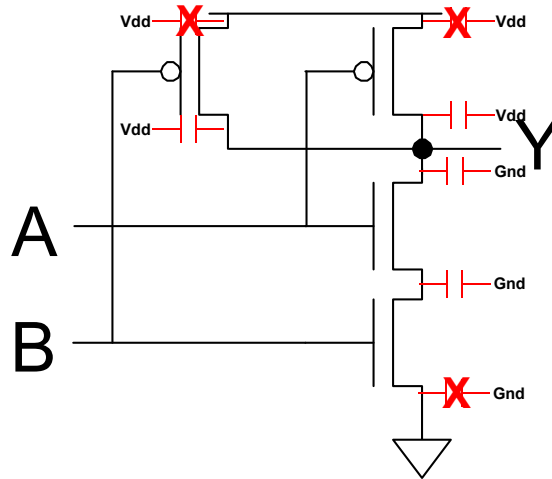


Delay A

CMOS VLSI Design

Slide 11

OK- What are Their Values?

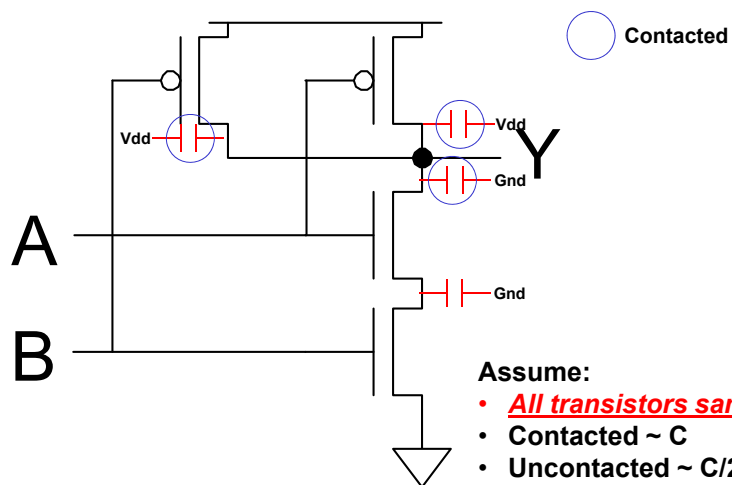


Delay A

CMOS VLSI Design

Slide 12

OK – What's the Final Model

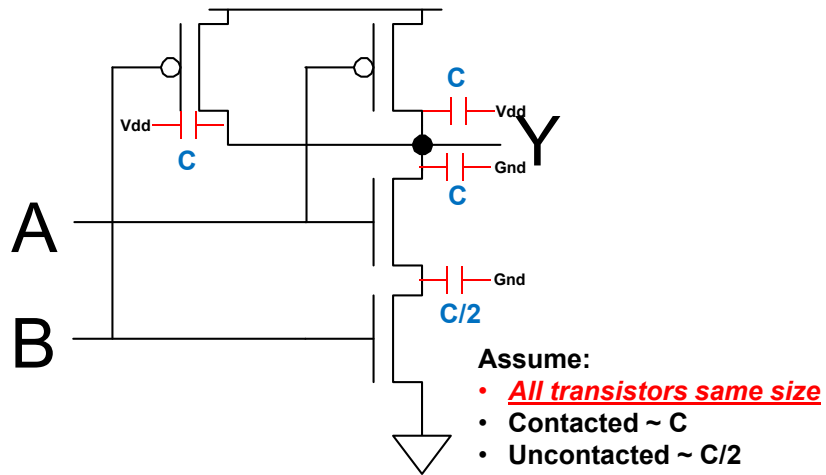


Delay A

CMOS VLSI Design

Slide 13

Final Model

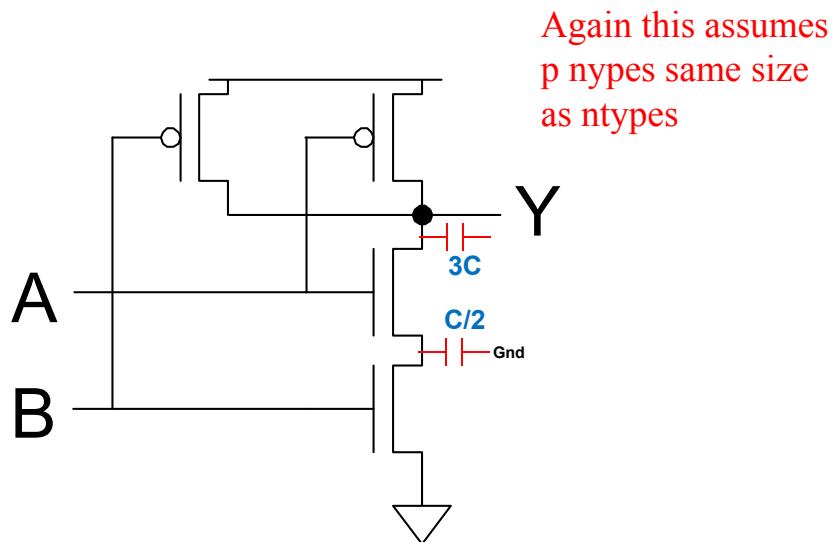


Delay A

CMOS VLSI Design

Slide 14

RC Delay Model

 - Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - **Unit nMOS** has resistance R , capacitance C
 - **Unit pMOS** has resistance $2R$, capacitance C
 - Why?
- Actual Capacitance proportional to minimum width “ k ”
- Actual Resistance inversely proportional to width “ k ”




Delay A

CMOS VLSI Design

Slide 15

Driving Another Gate

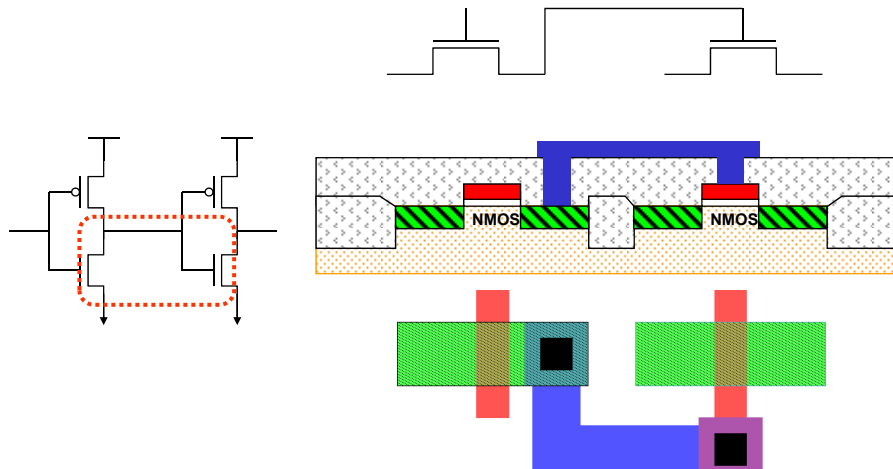


Output of 1st gate “sees” aggregate input capacitance of 2nd Gate
 Termed **Load Capacitance C_L**

Delay A



CMOS VLSI Design

Slide 16

Between Cells

 

Inverter "Stick Diagram"

  


Green: diffusion; Red: poly; Blue/gray: metal wire; black: contact

Delay A

CMOS VLSI Design

Slide 17

1st Inv Falling Output (1)

 


Before $t=0$, input stable & capacitor fully charged

Delay A

CMOS VLSI Design

Slide 18

Falling Output (2)

 


After $t=0$, capacitor discharges through NMOS

Delay A

CMOS VLSI Design

Slide 19

Rising Output (1)

 


Before $t=0$, input stable & capacitor fully discharged

Delay A

CMOS VLSI Design

Slide 20

Rising Output (2)

 

After $t=0$, capacitor charges through PMOS


Delay A

CMOS VLSI Design

Slide 21

Solving

 - How long does it take to discharge the output from starting voltage V_0 to voltage V_1 ?



Kirchhoff's current law at output

$$I_R = -I_C$$

$$\frac{V}{R} = -C \frac{dV}{dt}$$

$$\int_{t_0}^{t_1} dt = -RC \int_{V_0}^{V_1} \frac{1}{V} dV$$

$$t_1 - t_0 = -RC (\ln V_1 - \ln V_0)$$

$$= RC \ln \frac{V_0}{V_1}$$

If $V_1 = V_0/2$, Time = $RC \ln(2) = 0.69 RC$

REMEMBER THIS #!
Slide 22

Delay A

CMOS VLSI Design

Definitions


- Waveform
 - **Rise time t_r** = time to rise from 20% of Vdd to crossing 80% of Vdd
 - **Fall time t_f** = time fall from 80% of Vdd to crossing 20% of Vdd
 - **Edge Rate t_{rr}** = $(t_r + t_f)/2$
- Logic gate input to output
 - **Propagation delay t_{pd}** = max time from input crossing 50% of Vdd to output crossing 50% of Vdd
 - t_{pdr} = delay when input is rising
 - t_{pHL} = delay when output goes from High to Low
 - t_{pdf} = delay when input is falling
 - t_{pLH} = delay when output goes from Low to High
 - **Delay t_p** = $(t_{pHL} + t_{pLH})/2$
 - **Contamination delay t_{cd}** = min time from input crossing 50% of Vdd to output crossing 50% of Vdd
 - i.e **with no load on output, in either direction**

Delay A

CMOS VLSI Design

Slide 23

Delay Definitions


 


Delay A


CMOS VLSI Design

Slide 24

RC Propagation Delay Estimation

  

assume V_{in} rise time is 0

 

$$\begin{aligned} \Delta t &= RC \ln \frac{V_0}{V_1} \\ t_{PHL} &= RC \ln \frac{V_{dd}}{V_{dd}/2} \\ &= RC \ln(2) \\ &= .69RC \end{aligned}$$

Delay A

CMOS VLSI Design

Slide 25

Effective Resistance



- ❑ Shockley models have limited value
 - Not accurate enough for modern transistors
 - Too complicated for much hand analysis
- ❑ Simplification: treat transistor in on state as resistor
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with **Effective Resistance R**
 - $I_{ds} \sim V_{ds}/R$
 - R averaged across switching of digital gate
- ❑ Too inaccurate to predict current at any given time
 - **But good enough to predict RC delay**

Delay A

CMOS VLSI Design

Slide 26

Switching Voltages

  


Delay A

CMOS VLSI Design

Slide 27

Approximating Output Resistance (4.3.7)

 - ❑ Want Effective Resistance that has \sim same current as transistor when $V_{DS} = V_{dd}/2$
- ❑ No single R value matches transistor through switching event
- ❑ Approach:
 - Look at IV trajectory as input V_{gs} rises high enough to start transition
 - While still being in saturation
 - Compute average V/I on this trajectory



$$R = \ln(2) * (3/4) * V_{dd}/I_{dsat}$$

$$\sim (1/2) * (V_{dd}/I_{dsat})$$

Delay A

CMOS VLSI Design

Slide 28

Relating Back to Delay


- ❑ From before: $R = \ln(2) * (3/4) * V_{dd}/I_{dsat}$
- ❑ If we compute delay as $\ln(2) RC$
 - then $R \sim (3/4) * V_{dd}/I_{dsat}$
- ❑ If we compute delay as “R’C” then use above
 - I.e. choose effective R to include $\ln(2)$
 - OR: $t_{pd} = RC$

Delay A

CMOS VLSI Design

Slide 29

Let's Look at a Real Curve

 


Delay A

CMOS VLSI Design

Slide 30

Approximating R_{ON}

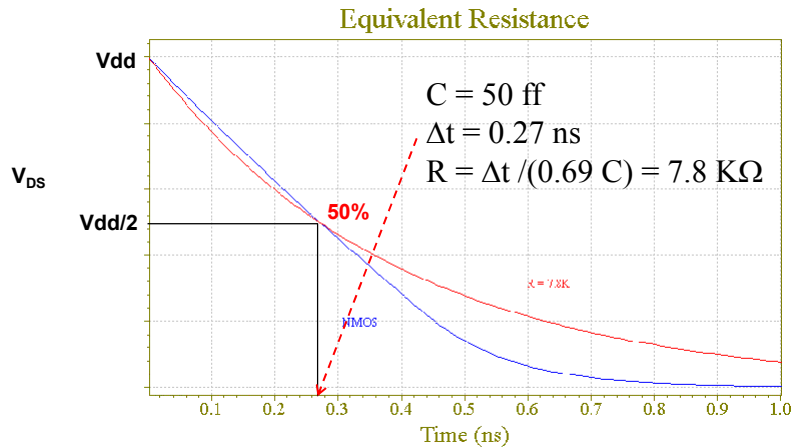

Delay A

CMOS VLSI Design

Slide 31

RC Values

- Capacitance

Question: Why?

 - $C \approx C_g \approx C_{sb} \approx C_{db} \approx 2 \text{ fF}/\mu\text{m}$ of gate width
 - Values similar across many processes for minimal gate length.
- Resistance

	V_{DD}
0.6 μm :	5 V
0.35 μm :	3.3 V
0.25 μm :	2.5 V
0.18 μm :	1.8 V
130 nm:	1.5 V
90 nm:	1.2 V

 - $I_{Dsat} \approx 550 \mu\text{A}/\mu\text{m}$
 - $V_{DD} \propto \lambda$
 - $R_{eq} \approx 0.75 V_{DD}/I_{dsat} \propto \lambda$
 - $R_{eq} \approx 7 \text{ K}\Omega \cdot \mu\text{m}$ in 0.6 μm process
 - $R_{eq} \approx 2 \text{ K}\Omega \cdot \mu\text{m}$ in 90 nm process
- Unit transistors
 - May refer to minimum contacted device ($4/2 \lambda$)
 - Or maybe 1 μm wide device
 - Doesn't matter as long as you are consistent

Delay A

CMOS VLSI Design

Slide 32

Drawing Equivalent Circuits for Delay

- Model rise and fall as separate circuits
- Look at only the output of logic gate being modeled
 - But consider capacitance from the gate it is driving
- Model transistors that turn “OFF” by an open
- Ignore all capacitors with both ends to a rail
- Model transistors that turn “ON” by their resistance
 - If source is V_{dd} or V_{gnd} , model voltage on that terminal as a “STEP Voltage”
- Ignore all capacitors with one end “floating”
- Lump ALL capacitors tied to same wire together
 - Ignore which rail other side goes to
- Draw as equivalent RC “Ladder” driven by step voltage

Delay A

CMOS VLSI Design

Slide 33