

# Introduction to CMOS VLSI Design

## Logical Effort Part A

Lecture by Jay Brockman

University of Notre Dame Fall 2008

Modified by Peter Kogge Fall 2010,2011,2015, 2018

Based on lecture slides by David Harris, Harvey Mudd College


<http://www.cmosvlsi.com/coursematerials.html>

Logical Effort A

Slide 1
 
# Introduction

- ❑ Chip designers face a bewildering array of choices
  - What is the best circuit topology?
  - What gives least delay?
  - How wide should the transistors be?
  
- ❑ **Logical effort:** a method to make these decisions
  - Simple model of delay
  - “Back-of-the-envelope”
  - Rapid comparisons between alternatives
  - Emphasizes remarkable symmetries




Logical Effort A

CMOS VLSI Design

Slide 2
 
# Motivating Example

- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the *decoder* for a 16x32 register file.




- Decoder specifications:
  - 16 word register file
  - Each word is 32 bits wide
  - Each file bit presents load of 3 unit-sized transistors
  - Both true & complementary address inputs  $A[3:0]$  available
  - Each address input may drive 10 unit-sized transistors
- Ben needs to decide:
  - How many stages to use in decoder driver output buffers?
  - How large should each gate be?
  - How fast can decoder operate?

Logical Effort A

CMOS VLSI Design

Slide 3

# Some Review

 

- $k$ : transistor's width is  $k$  times unit width
- On resistance is  $1/k$  times unit transistor
- $C_g$  is capacitance of gate to body
  - Unit transistor's  $C_g$  is "1 unit"
  - $C_{g-k}$  is  $k$  times  $C_{g-unit}$  of unit transistor
- $C_{diff}$  is capacitance to body from a contacted source or drain
  - Approximately =  $C_g$
- Diffusion capacitance of uncontacted source or drain is less (approx  $1/2$ )
  - For simplicity assume the same

Logical Effort A

CMOS VLSI Design

Slide 4

## N vs P Widths


- ❑ To make rise  $\approx$  fall time, want  $\sim$  equality between
  - On resistance of N side of circuit
  - On resistance of P side of circuit
- ❑ Remember
  - Unit width PMOS  $\approx$  2X unit width NMOS
  - Resistors in series add
  - Resistors in parallel =  $1/\text{sum}(\text{reciprocal of } R_s)$
- ❑ When multiple paths are possible
  - Reflecting multiple possible input conditions
  - Choose one with max resistance

Logical Effort A

CMOS VLSI Design

Slide 5

## Elmore Delay Model

 

**FIG 4.3** RC ladder for Elmore delay


$$\text{Delay} = \sum_1^{N-i} R_{n-i} C_i \sim \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Logical Effort A

CMOS VLSI Design

Slide 6

## What If Output Not At End?

 

Ignore  $R_2$  thru  $R_n$ , & just sum  $C$ 's

$$\text{Delay} = R_1 * \sum C_i$$

In reality,  $C_2, \dots, C_N$  "shielded" by  $R$ 's  
(don't have to charge all way to voltage at  $Y$ )  
Thus a "conservative" estimate

Logical Effort A

CMOS VLSI Design

Slide 7

## Resistance Examples

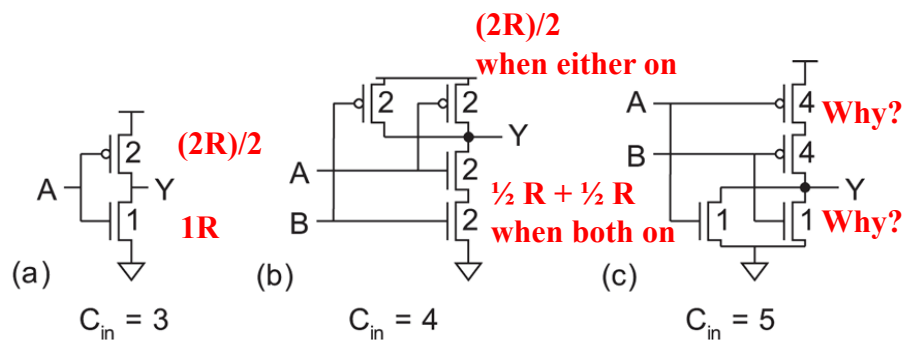



FIG 4.9 Logic gates sized for unit resistance

Logical Effort A

CMOS VLSI Design

Slide 8

## What's $C_{in}$ : the Input Capacitance?

 

**FIG 4.9** Logic gates sized for unit resistance

Assuming:

- gate size is indicated as # in each transistor
- gate capacitance of unit transistor  $1 C_g = C$

Logical Effort A

CMOS VLSI Design

Slide 9

## General Input Capacitance: Minimum Transistors

# of Inputs	NAND	NOR
1	3C: Inverter	
2	4C	5C
3	?	?
4	?	?
N	?	?


How About for K inputs:  $(K+2)C$        $(2K+1)C$

Logical Effort A


CMOS VLSI Design

Slide 10


# Sample Circuit Extraction

 

**FIG 4.1** 3-input NAND gate with unit rise and fall resistance

 

**FIG 4.2** 3-input NAND gate annotated with capacitances Assuming all diffusion nodes contacted

 

**FIG 4.3** 3-input NAND annotated with diffusion capacitances extracted from the layout

**Real world Slightly smaller**

# Key Definitions

- ❑ **Parasitic Delay:** gate delay when no load attached
  - Count only diffusion capacitances
- ❑ **Contamination Delay:** Minimum (fastest) time from some input changes until any output starts to change
  - Look for input pattern that minimizes delay
- ❑ **Logical Effort** of some gate: ratio of its input capacitance to input capacitance of inverter that can deliver same output current
  - I.e. has same pullup/pulldown resistance
- ❑ **Ideal Delay:** ideal inverter (with no parasitic diffusion capacitance) driving an identical inverter
- ❑ **Effort Delay:** Delay imposed by external load

# Approximate Parasitic Delay of Gates

- Parasitic delay = delay when it drives zero load
- Normalized to multiples of  $p_{inv} = 3RC$


Parasitic Delay (Normalized)					
Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

Logical Effort A

CMOS VLSI Design

Slide 13

# Real Life Parasitic Delay

 

Applying Elmore model when all but **lowest**=1 & lowest:0→1:

$$t_{pd} = (n^2/2 + 5n/2)RC$$

Note the square term!!!!

Big gates are *slooooooowwwweeeerrrrrr*


Logical Effort A

CMOS VLSI Design

Slide 14
 
# Contamination Delay

- ❑ **Minimum time** from some input change until any output starts to change for any input pattern
  - A function of load capacitance
- ❑ E.g. 3NAND: On fall, best if both bottom NMOS Ts on
  - Diffusion cap already drained
  - Only R effective left
  - Delay = ?
- ❑ On rise, best when ALL 3 PMOS turn on
  - Resistances in parallel
  - Delay = ?




Delay B


CMOS VLSI Design

Slide 15

# 3 Input NAND

 


(a)

 


(b)

**FIGURE 4.7** Equivalent circuits for a 3-input NAND gate

 

(c)

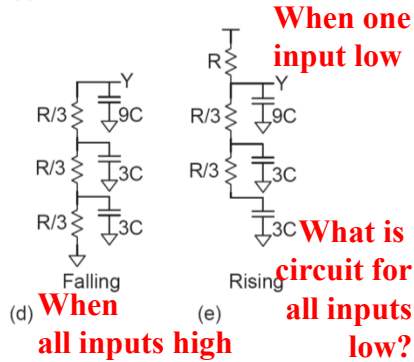

(d) **When all inputs high**

(e) **When one input low**  
**What is circuit for all inputs low?**

Logical Effort A


CMOS VLSI Design

Slide 16


 
# Logical Effort

- ❑ **Logical effort  $g$** : ratio of input capacitance of a gate to the input capacitance of an inverter *delivering the same output current* (same pullup/down resistance).
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths
- ❑ **AND divide by 3 to “normalize”**



Logical Effort A

CMOS VLSI Design

Slide 17

# Logical Effort of Gates

Logical Effort (Normalized)					
Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	?

*All inputs are not the same!*


Logical Effort A

CMOS VLSI Design

Slide 18
 
# Now Consider Loaded Gates

- Estimate worst-case rising and falling delay of 2-input NAND driving  $h$  identical 2in NAND gates.




Logical Effort A

CMOS VLSI Design

Slide 19

# Summary Delay Estimation

Assume driving  $h$  identical 2in NANDS

 

**FIG 4.6** NAND gate delay estimation

Elmore delays:

$$\text{Worst Case Rise} = R(6+4h)C = (6+4h)RC$$

$$\text{Worst Case Fall} = (R/2)(2C) + R*(6+4h)C = (7+4h)RC$$


Logical Effort A

CMOS VLSI Design

Slide 20

## What If All Transistors *k Wider?*

- What happens to capacitances? Resistance?
- Assume output load =  $4h'C$ 
  - $h'=h$  if driving small gates; =  $kh$  if larger gates

 

**FIG 4.7** Scaled NAND gate delay estimation

Elmore delays if driving  $h$  copies of scaled gates:


$$\text{Worst Case Rise} = (6+4h)RC$$

$$\text{Worst Case Fall} = (7+4h)RC$$

The same as before: **WHY?**

 
## Ideal Gate Delay $\tau$

- Imagine *ideal inverter* (with *no* parasitic diffusion capacitance) driving *an identical inverter*



$$\tau = 3RC = \text{Ideal Inverter Delay}$$

# What If We Count Diffusion?

 


- ❑ delay =  $6RC = 3RC$  (from diffusion) +  $3RC$  (from load)
- ❑ Let's convert to **normalized delay**
  - Divide by  $\tau = 3RC$
  - Get  $2\tau$
- ❑ So *real* gate has **TWICE** delay of our "*ideal*"

Logical Effort A

CMOS VLSI Design

Slide 23

# Sample Inverters

 

Capacitance =  $3C$  (diffusion)  
+  $h3C$  (combined load)

Delay =  $R*(3C + h3C)$

Dividing by  $t = 3RC$  yields

$$1 + h$$

This is *normalized delay* of a **Fanout of h inverter** – denoted  $FO^h$

Logical Effort A

CMOS VLSI Design

Slide 24

## Linear Delay Model

$$\text{delay } d = p + f = p + hg$$

Prior delay had two parts

- **p: Parasitic delay**
  - 3RC for inverter
  - *Independent* of load
- **f: Effort delay**
  - 3h RC
  - *Proportional* to total load capacitance
- =  $h \cdot g$  if driving *identical* circuits
  - $h$  = # of copies of gate (also called "**Fanout**")
  - $g$  = "**Logical Effort**" (function of gate complexity)
    - 3RC for simple inverter

Logical Effort A

CMOS VLSI Design

Slide 25

## Normalized Linear Delay

- Remember
  - 3RC = parasitic delay of inverter
  - 3RC + 3hRC = delay if driving h copies
- **Normalized delay**: divide delay by 3RC
  - Measure of how much "slower" a circuit is than an inverter
  - = 1 + h for inverter driving h inverters

Logical Effort A

CMOS VLSI Design

Slide 26

## What If We're Not Driving Identical Copies of Self?

- ❑ Let  $C_{in}$  = input capacitance of gate *doing the driving*
- ❑ Let  $C_{out}$  = total capacitance *of load* presented to gate
- ❑ Express **fanout h** as  $C_{out}/C_{in}$ 
  - Also called the **electrical effort**
  - How many equivalent copies of driving gate the actual load is

Logical Effort A

CMOS VLSI Design

Slide 27

## Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$\tau = 3RC$  for ideal inverter  
 $\approx 12$  ps in 180 nm process  
 $40$  ps in 0.6  $\mu\text{m}$  process

Logical Effort A

CMOS VLSI Design

Slide 28

## Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

f: property of driven circuit

p: property of driving gate

## Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- **Parasitic delay  $p$**

- Represents delay of gate driving no load
- Set by internal parasitic capacitance

## Question?

- ❑ What happens to Parasitic Delay  $p$  if we scale all transistors by same factor?
  - Drops
  - Stays the same
  - Increases

## Delay in a Logic Gate

- ❑ Express delays in *process-independent unit*

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ **Effort delay**  $f = gh$  (a.k.a. stage effort)

- Again has two components

- ❑  $g$ : **logical effort**

- Measures *relative* ability of gate to deliver current
  - $g \equiv 1$  for unit inverter



## Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$


- Effort delay  $f = gh$  (a.k.a. stage effort)

- Again has two components

- $h$ : **electrical effort** =  $C_{out} / C_{in}$

- Ratio of output to input capacitance of driving gate

- Sometimes called **fanout**

 

Logical Effort A

CMOS VLSI Design

Slide 33

## Question?

- What happens to Logical Effort  $g$  if we scale all transistors by same factor?

- Drops
- Stays the same
- Increases

Logical Effort A

CMOS VLSI Design

Slide 34