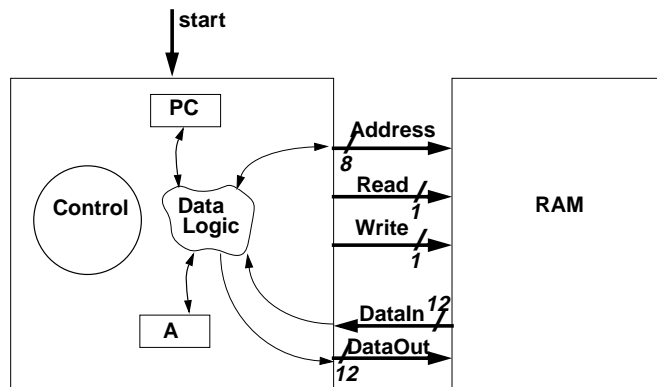


## Unit 4 A Simple Processor Simple-12

### What is Simple-12?

- Expansion of MaxFinder into a simple computer
- Reminiscent of first true computers
- Focus on Micro operations, Micro Instructions, Microprograms
- Gain some experience with design-induced limitations

### SIMPLE-12 Basic Organization



Programmer Visible Registers:


A: Accumulator: - Holds 12 data bits

PC: Program Counter- Holds 8 bits of current instruction address

Question: Is this a **Harvard** or **Princeton** machine?

### Simple-12: Skeleton Microprogram

#### Instruction Format:

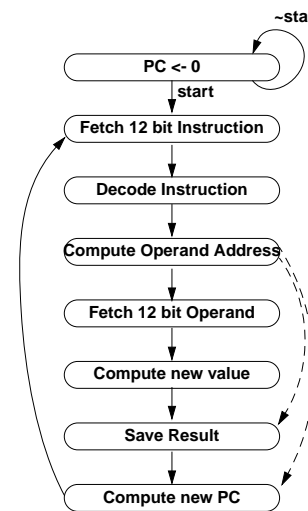

Machine general properties

- 256 words of 12 bits each
- Addresses all 8 bits wide
- Opcode selects one of 16 instructions from 4 Classes:
  - Jump Class: change PC
  - Load/Store Class: access memory
  - Operate Class: compute new value
  - Reserved (for your later enjoyment)


Dotted lines represent instructions which do not need certain micro-instructions

### Simple-12 Instruction Set Architecture (ISA)

Opcode	Mnemonic	RTL
0000	JMP X	PC<-X
0001	JN X	if A<0 then PC<-X else PC++
0010	JZ X	if A=0 then PC<-X else PC++
0011	reserved	
0100	LOAD X	A<-M(X)    PC++
0101	STORE X	M(X)<-A    PC++
0110	reserved	
0111	reserved	
1000	AND X	A<- A and M(X)    PC++
1001	OR X	A<- A or M(X)    PC++
1010	ADD X	A<- A + M(X)    PC++
1011	SUB X	A<- A - M(X)    PC++
1100	reserved	
1101	reserved	
1110	reserved	
1111	reserved	

After each instruction completes, next instruction is from Mem(PC)


### A MaxFinder-Like Organization

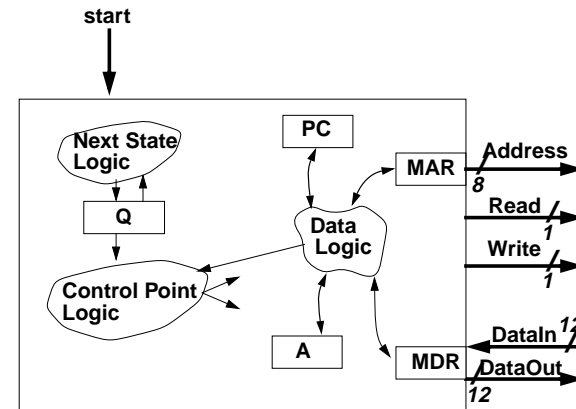

Note: Q, MAR, MDR are part of organizational view of SIMPLE-12

Note!!!: Q, MAR, MDR are NOT PART of architecture; They are NOT VISIBLE to the programmer!

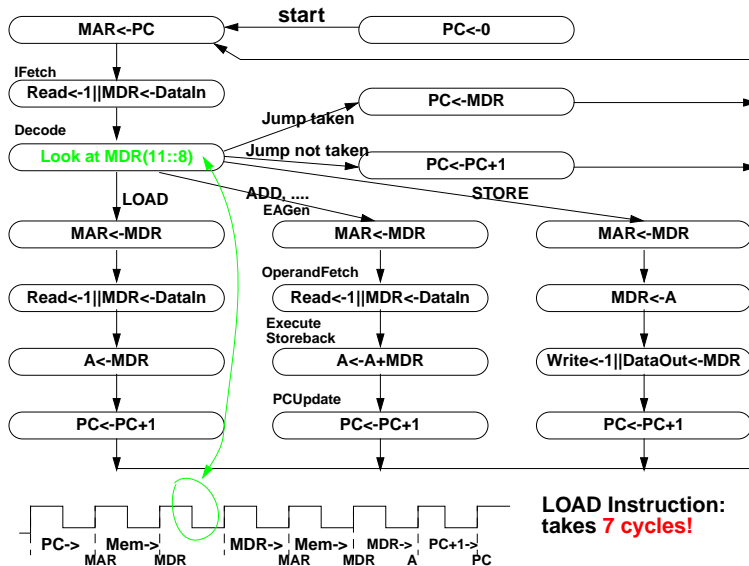
### A More Detailed Microprogram (Moore Machine)



### Instruction Cycle Count

Opcode	# Cycles	# Memory Reads	# Memory Writes
JMP X	4	1	0
JN X	4	1	0
JZ X	4	1	0
LOAD X	7	2	0
STORE X	7	1	1
AND X	7	2	0
OR X	7	2	0
ADD X	7	2	0
SUB X	7	2	0

### Aside: State Machine Types & Timing

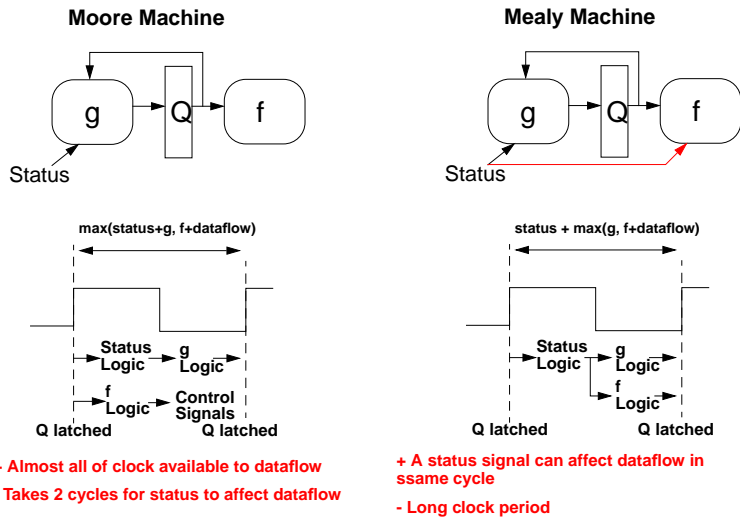

### Potential Improvements

- Moore model forbids using instruction being read in from memory at ifetch from being used in immediate decode
  - Cannot use it in next cycle for control signals because opcode is in MDR, not Q
  - Thus for pure Moore model, we must wait one cycle to get opcode into Q
- Solution: Add a new register IR
  - Loaded from memory bits 11 thru 8 at same time as MDR
  - Serves directly as part of Q state register
- Why waste a cycle in each instruction moving PC to MAR?
  - Include this microoperation at same time that PC is updated
- The only write to memory is from A. Why not tie it to Data\_out and save the cycle of transfer MDR<-A?
- We often have a separate cycle PC<-PC+1
  - Why not do this operation in parallel with some other operation
- Most microinstructions are “the same” or “similar” across multiple instruction opcodes
  - Why not group into common states (requires IR as part of Q)
- Several other improvements possible

### A Revised Microprogram in RTL


```

Stopped: If start=1 then (MAR<-PC<-0 || -> IFetch) else -> stopped
IFetch: Read<-1 || MDR<-DataIn || PC<-PC+1 || IR<-DataIn(11:8)||->EAGen
EAGen: if (IR=JMP) or (IR=JN and A(11)=1) or (IR=JZ and A=0)
      then (MAR<-PC<-MDR(7:0) || ->IFetch)
      else if (IR=JN) or (IR=JZ) then (MAR <-PC || ->IFetch)
      else MAR<-MDR(7:0) || ->OperandAccess
OperandAccess: MAR<-PC ||
              if IR=LOAD or IR(3:2)=10
              then (Read<-1 || MDR<-DataIn || -> Execute)
              else (i.e. a STORE) Write<-1 || DataOut<-A || ->IFetch
Execute: -> IFetch ||
        if IR=LOAD then A<- MDR
        else if IR=ADD then ....
    
```

Note: Mealy dependency of dataflow on A(11), A=0

Note: If Read or Write are not specified in a state, then they must be 0


### Revised Timing

 

Opcode	Cycles
JMP X	2
JN X	2
JZ X	2
LOAD X	4
STORE X	3
AND X	4
OR X	4
ADD X	4
SUB X	4
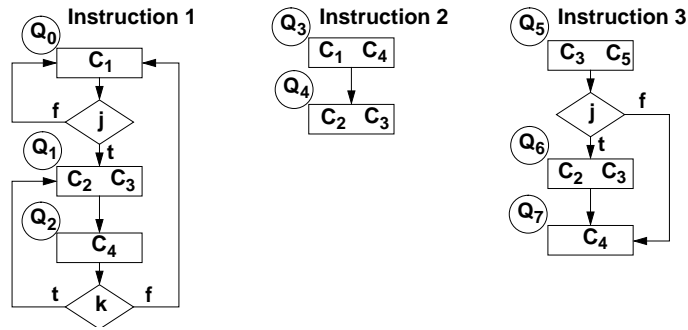
### Microprogram Controller Design

**Objective:** Design a controller that interprets each machine language instruction as a microprogram routine.  
**Insight:** Decode machine language op-code to determine starting state (address) of microprogram routine.




### Now Let's Tackle the DataFlow Design

First, what dataflow microoperations have to be done (and concurrently)?

- PC<-0
- MDR<-DataIn || IR<-DataIn || PC<-PC+1
- MAR<-MDR(7:0) || PC <- MDR(7:0)
- MAR<-PC
- A<-MDR
- A<-A+MDR
- A<-A-MDR
- A<-A and MDR
- A<-A or MDR

Resulting Control Points:

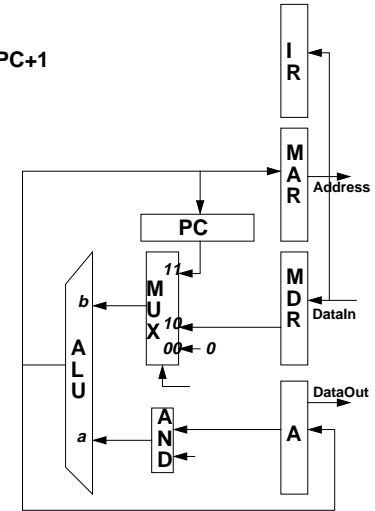- Load Signals for each register:
  - LoadPC, Load MDR, ...
- ALU Controls (4 bits)
  - b-invert, carry-in, op1, op0
- MUX1: Select PC, MDR, 0
- AND: Select 0 (0) or A



### Mealy Design Problem

Observation on RTL at State EAGen: we have a Mealy Machine where dataflow operations depend on status signals A(11) and A=0

EAGen: if (IR=JMP) or (IR=JN and A(11)=1) or (IR=JZ and A=0)  
 then (MAR<-PC<-MDR(7:0) || ->IFetch)  
 else if (IR=JN) or (IR=JZ) then (MAR <-PC || ->IFetch)  
 else MAR<-MDR(7:0) || -> OperandAccess

With current dataflow, using ALU zero tester to test A=0, we cannot test A and then change inputs to ALU to either MDR or PC **IN SAME CYCLE!**

One solution: insert an extra step for jumps not taken.

### Control Signal Table

Q	IR	s	A <sub>11</sub>	=0	Q*	L A	L P C	L M A R	L M D R	L I R	A L U	b M U X	a G a t e	R e a d	W r i t e
Stopped		0			Stopped	0	0	0	0	0				0	0
Stopped		1			IFetch	0	1	1	0	0	+	0		0	0
Ifetch					EAGen	0	1	0	1	1	+1	PC		0	1
EAGen	JMP				IFetch	0	1	1	0	0	+	MDR		0	0
EAGen	JN		1		IFetch	0	1	1	0	0	+	MDR		0	0
EAGen	JN		0		IFetch	0	0	1	0	0	+	PC		0	0
EAGen	JN		0		IFetch	0	0	1	0	0	+	PC		0	0
EAGen	JN		1		NoJump										
EAGen	JZ			1	IFetch	0	1	1	0	0	+	MDR		0	0
EAGen	JZ			0	IFetch	0	0	1	0	0	+	PC		0	0
EAGen	JZ			0	IFetch	0	0	1	0	0	+	PC		0	0
EAGen	JZ			1	NoJump										
EAGen	010X				Opnd	0	0	1	0	0				0	0
EAGen	10XX				Opnd	0	0	1	0	0				0	0
EAGen	0011				?	0	0	0	0	0				0	0
EAGen	010X				?	0	0	0	0	0				0	0

### Control Signal Table (Cont).

Q	IR	s	A <sub>11</sub>	=0	Q*	L A	L P C	L M A R	L M D R	L I R	A L U	b M U X	a G a t e	R e a d	W r i t e
Opnd	LOAD				Execute	0	0	0	1	0				1	0
Opnd	10XX				Execute	0	0	0	1	0				1	0
Opnd	STORE				IFetch	0	0	0	0	0				0	1
Execute	LOAD				IFetch	1	0	0	0	0	+	MDR	0	0	0
Execute	AND				IFetch	1	0	0	0	0	AND	MDR	1	0	0
Execute	OR				IFetch	1	0	0	0	0	OR	MDR	1	0	0
Execute	ADD				IFetch	1	0	0	0	0	+	MDR	1	0	0
Execute	SUB				IFetch	1	0	0	0	0	-	MDR	1	0	0
NoJump					IFetch	0	0	1	0	0	+	PC	0	0	0

NoJump is an added state to avoid Mealy Problem

### Designing for a Microprogrammed Implementation


Decisions to make:

- What is overall structure of microprogram in terms of microaddresses
- How are we going to sequence thru these microinstructions
- How do we design the microsequencer
- What are the fields of the microinstructions

There are no *single correct* answers! *Many solutions* possible

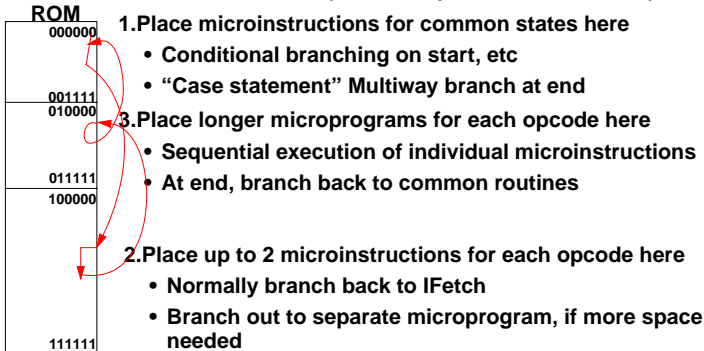
### What is overall Structure & Sequencing

- Some states like Stopped, IFetch are common to all opcodes
- There are 16 opcodes, so it makes sense to at some point have 16 separate microinstructions, one for each opcode
- Each opcode has a sequence of somewhat distinct OperandAccess & Execute microinstructions
- Prior tables identified potentially 22 separate microinstructions: assume we have room for 64 (some “slop” for additions later)




### Microprogrammed Design: Sequencing Logic


Note: we will make IR “part” of Q

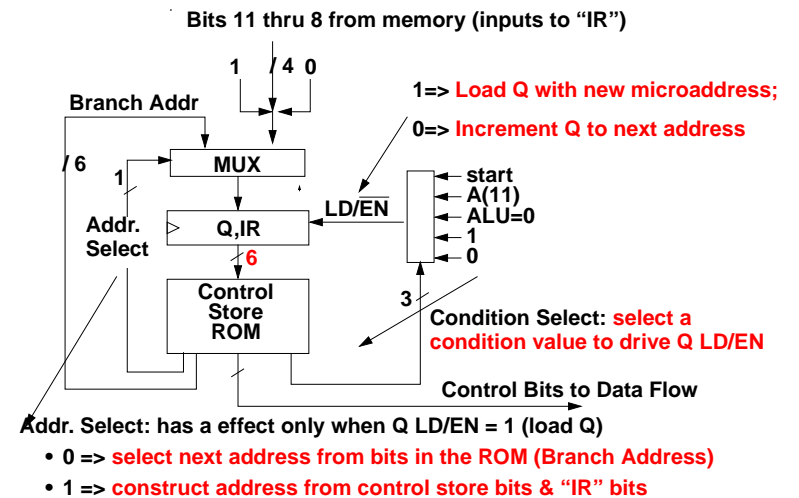


### Microinstruction Template

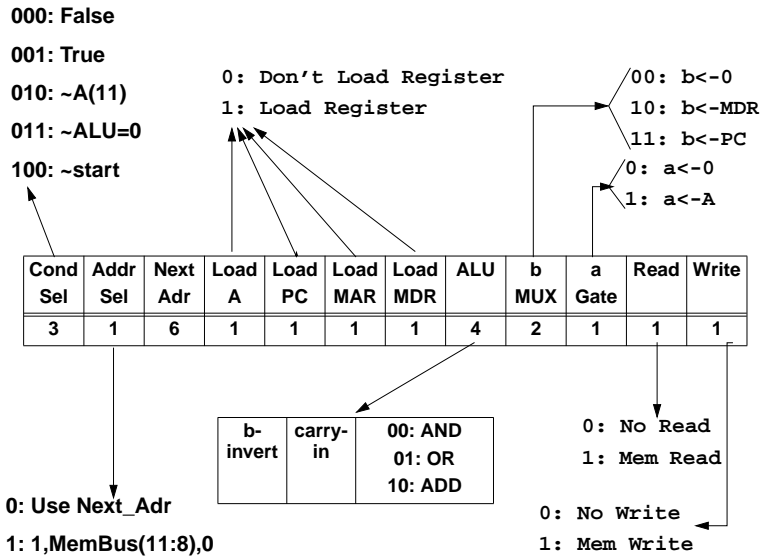


### Sample Microinstruction

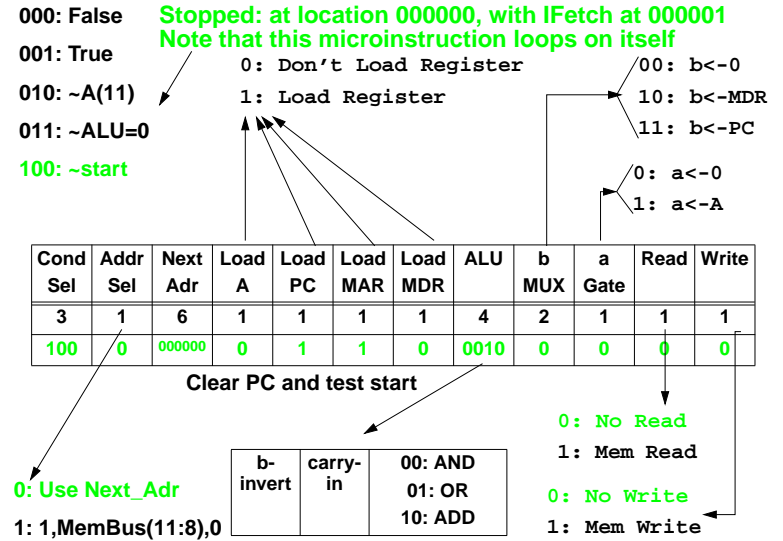

### Sample Microinstruction

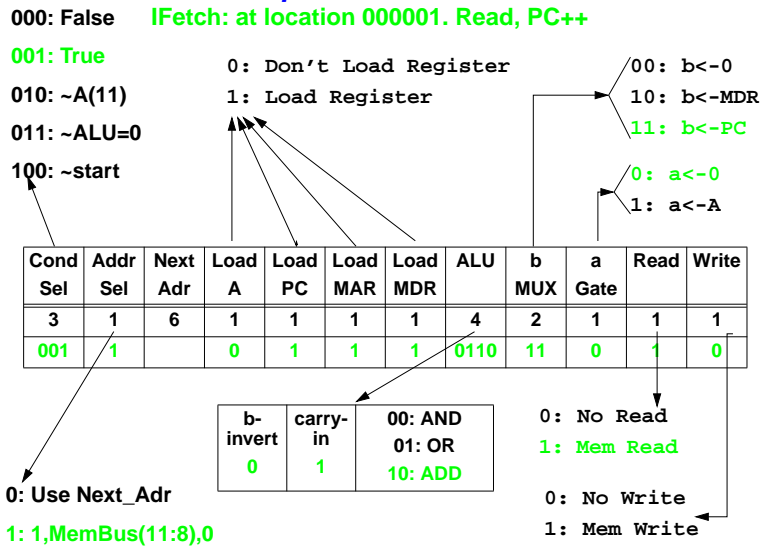

### Your Turn

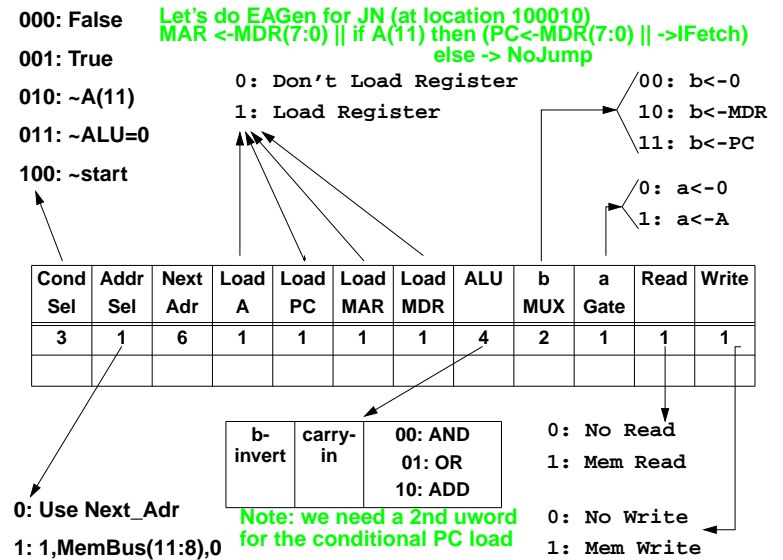

### Microprogram (page 1)

Adr	Cond Sel	Addr Sel	Next Addr	Load A	Load PC	Load MAR	Load MDR	ALU	b MUX	a Gate	Read	Write
000000	100	0	000000	0	1	1	0	0010	0	0	0	0
000001	001	1		0	1	1	1	0110	11	0	1	0
000010												
000011												
000100												
000101												
000110												
000111												
001000												
001001												
001010												
001011												
001100												
001101												
001110												
001111												

- Stopped = 000000: clear PC & test start
- IFetch=000001: Do a multiway branch by loading IR (part of Q)

### Microprogram (page 2)

Adr	Cond Sel	Addr Sel	Next Addr	Load A	Load PC	Load MAR	Load MDR	ALU	b MUX	a Gate	Read	Write
010000												
010001												
010010												
010011												
010100	001	0	000001	1	0	0	0	0010	10	0	0	0
010101												
010110												
010111												
011000	001	0	000001	1	0	0	0	0000	10	1	0	0
011001	001	0	000001	1	0	0	0	0001	10	1	0	0
011010	001	0	000001	1	0	0	0	0010	10	1	0	0
011011	001	0	000001	1	0	0	0	1110	10	1	0	0
011100												
011101												
011110												
011111												

- \* The microinstructions here are ones that overflowed from the latter half
- \* Suggestion: have 01wxyz be a spare location for opcode program 1wxyz0, not all opcodes need an extra spot.

### Microprogram (page 3)

Adr	Cond Sel	Addr Sel	Next Addr	Load A	Load PC	Load MAR	Load MDR	ALU	b MUX	a Gate	Read	Write
100000	001	0	000001	0	1	1	0	0010	10	0	0	0
100001												
100010	010	0	000001	0	0	0	0				0	0
100011	001	0	000001	0	1	1	0	0010	10	0	0	0
100100	011	0	000001	0	0	0	0					
100101	001	0	000001	0	1	1	0	0010	10	0		
100110												
100111												
101000	000			0	0	1	0	0010	10	0	0	0
101001	001	0	010100	0	0	0	1				1	0
101010	000			0	0	1	0	0010	10	0	0	0
101011	001	0	000001	0	0	0	0				0	1
101100												
101101												
101110												
101111												

- Microaddress of 1wxyz0 is 1st of 2 locations set aside for opcode wxyz, starting with EAGen
- Thus 101000 is start of microprogram for LOAD (opcode 0100) with 101001 being the operand access cycle

### Microprogram (page 4)

Adr	Cond Sel	Addr Sel	Next Addr	Load A	Load PC	Load MAR	Load MDR	ALU	b MUX	a Gate	Read	Write
110000	000			0	0	1	0	0010	10	0	0	0
110001	001	0	011000	0	0	0	1				1	0
110010	000			0	0	1	0	0010	10	0	0	0
110011	001	0	011001	0	0	0	1				1	0
110100	000			0	0	1	0	0010	10	0	0	0
110101	001	0	011010	0	0	0	1				1	0
110110	000			0	0	1	0	0010	10	0	0	0
110111	001	0	011011	0	0	0	1				1	0
111000												
111001												
111010												
111011												
111100												
111101												
111110												
111111												